




PHYS102 - Capacitors

Dr. Suess


February 16, 2007



Capacitors

Capacitors Energy Symbols Circuits

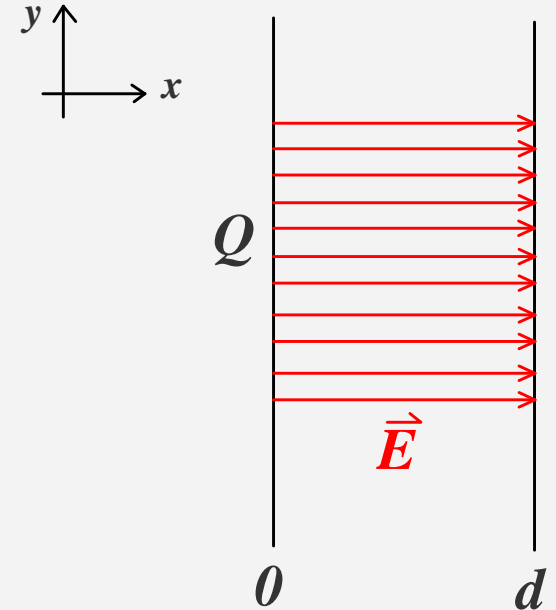
- When using a pair of conductors to store energy, we term the pair of conductors a capacitor.



Capacitors

Capacitors Energy Symbols Circuits

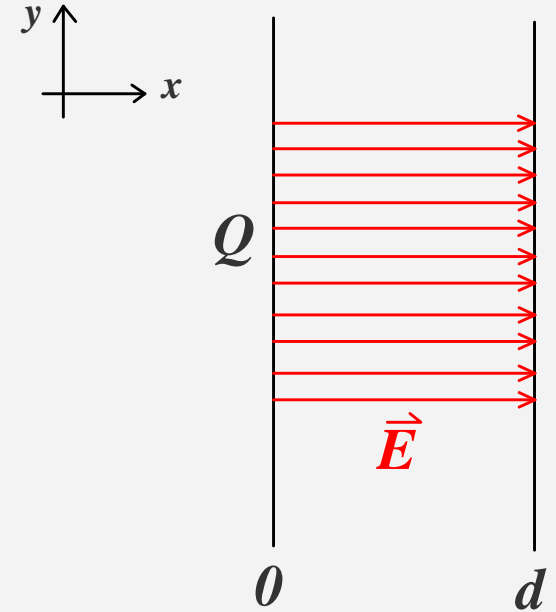
- When using a pair of conductors to store energy, we term the pair of conductors a capacitor.



Capacitors

Capacitors Energy Symbols Circuits

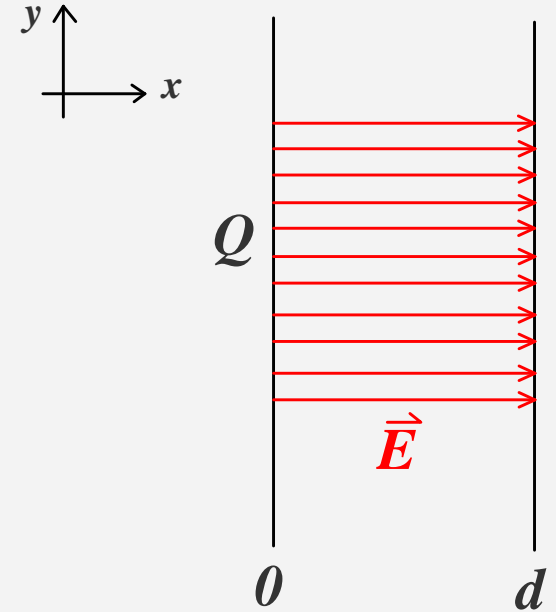
- When using a pair of conductors to store energy, we term the pair of conductors a capacitor.
- Capacitors typically used to store short-term electrical energy.



Capacitors

Capacitors Energy Symbols Circuits

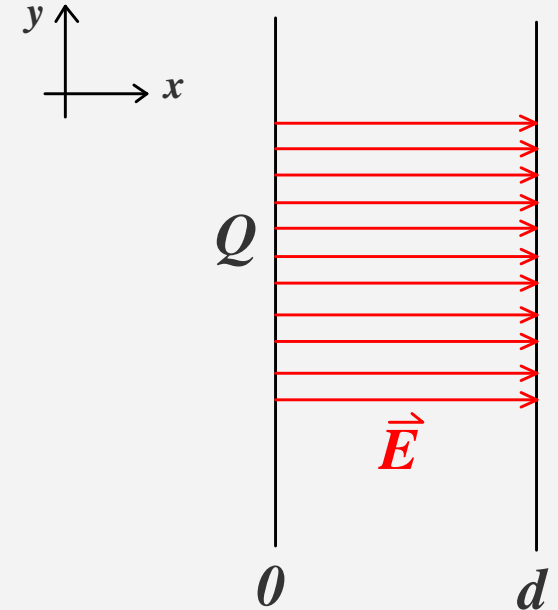
- When using a pair of conductors to store energy, we term the pair of conductors a capacitor.
- Capacitors typically used to store *short-term* electrical energy.



Capacitors

Capacitors Energy Symbols Circuits

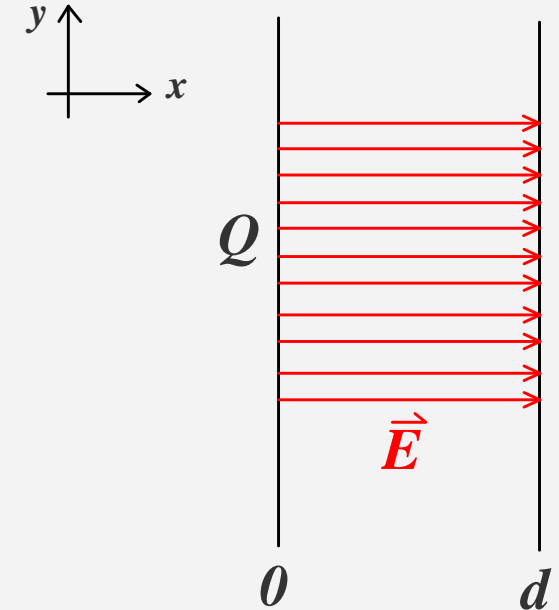- When using a pair of conductors to store energy, we term the pair of conductors a capacitor.
- Capacitors typically used to store *short-term* electrical energy.
- Consider our previous example:




Capacitors

Capacitors Energy Symbols Circuits

- When using a pair of conductors to store energy, we term the pair of conductors a capacitor.
- Capacitors typically used to store *short-term* electrical energy.
- Consider our previous example:

$$|\Delta V| = \frac{Q d}{\epsilon_0 A}$$

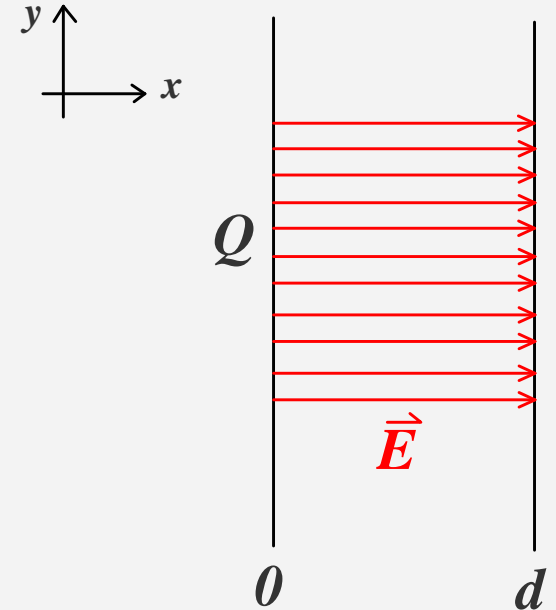


Capacitors

Capacitors Energy Symbols Circuits

- When using a pair of conductors to store energy, we term the pair of conductors a capacitor.
- Capacitors typically used to store *short-term* electrical energy.
- Consider our previous example:

$$|\Delta V| = \frac{Q d}{\epsilon_0 A} \rightarrow |\Delta V| \propto Q$$

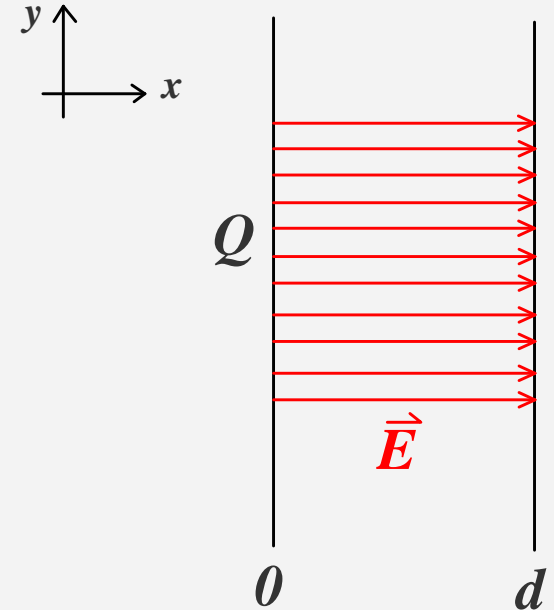


Capacitors

Capacitors Energy Symbols Circuits

- When using a pair of conductors to store energy, we term the pair of conductors a capacitor.
- Capacitors typically used to store *short-term* electrical energy.
- Consider our previous example:

$$|\Delta V| = \frac{Q d}{\epsilon_0 A} \rightarrow |\Delta V| \propto Q$$


$$|\Delta V| = Q \left(\frac{d}{\epsilon_0 A} \right)$$

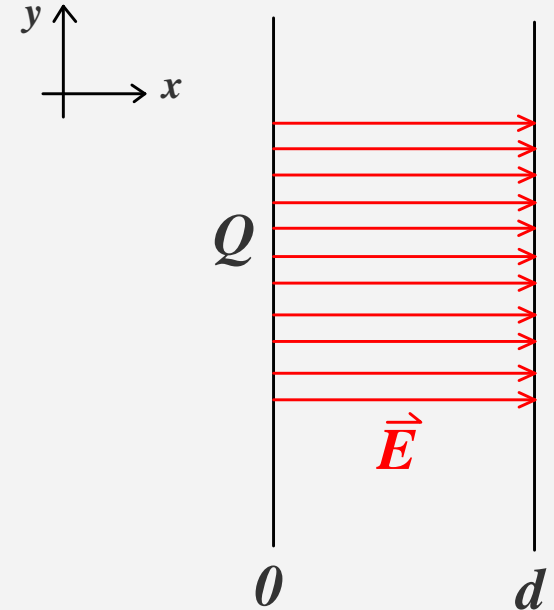

Capacitors II

Capacitors Energy Symbols Circuits

$$|\Delta V| = Q \left(\frac{d}{\epsilon_0 A} \right)$$

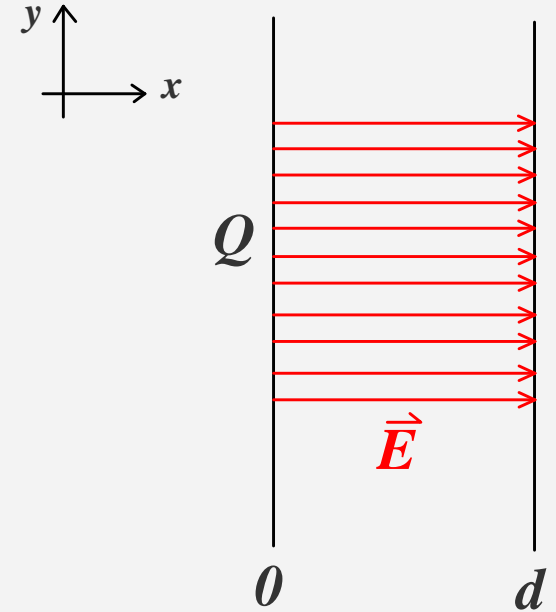


Capacitors II

Capacitors Energy Symbols Circuits

$$|\Delta V| = Q \left(\frac{d}{\epsilon_0 A} \right)$$

- Rewriting to find the amount of charge Q .

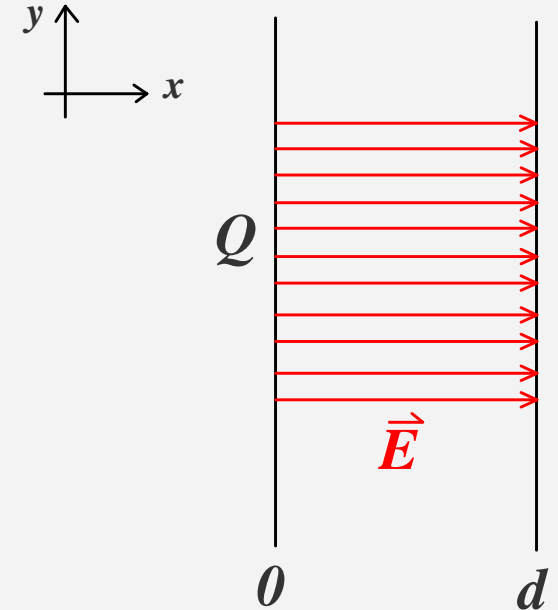


Capacitors II

Capacitors Energy Symbols Circuits

$$|\Delta V| = Q \left(\frac{d}{\epsilon_0 A} \right)$$

- Rewriting to find the amount of charge Q .

$$Q = |\Delta V| \left(\frac{\epsilon_0 A}{d} \right)$$

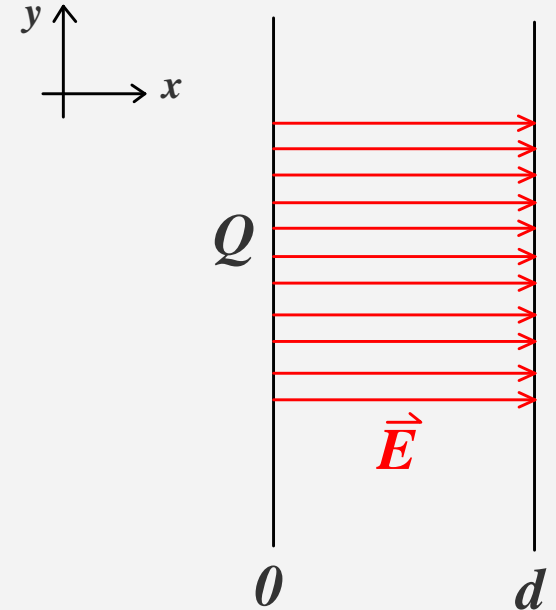


Capacitors II

Capacitors Energy Symbols Circuits

$$|\Delta V| = Q \left(\frac{d}{\epsilon_0 A} \right)$$

- Rewriting to find the amount of charge Q .

$$Q = |\Delta V| \left(\frac{\epsilon_0 A}{d} \right) \rightarrow \frac{Q}{|\Delta V|} = \frac{\epsilon_0 A}{d}$$

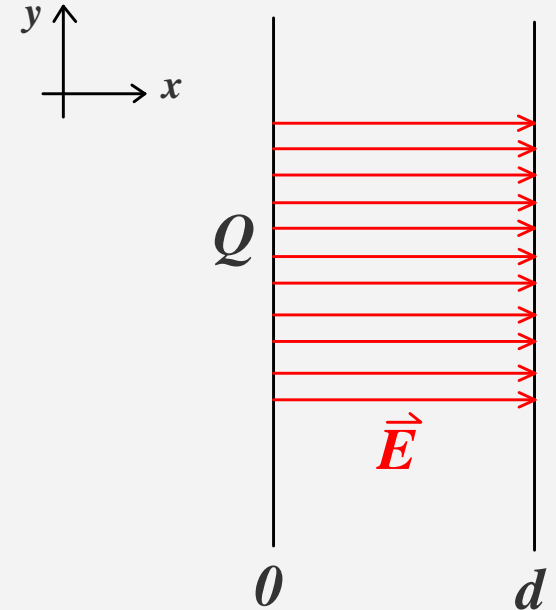

Capacitors II


Capacitors Energy Symbols Circuits

$$|\Delta V| = Q \left(\frac{d}{\epsilon_0 A} \right)$$

- Rewriting to find the amount of charge Q .

$$Q = |\Delta V| \left(\frac{\epsilon_0 A}{d} \right) \rightarrow \frac{Q}{|\Delta V|} = \frac{\epsilon_0 A}{d}$$

- Notice that the ratio Q/V depends only the geometry of the specific problem.

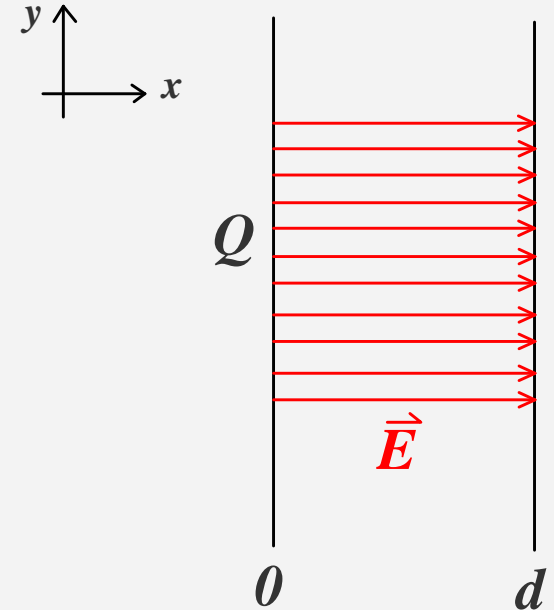

Capacitors II


Capacitors Energy Symbols Circuits

$$|\Delta V| = Q \left(\frac{d}{\epsilon_0 A} \right)$$

- Rewriting to find the amount of charge Q .

$$Q = |\Delta V| \left(\frac{\epsilon_0 A}{d} \right) \rightarrow \frac{Q}{|\Delta V|} = \frac{\epsilon_0 A}{d}$$

- Notice that the ratio Q/V depends only the geometry of the specific problem.
- The ratio $C \equiv Q/V$ is termed the capacitance.

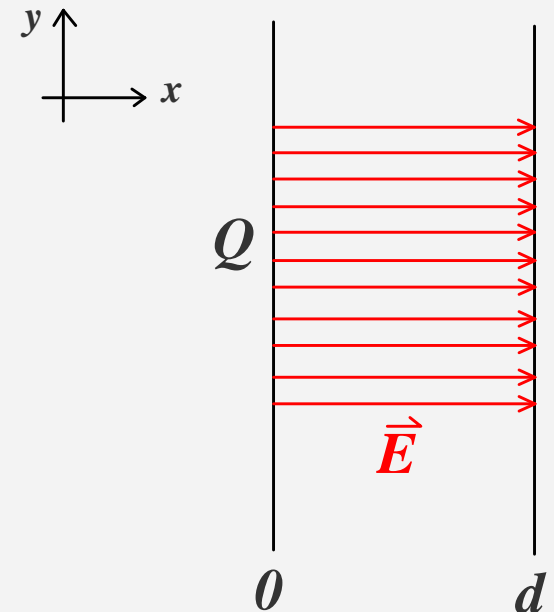



Capacitors II



Capacitors Energy Symbols Circuits

- C is a measure of the capacity to store charge for a given potential difference across two conductors.

Capacitors II

Capacitors Energy Symbols Circuits

- C is a measure of the capacity to store charge for a given potential difference across two conductors.
- The unit of capacitance is one “Farad”.

Capacitors II

Capacitors Energy Symbols Circuits

- C is a measure of the capacity to store charge for a given potential difference across two conductors.
- The unit of capacitance is one “Farad”.

$$[C] = \frac{[Q]}{[V]} = 1\text{C} / 1\text{V} \equiv 1\text{Farad}$$

Capacitors II

Capacitors Energy Symbols Circuits

- C is a measure of the capacity to store charge for a given potential difference across two conductors.
- The unit of capacitance is one “Farad”.

$$[C] = \frac{[Q]}{[V]} = 1\text{C} / 1\text{V} \equiv 1\text{Farad}$$

- 1 Farad is a very large value, and typical values of capacitance are:

Capacitors II

Capacitors Energy Symbols Circuits

- C is a measure of the capacity to store charge for a given potential difference across two conductors.
- The unit of capacitance is one “Farad”.

$$[C] = \frac{[Q]}{[V]} = 1\text{C} / 1\text{V} \equiv 1\text{Farad}$$

- 1 Farad is a very large value, and typical values of capacitance are:pF

Capacitors II

Capacitors Energy Symbols Circuits

- C is a measure of the capacity to store charge for a given potential difference across two conductors.
- The unit of capacitance is one “Farad”.

$$[C] = \frac{[Q]}{[V]} = 1\text{C} / 1\text{V} \equiv 1\text{Farad}$$

- 1 Farad is a very large value, and typical values of capacitance are:pF, nF

Capacitors II

Capacitors Energy Symbols Circuits

- C is a measure of the capacity to store charge for a given potential difference across two conductors.
- The unit of capacitance is one “Farad”.

$$[C] = \frac{[Q]}{[V]} = 1\text{C} / 1\text{V} \equiv 1\text{Farad}$$

- 1 Farad is a very large value, and typical values of capacitance are: pF, nF, and μF .

Capacitors II

Capacitors Energy Symbols Circuits

- C is a measure of the capacity to store charge for a given potential difference across two conductors.
- The unit of capacitance is one “Farad”.


$$[C] = \frac{[Q]}{[V]} = 1\text{C} / 1\text{V} \equiv 1\text{Farad}$$

- 1 Farad is a very large value, and typical values of capacitance are: pF, nF, and μF . Note: 1 miliFarad is also large.

Calculating Capacitance

Capacitors Energy Symbols Circuits

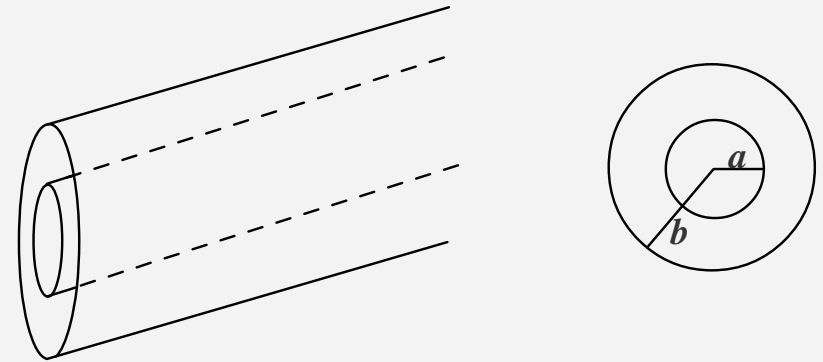
- Calculate the capacitance for a long coaxial cable of length L . Represent the cable as two concentric cylindrical conductors with radii a and b ($b > a$) as shown on the right.



Calculating Capacitance

Capacitors Energy Symbols Circuits

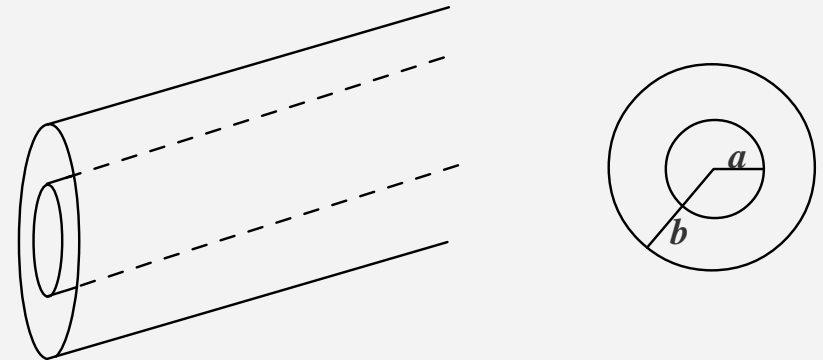- Calculate the capacitance for a long coaxial cable of length L . Represent the cable as two concentric cylindrical conductors with radii a and b ($b > a$) as shown on the right.
- ◆ Let the inner conductor carry a charge $+Q$ uniformly distributed over its length.




Calculating Capacitance

Capacitors Energy Symbols Circuits

- Calculate the capacitance for a long coaxial cable of length L . Represent the cable as two concentric cylindrical conductors with radii a and b ($b > a$) as shown on the right.
- ◆ Let the inner conductor carry a charge $+Q$ uniformly distributed over its length.
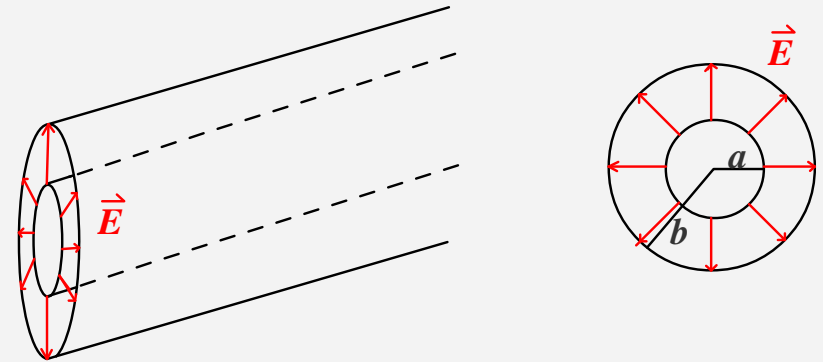
$$\Delta V_{ba} = - \int_b^a \vec{E} \cdot d\vec{l}$$




Calculating Capacitance

Capacitors Energy Symbols Circuits

- Calculate the capacitance for a long coaxial cable of length L . Represent the cable as two concentric cylindrical conductors with radii a and b ($b > a$) as shown on the right.
- ◆ Let the inner conductor carry a charge $+Q$ uniformly distributed over its length.

$$\Delta V_{ba} = - \int_b^a \vec{E} \cdot d\vec{l}$$
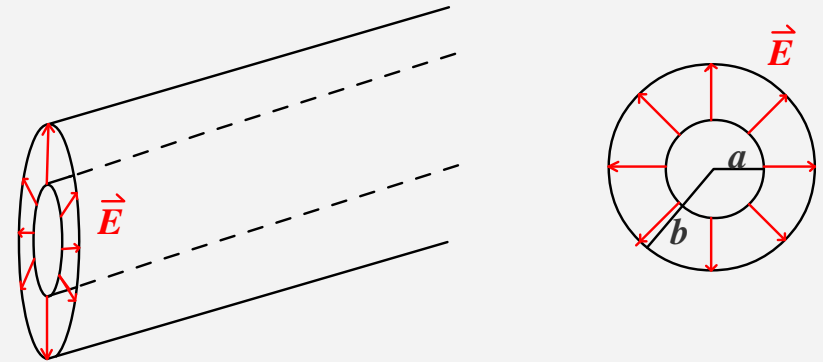
$$\vec{E}(a < r < b) = \frac{\lambda}{2\pi\epsilon_0 r} \hat{r}$$



Calculating Capacitance


Capacitors Energy Symbols Circuits

- Calculate the capacitance for a long coaxial cable of length L . Represent the cable as two concentric cylindrical conductors with radii a and b ($b > a$) as shown on the right.
- ◆ Let the inner conductor carry a charge $+Q$ uniformly distributed over its length.

$$\Delta V_{ba} = - \int_b^a \vec{E} \cdot d\vec{l}$$

$$\vec{E}(a < r < b) = \frac{\lambda}{2\pi\epsilon_0 r} \hat{r}$$

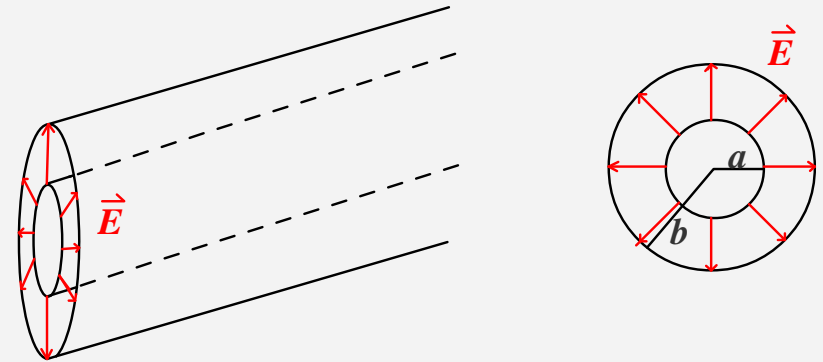
$$\Rightarrow \Delta V_{ba} = \frac{Q}{2\pi\epsilon_0 L} \ln(b/a)$$



Calculating Capacitance

Capacitors Energy Symbols Circuits

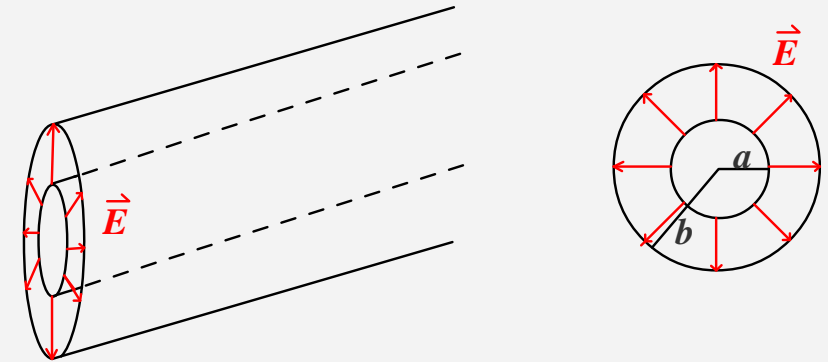- Calculate the capacitance for a long coaxial cable of length L . Represent the cable as two concentric cylindrical conductors with radii a and b ($b > a$) as shown on the right.
- ◆ Let the inner conductor carry a charge $+Q$ uniformly distributed over its length.



$$\Delta V_{ba} = - \int_b^a \vec{E} \cdot d\vec{l}$$


$$\vec{E}(a < r < b) = \frac{\lambda}{2\pi\epsilon_0 r} \hat{r}$$

$$\Rightarrow \Delta V_{ba} = \frac{Q}{2\pi\epsilon_0 L} \ln(b/a) \rightarrow \Delta V_{ba} > 0.$$

Calculating Capacitance

Capacitors Energy Symbols Circuits

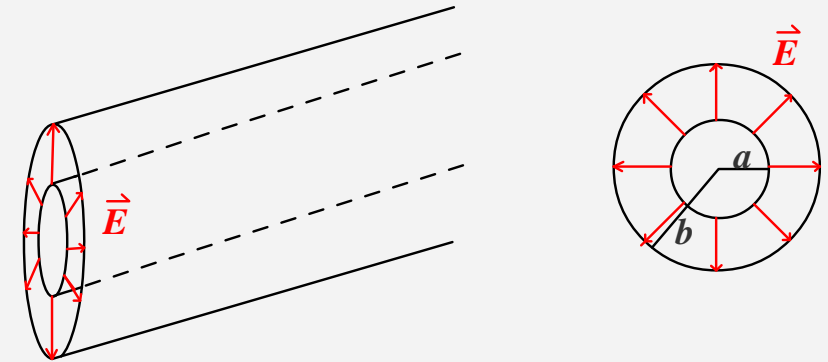- Calculate the capacitance for a long coaxial cable of length L . Represent the cable as two concentric cylindrical conductors with radii a and b ($b > a$) as shown on the right.
- ◆ Let the inner conductor carry a charge $+Q$ uniformly distributed over its length.



$$\Delta V_{ba} = - \int_b^a \vec{E} \cdot d\vec{l}$$


$$\vec{E}(a < r < b) = \frac{\lambda}{2\pi\epsilon_0 r} \hat{r}$$

$$\Rightarrow \Delta V_{ba} = \frac{Q}{2\pi\epsilon_0 L} \ln(b/a) \rightarrow \Delta V_{ba} > 0. \checkmark$$

Calculating Capacitance II

Capacitors Energy Symbols Circuits

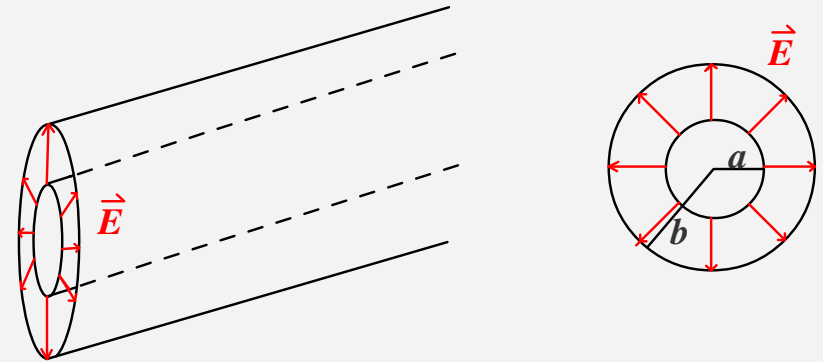
$$\Delta V_{ba} = \frac{Q}{2\pi\epsilon_0 L} \ln(b/a)$$



Calculating Capacitance II

Capacitors Energy Symbols Circuits
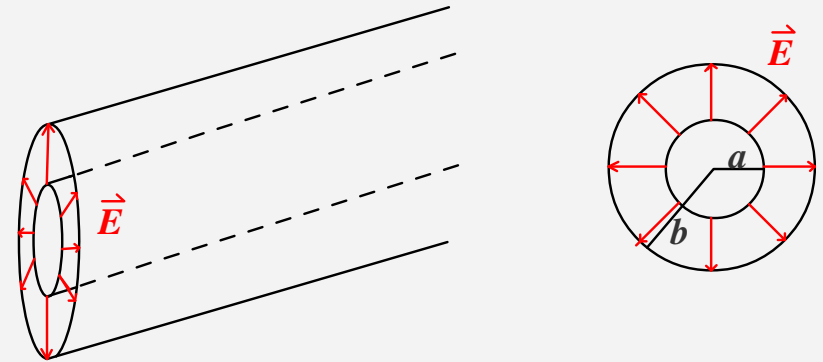
$$\Delta V_{ba} = \frac{Q}{2\pi\epsilon_0 L} \ln(b/a)$$
$$\Rightarrow C = Q/V = \frac{2\pi\epsilon_0 L}{\ln(b/a)}$$




Calculating Capacitance II

Capacitors Energy Symbols Circuits

$$\Delta V_{ba} = \frac{Q}{2\pi\epsilon_0 L} \ln(b/a)$$
$$\Rightarrow C = Q/V = \frac{2\pi\epsilon_0 L}{\ln(b/a)}$$

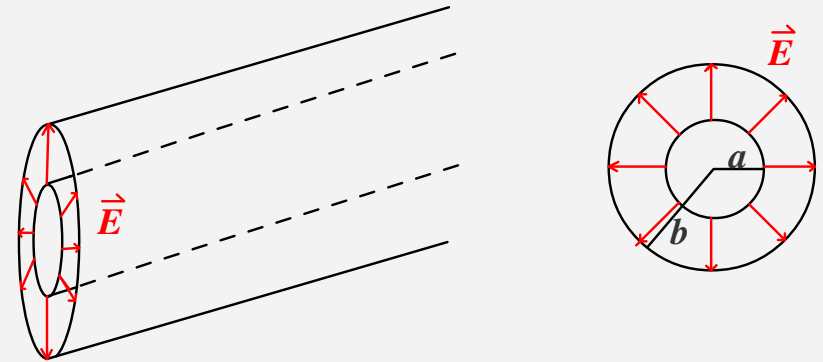- The capacitance of a coaxial cable varies as the length of the cable varies.




Calculating Capacitance II

Capacitors Energy Symbols Circuits

$$\Delta V_{ba} = \frac{Q}{2\pi\epsilon_0 L} \ln(b/a)$$
$$\Rightarrow C = Q/V = \frac{2\pi\epsilon_0 L}{\ln(b/a)}$$

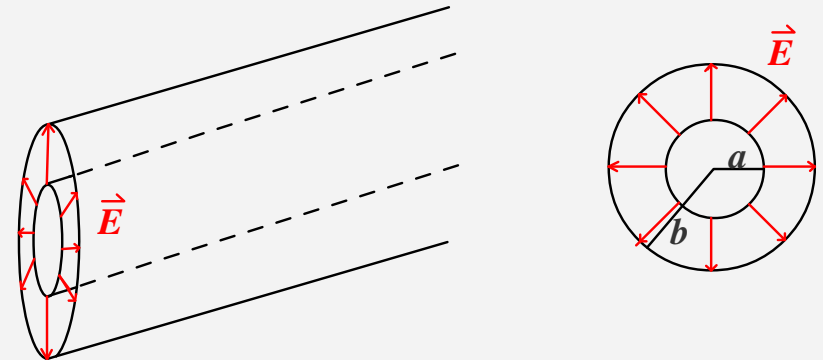- The capacitance of a coaxial cable varies as the length of the cable varies. **This is a very important result for many experiments.**




Calculating Capacitance II

Capacitors Energy Symbols Circuits

$$\Delta V_{ba} = \frac{Q}{2\pi\epsilon_0 L} \ln(b/a)$$
$$\Rightarrow C = Q/V = \frac{2\pi\epsilon_0 L}{\ln(b/a)}$$

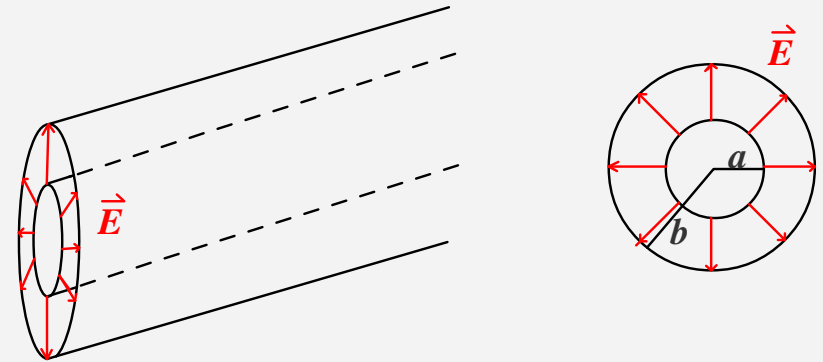- The capacitance of a coaxial cable varies as the length of the cable varies. **This is a very important result for many experiments.**
- It is convenient to talk about the capacitance per unit length for a coaxial cable.




Calculating Capacitance II

Capacitors Energy Symbols Circuits

$$\Delta V_{ba} = \frac{Q}{2\pi\epsilon_0 L} \ln(b/a)$$
$$\Rightarrow C = Q/V = \frac{2\pi\epsilon_0 L}{\ln(b/a)}$$

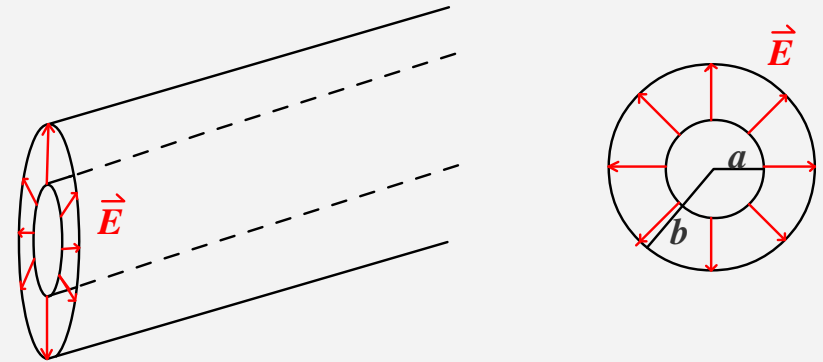- The capacitance of a coaxial cable varies as the length of the cable varies. **This is a very important result for many experiments.**
- It is convenient to talk about the capacitance per unit length for a coaxial cable.



$$C/L = \frac{2\pi\epsilon_0}{\ln(b/a)}$$

Capacitance and Energy

Capacitors Energy Symbols Circuits

- We can rewrite the energy required to charge a conductor to final charge Q in terms of capacitance and potential difference between the two surfaces of a capacitor.

Capacitance and Energy

Capacitors Energy Symbols Circuits

- We can rewrite the energy required to charge a conductor to final charge Q in terms of capacitance and potential difference between the two surfaces of a capacitor.

$$U = \int dU = \int_0^Q V dq$$

Capacitance and Energy

Capacitors Energy Symbols Circuits

- We can rewrite the energy required to charge a conductor to final charge Q in terms of capacitance and potential difference between the two surfaces of a capacitor.

$$U = \int dU = \int_0^Q V dq = \int_0^Q q/C dq$$

Capacitance and Energy

Capacitors Energy Symbols Circuits

- We can rewrite the energy required to charge a conductor to final charge Q in terms of capacitance and potential difference between the two surfaces of a capacitor.

$$U = \int dU = \int_0^Q V dq = \int_0^Q q/C dq \quad (\text{where } V = q/C.)$$

Capacitance and Energy

Capacitors Energy Symbols Circuits

- We can rewrite the energy required to charge a conductor to final charge Q in terms of capacitance and potential difference between the two surfaces of a capacitor.

$$U = \int dU = \int_0^Q V dq = \int_0^Q q/C dq \quad (\text{where } V = q/C.)$$

$$U = \frac{Q^2}{2C}$$

Capacitance and Energy

Capacitors Energy Symbols Circuits

- We can rewrite the energy required to charge a conductor to final charge Q in terms of capacitance and potential difference between the two surfaces of a capacitor.

$$U = \int dU = \int_0^Q V dq = \int_0^Q q/C dq \quad (\text{where } V = q/C.)$$

$$U = \frac{Q^2}{2C} = \frac{QV}{2}$$

Capacitance and Energy

Capacitors Energy Symbols Circuits

- We can rewrite the energy required to charge a conductor to final charge Q in terms of capacitance and potential difference between the two surfaces of a capacitor.

$$U = \int dU = \int_0^Q V dq = \int_0^Q q/C dq \quad (\text{where } V = q/C.)$$

$$U = \frac{Q^2}{2C} = \frac{QV}{2} = \frac{CV^2}{2}$$

Capacitance and Energy

Capacitors Energy Symbols Circuits

- We can rewrite the energy required to charge a conductor to final charge Q in terms of capacitance and potential difference between the two surfaces of a capacitor.

$$U = \int dU = \int_0^Q V dq = \int_0^Q q/C dq \quad (\text{where } V = q/C.)$$

$$U = \frac{Q^2}{2C} = \frac{QV}{2} = \frac{CV^2}{2}$$

- The three equations above are equivalent since $C \equiv Q/V$.



Circuit Symbols



Capacitors Energy Symbols Circuits

- Typically, one uses a combination of capacitors in an electric circuit (to store electric energy).



Circuit Symbols

Capacitors Energy Symbols Circuits




- Typically, one uses a combination of capacitors in an electric circuit (to store electric energy).
- We need to define symbols which will represent capacitors and batteries (very common in everyday electric circuits).

Circuit Symbols

Capacitors Energy Symbols Circuits


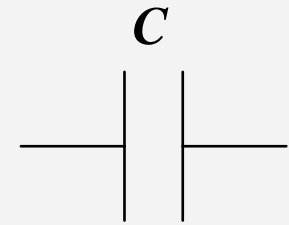
- Typically, one uses a combination of capacitors in an electric circuit (to store electric energy).
- We need to define symbols which will represent capacitors and batteries (very common in everyday electric circuits).
- The figure on the right (two parallel lines of equal length) will be used to represent a capacitor.



Circuit Symbols

Capacitors Energy Symbols Circuits



- Typically, one uses a combination of capacitors in an electric circuit (to store electric energy).
- We need to define symbols which will represent capacitors and batteries (very common in everyday electric circuits).
- The figure on the right (two parallel lines of equal length) will be used to represent a capacitor.
- The next figure on the right will be used to represent a battery (Notice the long and short sides).

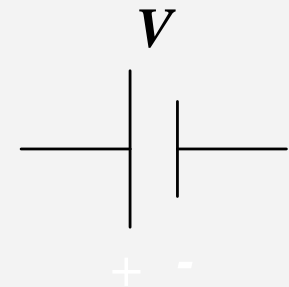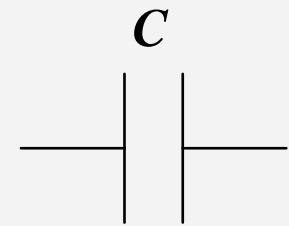

Circuit Symbols

Capacitors Energy Symbols Circuits



- Typically, one uses a combination of capacitors in an electric circuit (to store electric energy).
- We need to define symbols which will represent capacitors and batteries (very common in everyday electric circuits).
- The figure on the right (two parallel lines of equal length) will be used to represent a capacitor.
- The next figure on the right will be used to represent a battery (Notice the long and short sides).
 - ◆ The long side of the battery represents the side of a battery which is at a higher potential (i.e., +).

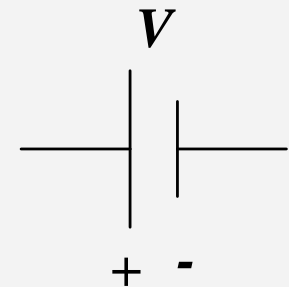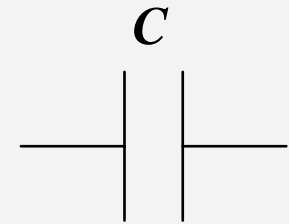

Circuit Symbols

Capacitors Energy Symbols Circuits

- Typically, one uses a combination of capacitors in an electric circuit (to store electric energy).
- We need to define symbols which will represent capacitors and batteries (very common in everyday electric circuits).
- The figure on the right (two parallel lines of equal length) will be used to represent a capacitor.
- The next figure on the right will be used to represent a battery (Notice the long and short sides).
 - ◆ The long side of the battery represents the side of a battery which is at a higher potential (i.e., +).
 - ◆ The short side of the battery represents the end of the battery which is lower in potential (i.e., -).

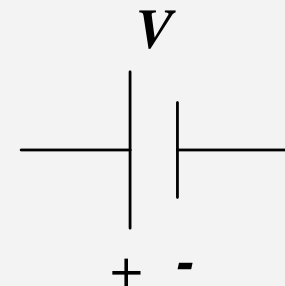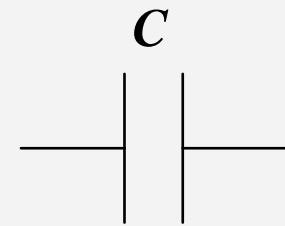



Circuits



Capacitors Energy Symbols Circuits

- We begin circuits with a circuit diagram (a map of how we want to connect our components).



Circuits



Capacitors Energy Symbols Circuits

- We begin circuits with a circuit diagram (a map of how we want to connect our components).
- Assumptions:
 - ◆ The components in our circuit will be connected by perfectly conducting wires.



Circuits



Capacitors Energy Symbols Circuits

- We begin circuits with a circuit diagram (a map of how we want to connect our components).
- Assumptions:
 - ◆ The components in our circuit will be connected by perfectly conducting wires.
 - ◆ The battery is an ideal battery unless otherwise stated.



Circuits



Capacitors Energy Symbols Circuits

- We begin circuits with a circuit diagram (a map of how we want to connect our components).
- Assumptions:
 - ◆ The components in our circuit will be connected by perfectly conducting wires.
 - ◆ The battery is an ideal battery unless otherwise stated.
 - The purpose of a battery is to maintain constant potential difference between the two ends of the battery at all costs.



Circuits




Capacitors Energy Symbols Circuits

- We begin circuits with a circuit diagram (a map of how we want to connect our components).
- Assumptions:
 - ◆ The components in our circuit will be connected by perfectly conducting wires.
 - ◆ The battery is an ideal battery unless otherwise stated.
 - The purpose of a battery is to maintain constant potential difference between the two ends of the battery at all costs.
- Let's begin.

Capacitors in Parallel

Capacitors Energy Symbols Circuits

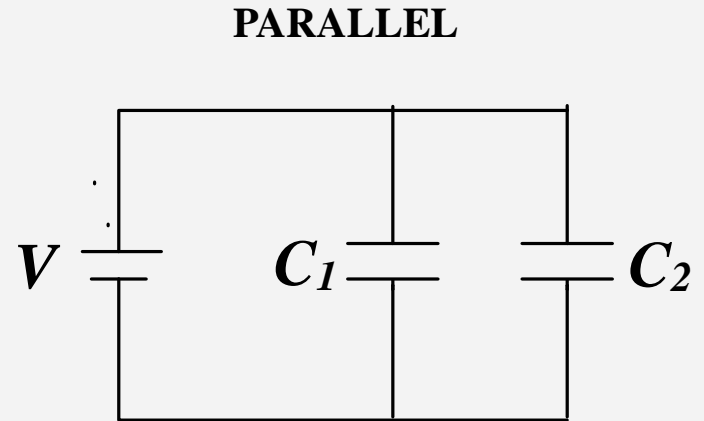
- When placing two or more components as shown in the figure on the right, we term the assembly a *PARALLEL* circuit.



Capacitors in Parallel

Capacitors Energy Symbols Circuits

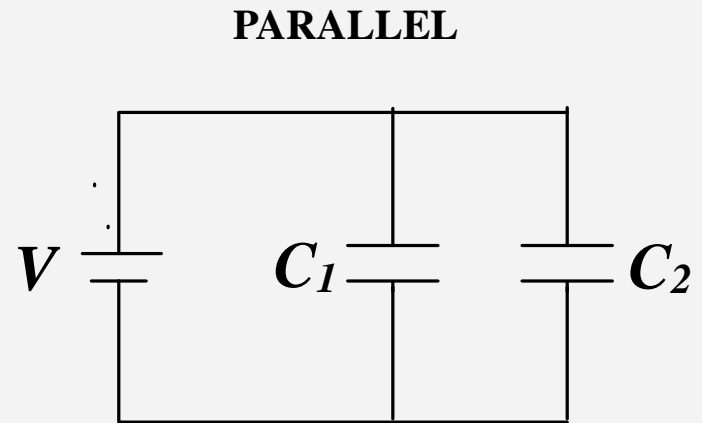
- When placing two or more components as shown in the figure on the right, we term the assembly a *PARALLEL* circuit.
- The top of the capacitors are connected to the top of the battery.



Capacitors in Parallel

Capacitors Energy Symbols Circuits

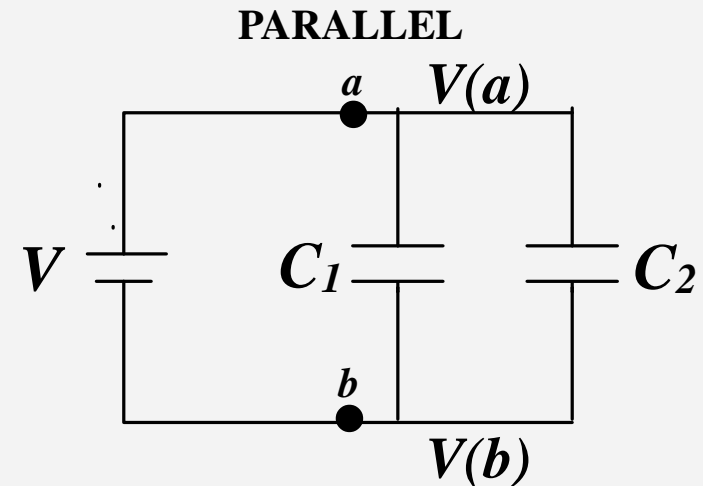
- When placing two or more components as shown in the figure on the right, we term the assembly a *PARALLEL* circuit.
- The top of the capacitors are connected to the top of the battery.
- The bottom of the capacitors are connected to the bottom of the battery.



Capacitors in Parallel

Capacitors Energy Symbols Circuits

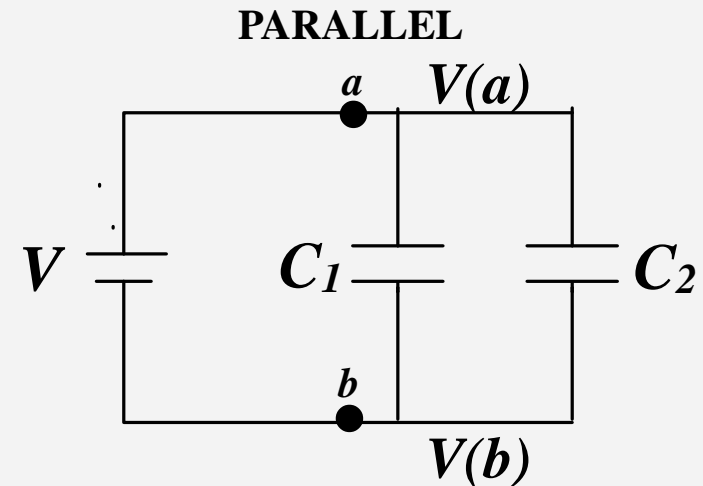
- When placing two or more components as shown in the figure on the right, we term the assembly a *PARALLEL* circuit.
- The top of the capacitors are connected to the top of the battery.
- The bottom of the capacitors are connected to the bottom of the battery.
- The difference in potential between the top and bottom of the battery is V .



Capacitors in Parallel

Capacitors Energy Symbols Circuits


- When placing two or more components as shown in the figure on the right, we term the assembly a *PARALLEL* circuit.
- The top of the capacitors are connected to the top of the battery.
- The bottom of the capacitors are connected to the bottom of the battery.
- The difference in potential between the top and bottom of the battery is V .
- This means that the potential difference across C_1 and C_2 is the same and is given by the V .

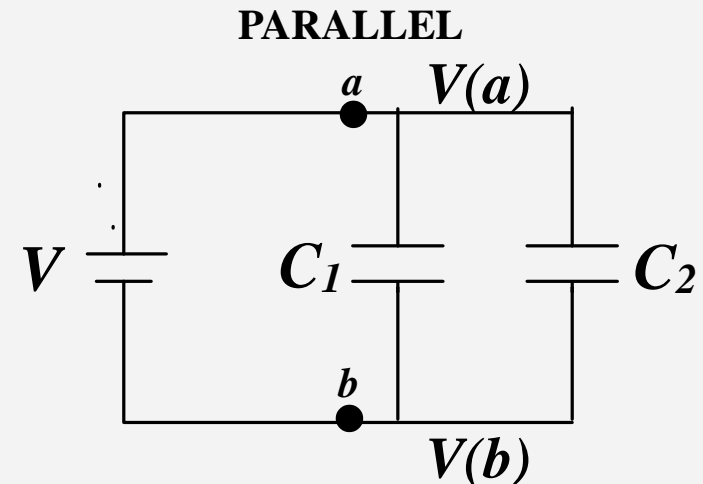

Capacitors in Parallel II

Capacitors Energy Symbols Circuits

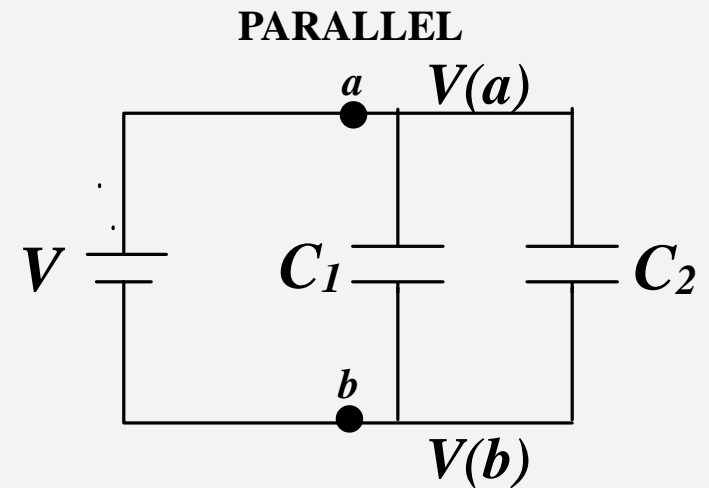- This means that the potential difference across C_1 and C_2 is the same and is given by the V .




Capacitors in Parallel II

Capacitors Energy Symbols Circuits

- This means that the potential difference across C_1 and C_2 is the same and is given by the V .

$$\Delta V_{ba} = V(a) - V(b)$$

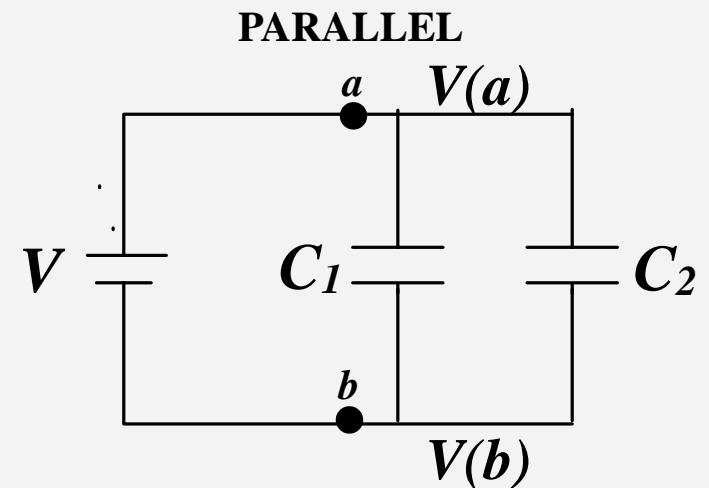


Capacitors in Parallel II

Capacitors Energy Symbols Circuits

- This means that the potential difference across C_1 and C_2 is the same and is given by the V .
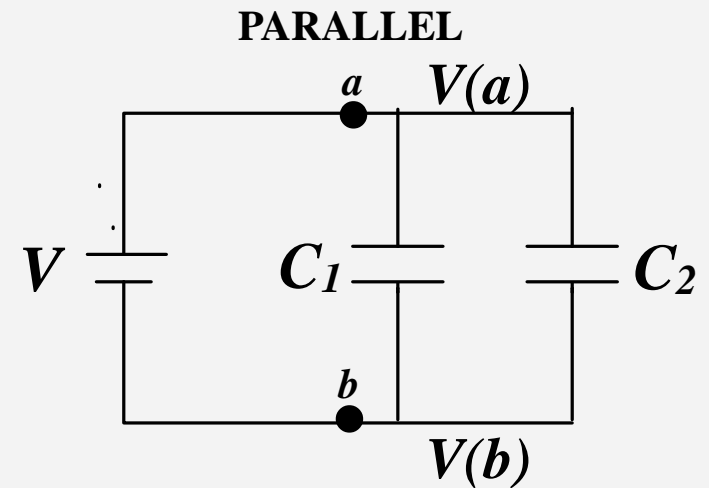
$$\Delta V_{ba} = V(a) - V(b) = V \quad (\text{The potential difference of the battery})$$




Capacitors in Parallel II

Capacitors Energy Symbols Circuits

- This means that the potential difference across C_1 and C_2 is the same and is given by the V .
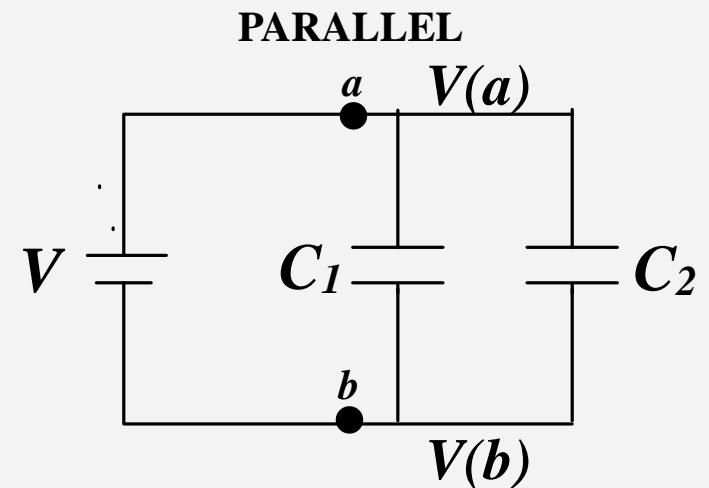
$$\Delta V_{ba} = V(a) - V(b) = V \quad (\text{The potential difference of the battery})$$
$$\Rightarrow Q_1 = C_1 V$$




Capacitors in Parallel II

Capacitors Energy Symbols Circuits

- This means that the potential difference across C_1 and C_2 is the same and is given by the V .
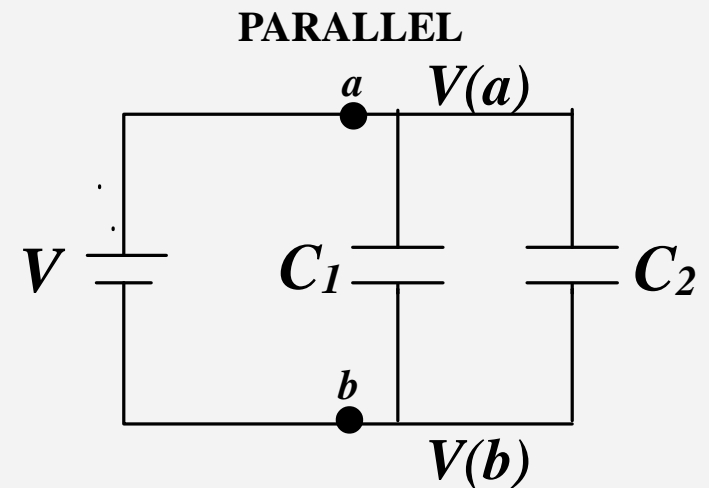
$$\Delta V_{ba} = V(a) - V(b) = V \quad (\text{The potential difference of the battery})$$
$$\Rightarrow Q_1 = C_1 V \quad \& \quad Q_2 = C_2 V$$




Capacitors in Parallel II

Capacitors Energy Symbols Circuits

- This means that the potential difference across C_1 and C_2 is the same and is given by the V .

$$\Delta V_{ba} = V(a) - V(b) = V \quad (\text{The potential difference of the battery})$$
$$\Rightarrow Q_1 = C_1 V \quad \& \quad Q_2 = C_2 V$$

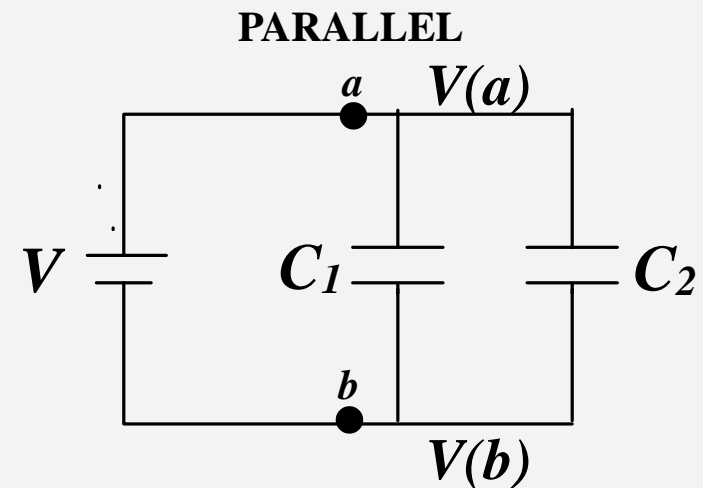- The total charge over the two capacitors must be the charge supplied by the battery!



Capacitors in Parallel II


Capacitors Energy Symbols Circuits

- This means that the potential difference across C_1 and C_2 is the same and is given by the V .

$$\Delta V_{ba} = V(a) - V(b) = V \quad (\text{The potential difference of the battery})$$
$$\Rightarrow Q_1 = C_1 V \quad \& \quad Q_2 = C_2 V$$

- The total charge over the two capacitors must be the charge supplied by the battery!

$$Q_T = Q_1 + Q_2$$

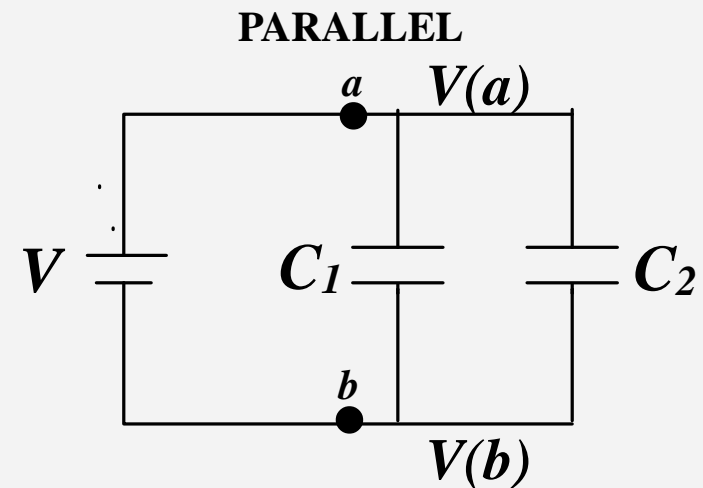

Capacitors in Parallel II


Capacitors Energy Symbols Circuits

- This means that the potential difference across C_1 and C_2 is the same and is given by the V .

$$\Delta V_{ba} = V(a) - V(b) = V \quad (\text{The potential difference of the battery})$$
$$\Rightarrow Q_1 = C_1 V \quad \& \quad Q_2 = C_2 V$$

- The total charge over the two capacitors must be the charge supplied by the battery!
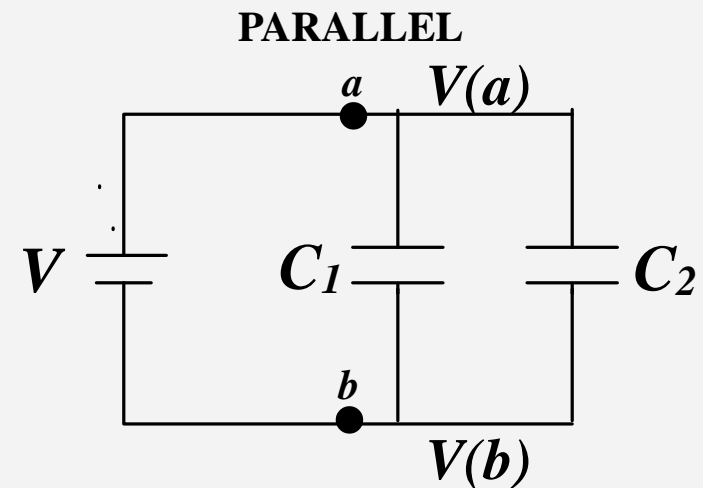
$$Q_T = Q_1 + Q_2$$
$$C_T V_T = C_1 V_1 + C_2 V_2$$



Capacitors in Parallel II


Capacitors Energy Symbols Circuits

- This means that the potential difference across C_1 and C_2 is the same and is given by the V .

$$\Delta V_{ba} = V(a) - V(b) = V \quad (\text{The potential difference of the battery})$$
$$\Rightarrow Q_1 = C_1 V \quad \& \quad Q_2 = C_2 V$$

- The total charge over the two capacitors must be the charge supplied by the battery!

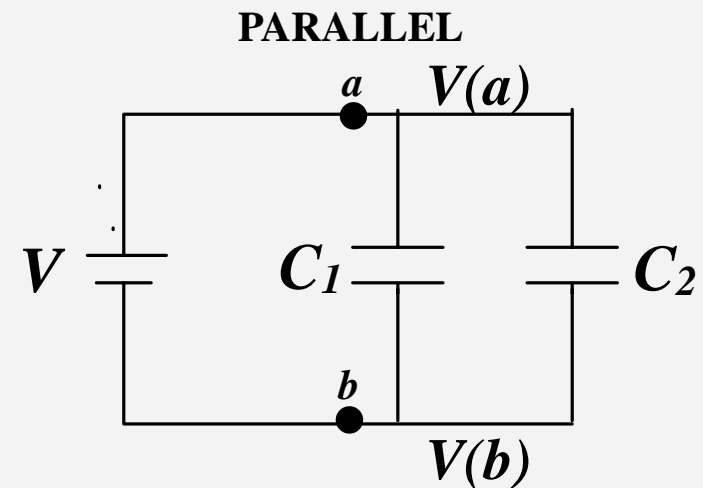
$$Q_T = Q_1 + Q_2$$
$$C_T V_T = C_1 V_1 + C_2 V_2$$
$$C_T V_T = V (C_1 + C_2)$$



Capacitors in Parallel III

Capacitors Energy Symbols Circuits


$$C_T V_T = V (C_1 + C_2)$$

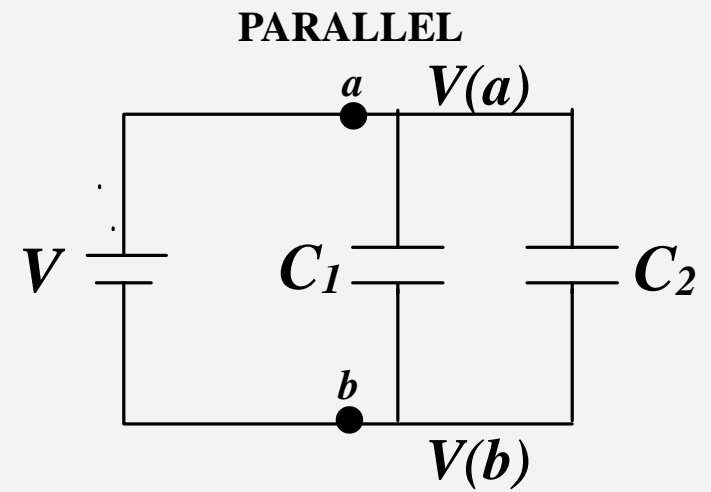

Capacitors in Parallel III

Capacitors Energy Symbols Circuits
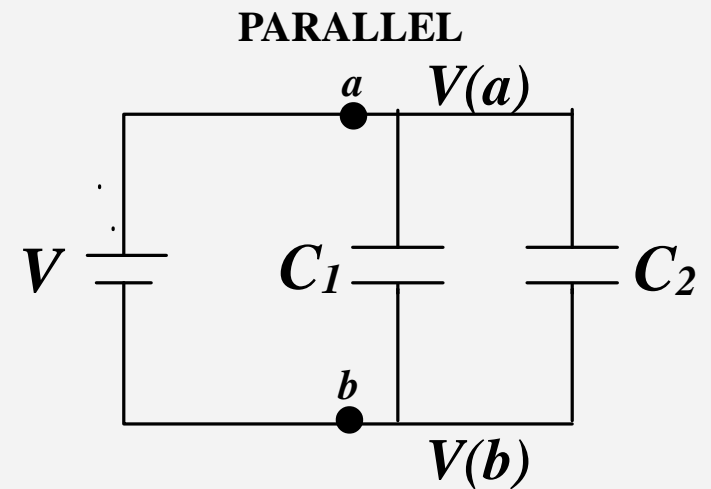
$$C_T V_T = V (C_1 + C_2) \Rightarrow C_T V = V (C_1 + C_2)$$




Capacitors in Parallel III

Capacitors Energy Symbols Circuits

$$C_T V_T = V (C_1 + C_2) \Rightarrow C_T V = V (C_1 + C_2)$$

$$C_T = (C_1 + C_2)$$

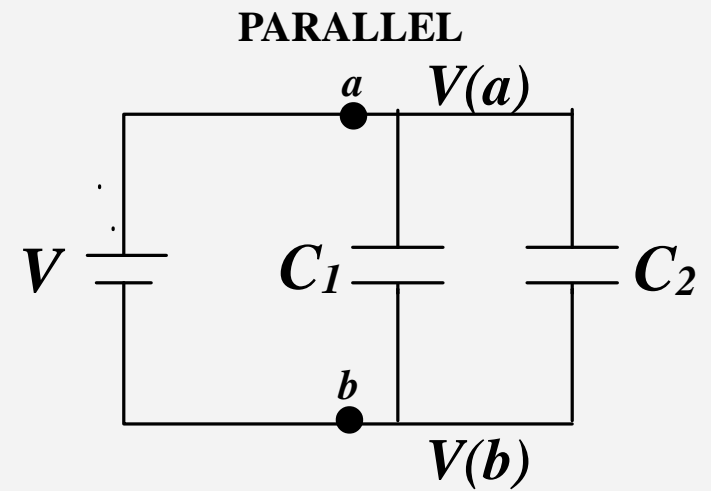


Capacitors in Parallel III

Capacitors Energy Symbols Circuits

$$C_T V_T = V (C_1 + C_2) \Rightarrow C_T V = V (C_1 + C_2)$$

$$C_T = (C_1 + C_2)$$

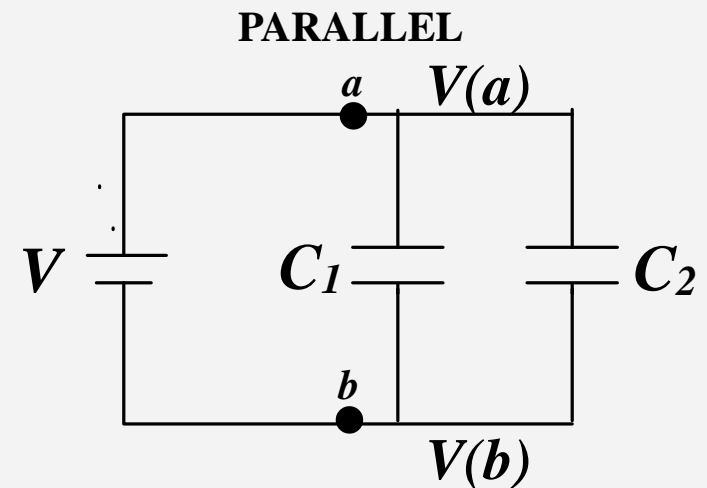- This means that the entire circuit may be represented as a single capacitor ($C_{\text{effective}}$) as shown on the right




Capacitors in Parallel III

Capacitors Energy Symbols Circuits

$$C_T V_T = V (C_1 + C_2) \Rightarrow C_T V = V (C_1 + C_2)$$

$$C_T = (C_1 + C_2)$$

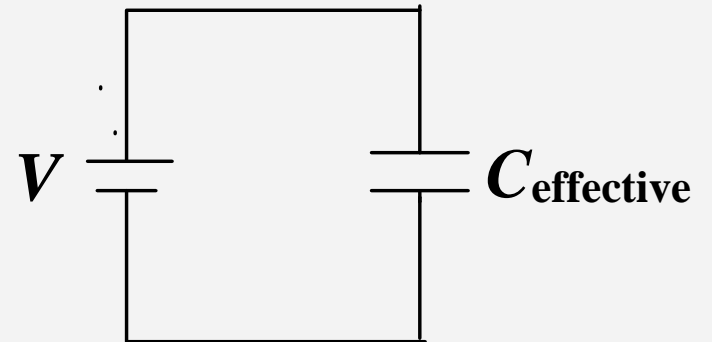- This means that the entire circuit may be represented as a single capacitor ($C_{\text{effective}}$) as shown on the right




Capacitors in Parallel III

Capacitors Energy Symbols Circuits

$$C_T V_T = V (C_1 + C_2) \Rightarrow C_T V = V (C_1 + C_2)$$

$$C_T = (C_1 + C_2)$$

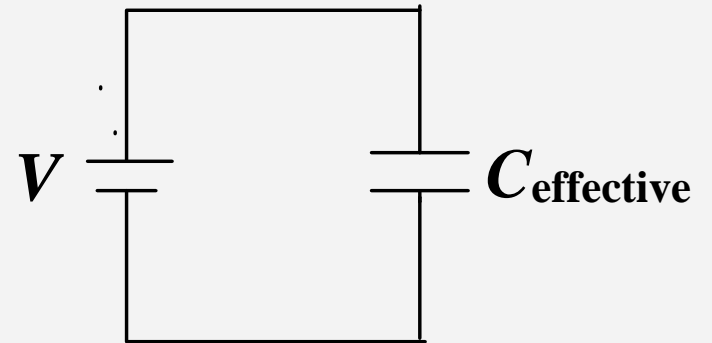- This means that the entire circuit may be represented as a single capacitor ($C_{\text{effective}}$) as shown on the right
- where $C_{\text{effective}} = C_1 + C_2$.




Capacitors in Parallel III

Capacitors Energy Symbols Circuits

$$C_T V_T = V (C_1 + C_2) \Rightarrow C_T V = V (C_1 + C_2)$$

$$C_T = (C_1 + C_2)$$

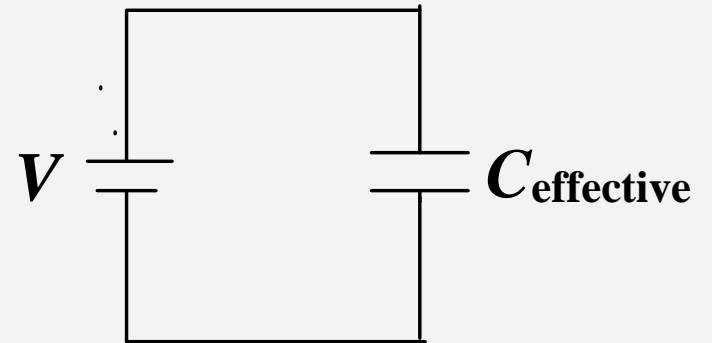- This means that the entire circuit may be represented as a single capacitor ($C_{\text{effective}}$) as shown on the right
- where $C_{\text{effective}} = C_1 + C_2$.
- If we generalize for capacitors connected in parallel:



Capacitors in Parallel III


Capacitors Energy Symbols Circuits

$$C_T V_T = V (C_1 + C_2) \Rightarrow C_T V = V (C_1 + C_2)$$

$$C_T = (C_1 + C_2)$$

- This means that the entire circuit may be represented as a single capacitor ($C_{\text{effective}}$) as shown on the right
- where $C_{\text{effective}} = C_1 + C_2$.
- If we generalize for capacitors connected in parallel:

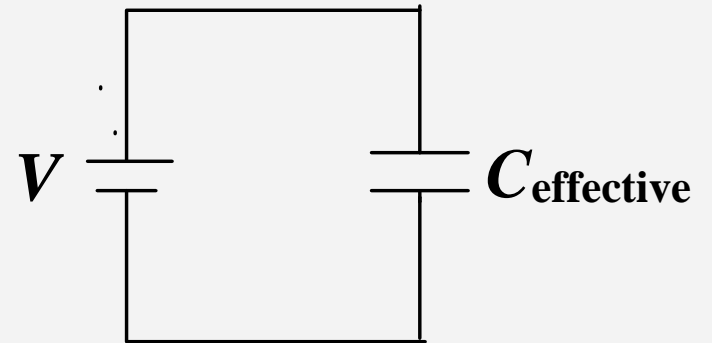
$$C_{\text{effective}} = C_1 + C_2 + C_3 + \dots$$



Capacitors in Series

Capacitors Energy Symbols Circuits

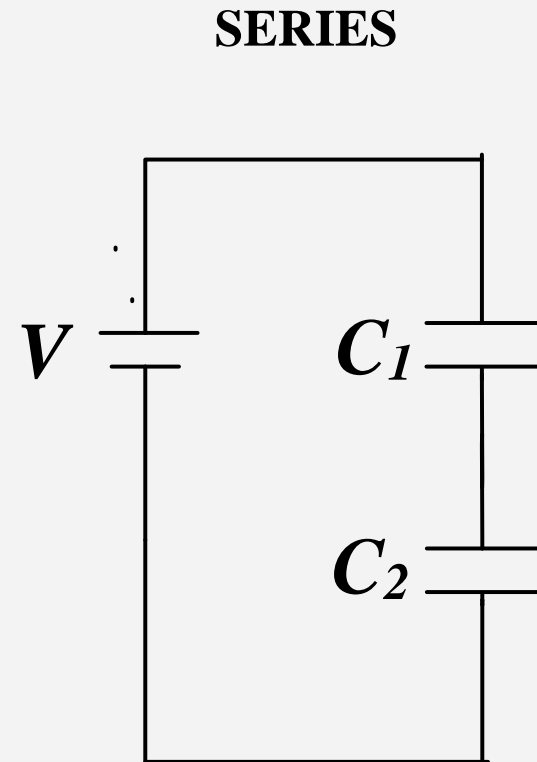
- When placing two or more components as shown in the figure on the right, we term the assembly a *SERIES* circuit.



Capacitors in Series

Capacitors Energy Symbols Circuits

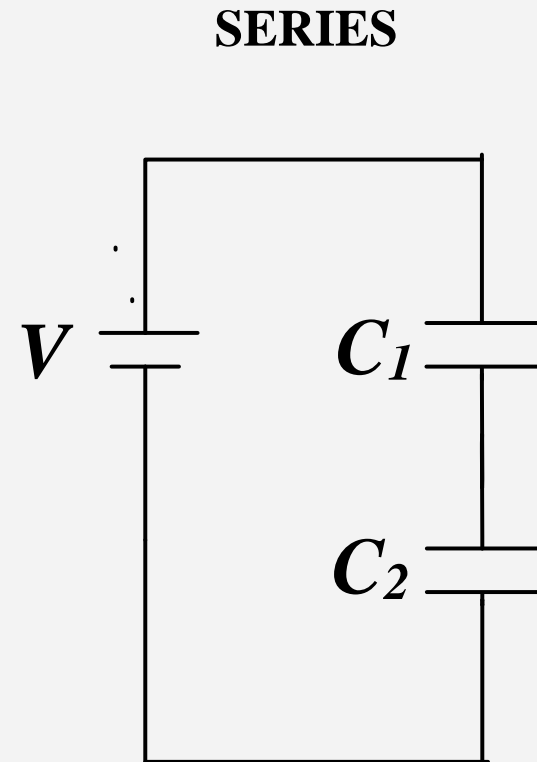
- When placing two or more components as shown in the figure on the right, we term the assembly a *SERIES* circuit.
- The capacitors are connected “back-to-back”.



Capacitors in Series

Capacitors Energy Symbols Circuits

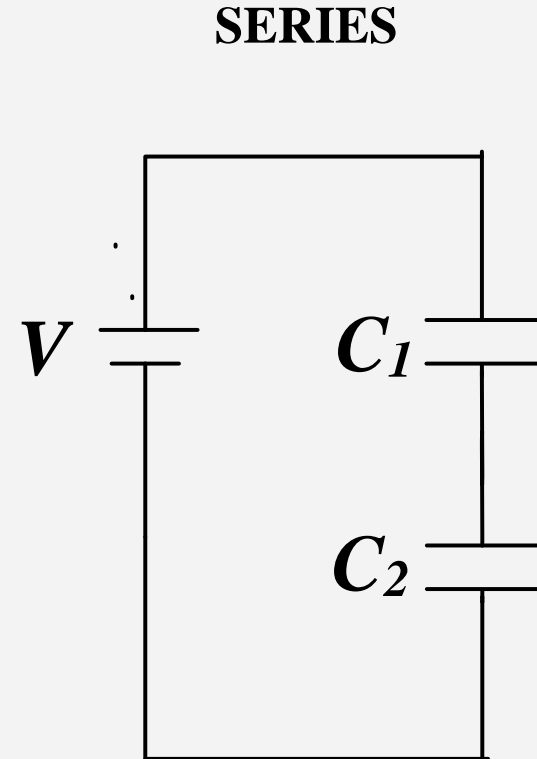
- When placing two or more components as shown in the figure on the right, we term the assembly a *SERIES* circuit.
- The capacitors are connected “back-to-back”.
- The bottom of one plate is connected *by the same wire* to the top of the other plate.



Capacitors in Series

Capacitors Energy Symbols Circuits

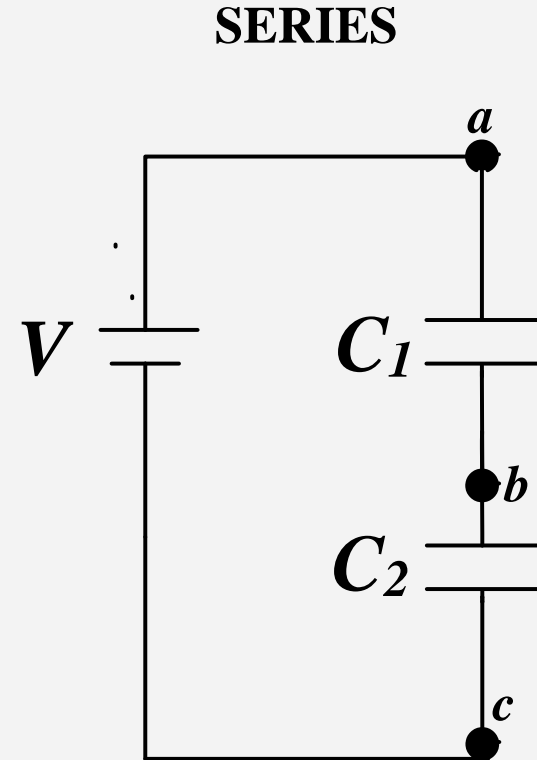
- When placing two or more components as shown in the figure on the right, we term the assembly a *SERIES* circuit.
- The capacitors are connected “back-to-back”.
- The bottom of one plate is connected *by the same wire* to the top of the other plate.
- If we label points along the circuit as in the diagram, we can discuss the potential difference across the points.



Capacitors in Series

Capacitors Energy Symbols Circuits


- When placing two or more components as shown in the figure on the right, we term the assembly a *SERIES* circuit.
- The capacitors are connected “back-to-back”.
- The bottom of one plate is connected *by the same wire* to the top of the other plate.
- If we label points along the circuit as in the diagram, we can discuss the potential difference across the points.
 - ◆ The difference in potential between points c and a is the potential difference, V , of the battery.

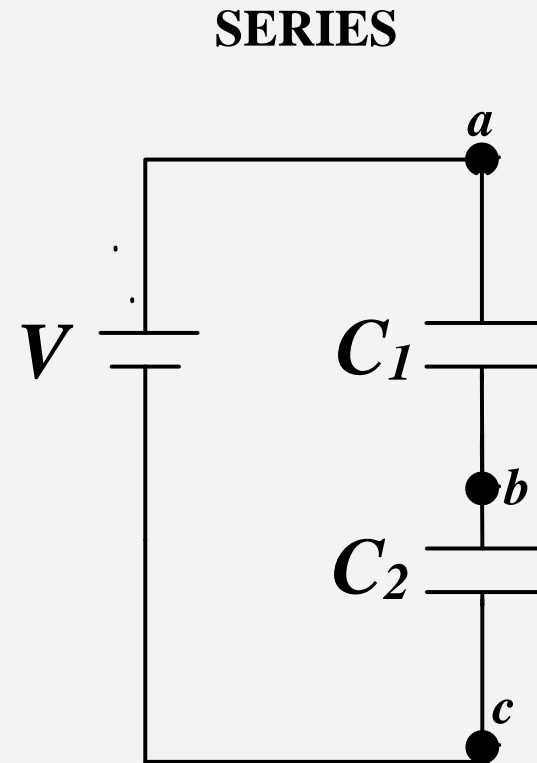

Capacitors in Series

Capacitors Energy Symbols Circuits


- When placing two or more components as shown in the figure on the right, we term the assembly a *SERIES* circuit.
- The capacitors are connected “back-to-back”.
- The bottom of one plate is connected *by the same wire* to the top of the other plate.
- If we label points along the circuit as in the diagram, we can discuss the potential difference across the points.
 - ◆ The difference in potential between points c and a is the potential difference, V , of the battery.

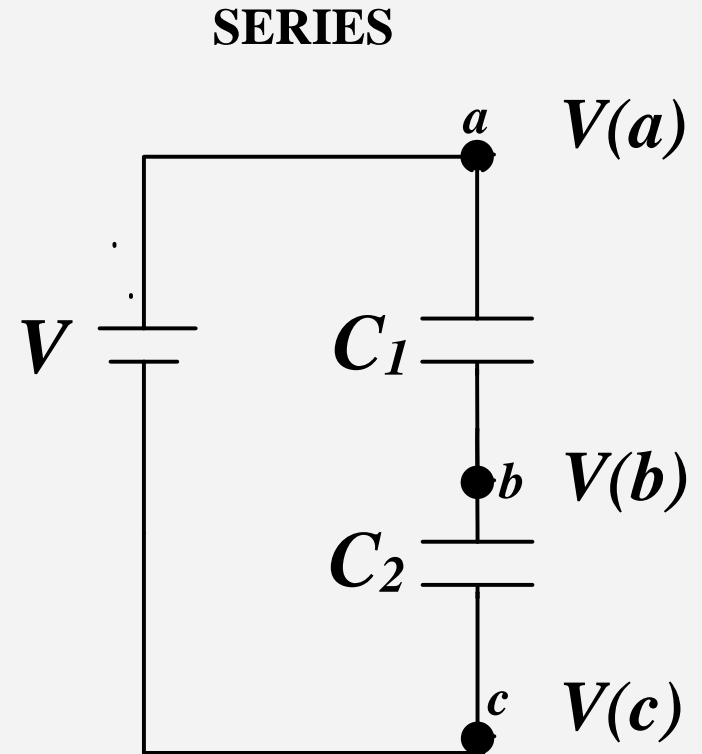

Capacitors in Series II

Capacitors Energy Symbols Circuits

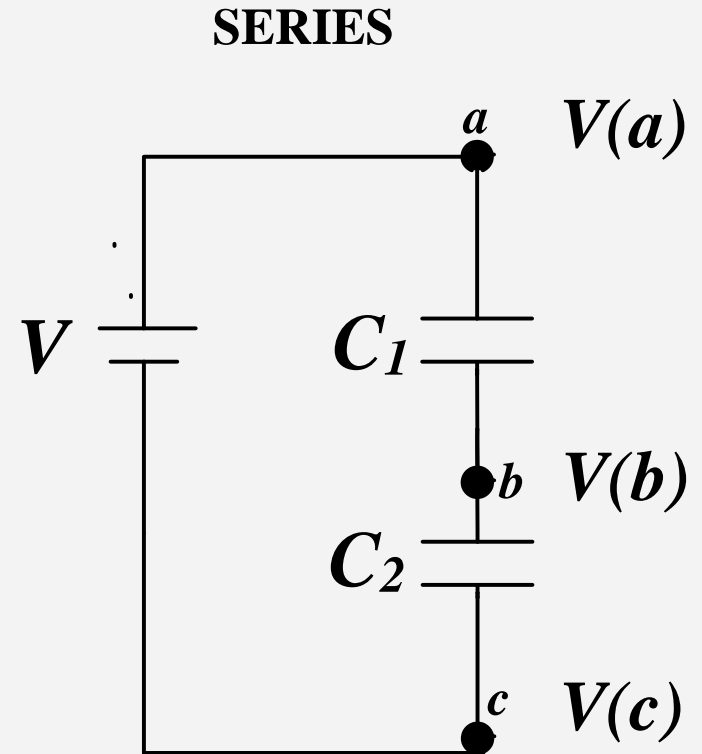- The difference in potential between points c and a is the potential difference, V , of the battery.




Capacitors in Series II

Capacitors Energy Symbols Circuits

- The difference in potential between points c and a is the potential difference, V , of the battery.

$$\Delta V_{ca}$$

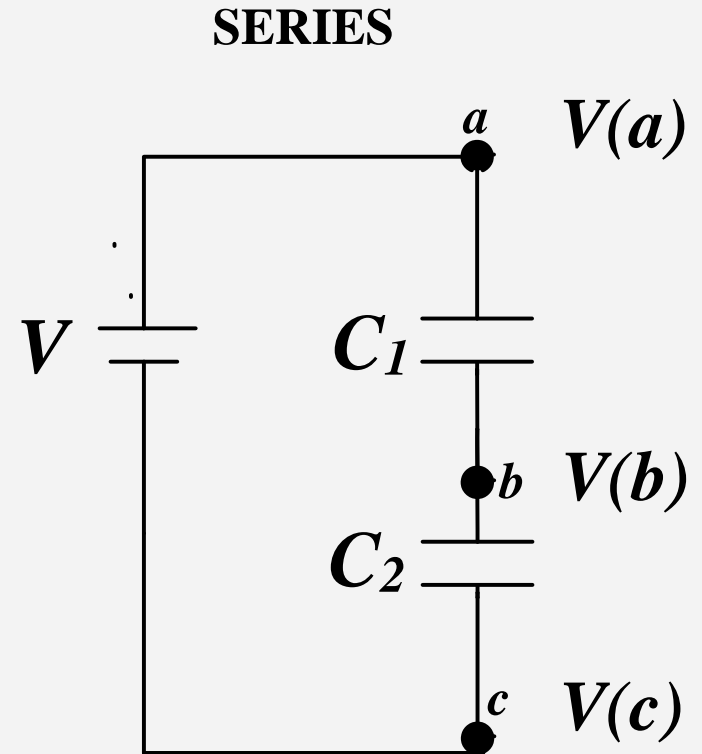


Capacitors in Series II

Capacitors Energy Symbols Circuits

- The difference in potential between points c and a is the potential difference, V , of the battery.

$$\Delta V_{ca} = V(a) - V(c) = V$$

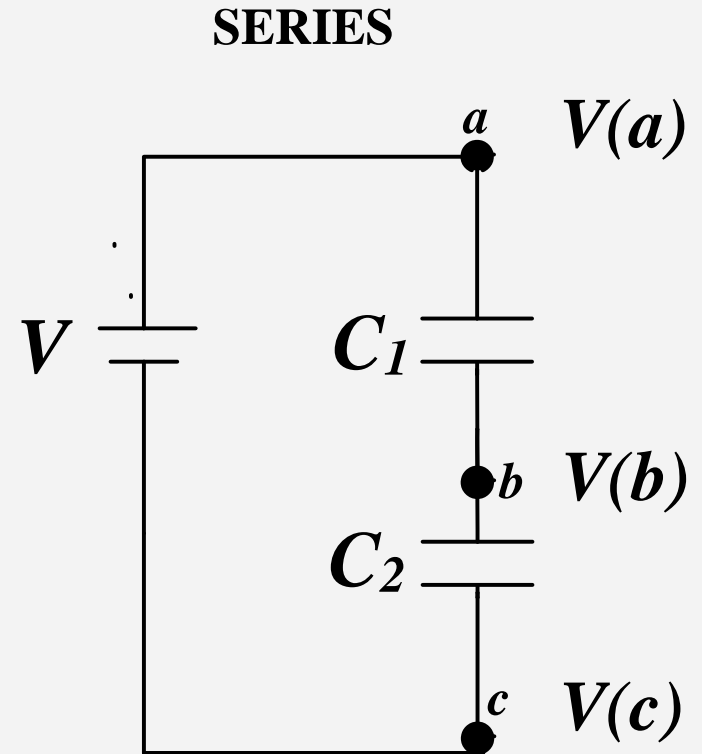


Capacitors in Series II

Capacitors Energy Symbols Circuits

- The difference in potential between points c and a is the potential difference, V , of the battery.

$$\Delta V_{ca} = V(a) - V(c) = V$$

$$\Delta V_{ba}$$

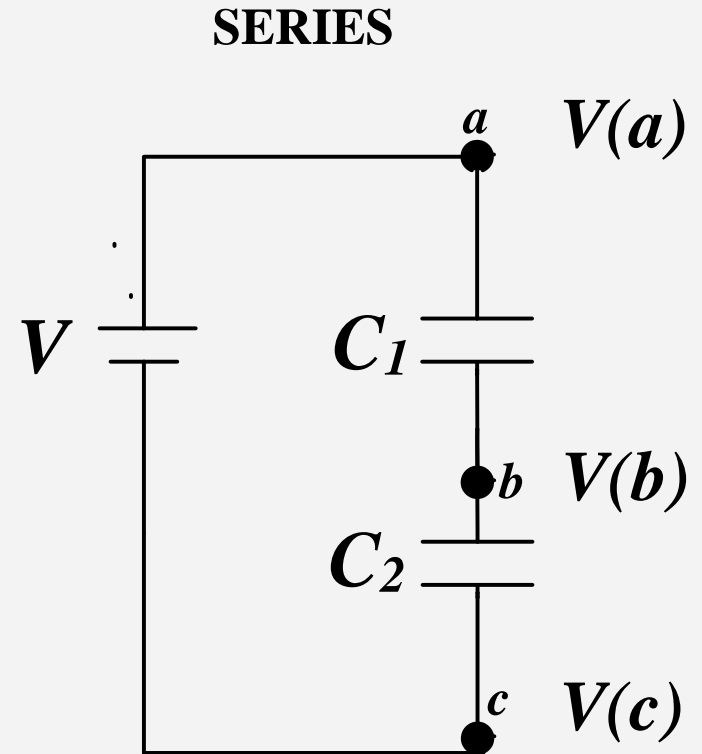


Capacitors in Series II

Capacitors Energy Symbols Circuits

- The difference in potential between points c and a is the potential difference, V , of the battery.

$$\Delta V_{ca} = V(a) - V(c) = V$$

$$\Delta V_{ba} = V(a) - V(b)$$

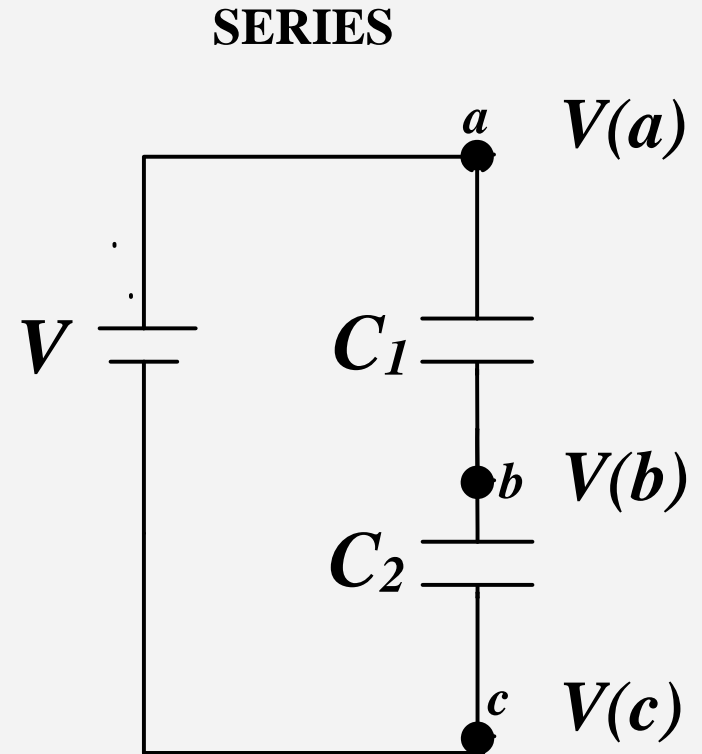

Capacitors in Series II


Capacitors Energy Symbols Circuits

- The difference in potential between points c and a is the potential difference, V , of the battery.

$$\Delta V_{ca} = V(a) - V(c) = V$$

$$\Delta V_{ba} = V(a) - V(b)$$

$$\Delta V_{cb}$$

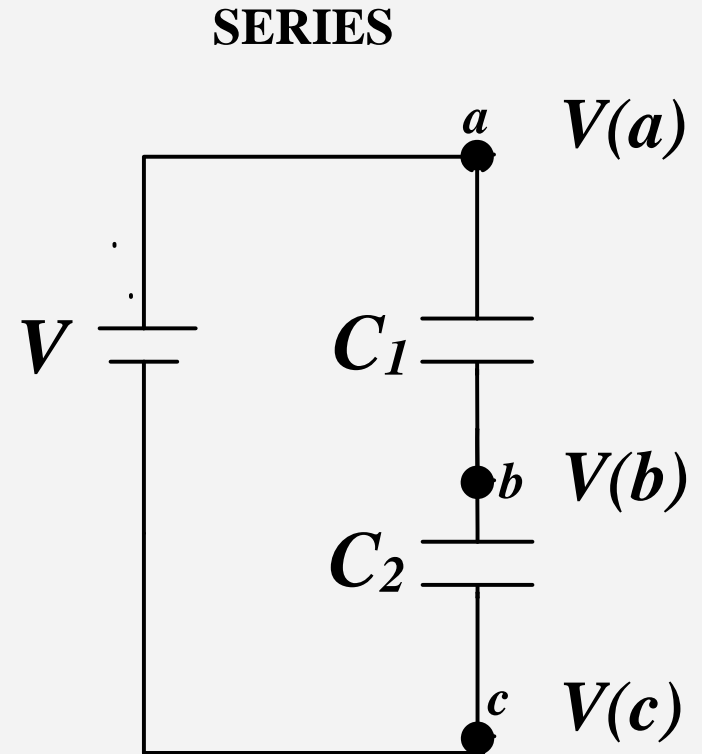

Capacitors in Series II


Capacitors Energy Symbols Circuits

- The difference in potential between points c and a is the potential difference, V , of the battery.

$$\Delta V_{ca} = V(a) - V(c) = V$$

$$\Delta V_{ba} = V(a) - V(b)$$

$$\Delta V_{cb} = V(b) - V(c)$$

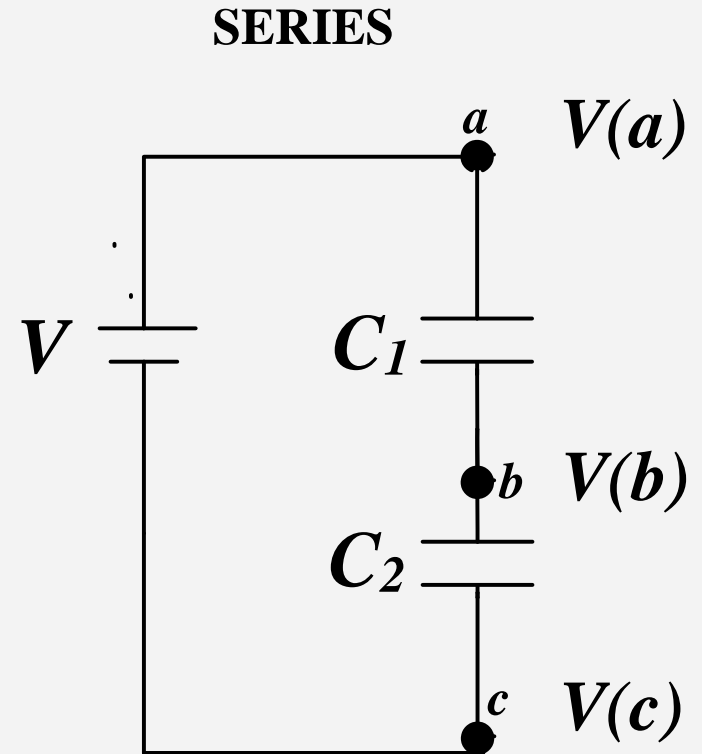

Capacitors in Series II

Capacitors Energy Symbols Circuits


- The difference in potential between points c and a is the potential difference, V , of the battery.

$$\Delta V_{ca} = V(a) - V(c) = V$$

$$\Delta V_{ba} = V(a) - V(b)$$

$$\Delta V_{cb} = V(b) - V(c)$$

$$\Delta V_{ca}$$

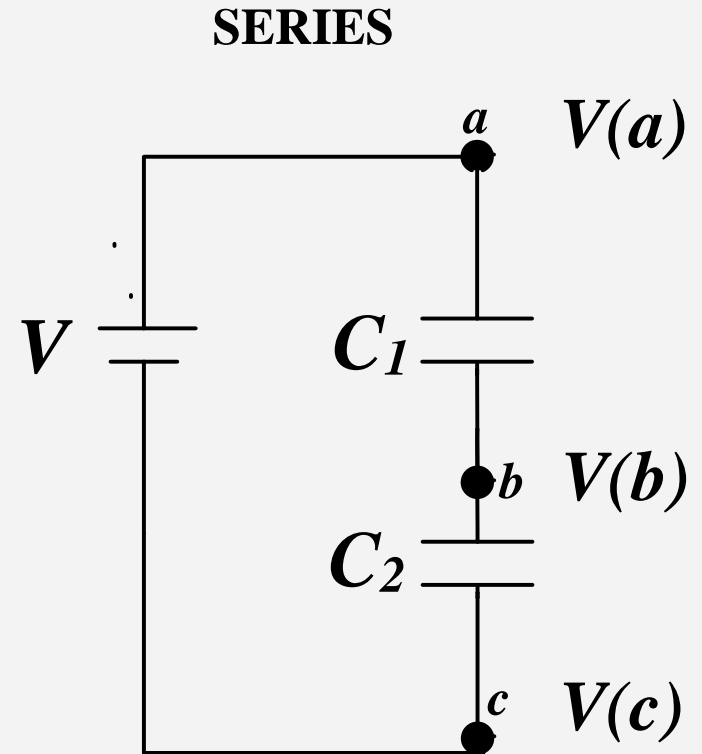

Capacitors in Series II

Capacitors Energy Symbols Circuits


- The difference in potential between points c and a is the potential difference, V , of the battery.

$$\Delta V_{ca} = V(a) - V(c) = V$$

$$\Delta V_{ba} = V(a) - V(b)$$

$$\Delta V_{cb} = V(b) - V(c)$$
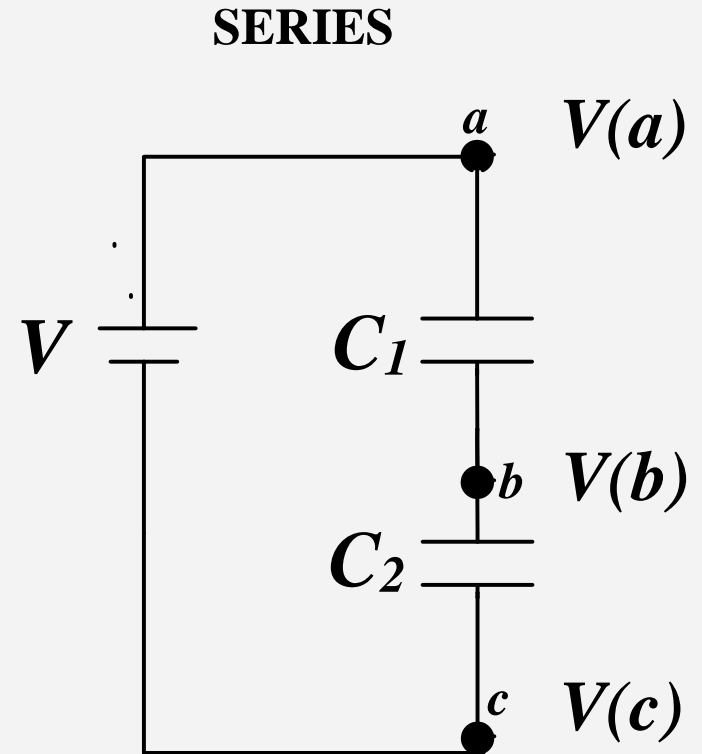
$$\Delta V_{ca} = \Delta V_{ba} + \Delta V_{cb}$$



Capacitors in Series II

Capacitors Energy Symbols Circuits

- The difference in potential between points c and a is the potential difference, V , of the battery.


$$\Delta V_{ca} = V(a) - V(c) = V$$

$$\Delta V_{ba} = V(a) - V(b)$$

$$\Delta V_{cb} = V(b) - V(c)$$

$$\Delta V_{ca} = \Delta V_{ba} + \Delta V_{cb}$$

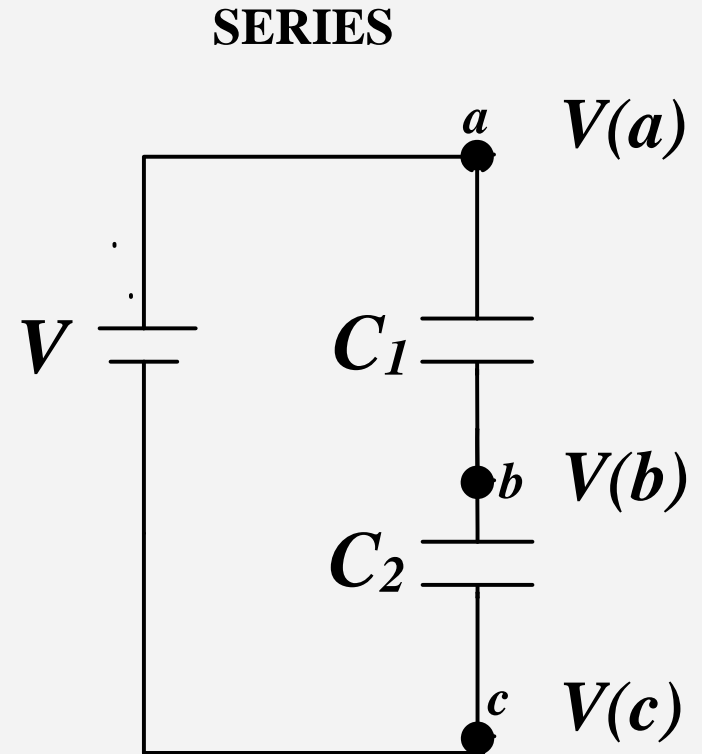- ΔV_{ba} is the potential difference across capacitor C_1



Capacitors in Series II

Capacitors Energy Symbols Circuits

- The difference in potential between points c and a is the potential difference, V , of the battery.


$$\Delta V_{ca} = V(a) - V(c) = V$$

$$\Delta V_{ba} = V(a) - V(b)$$

$$\Delta V_{cb} = V(b) - V(c)$$

$$\Delta V_{ca} = \Delta V_{ba} + \Delta V_{cb}$$

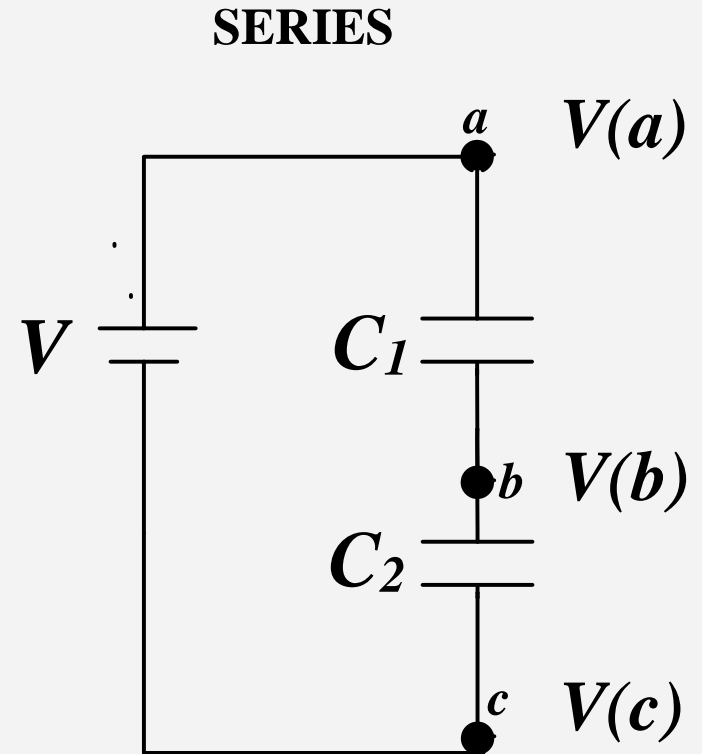- ΔV_{ba} is the potential difference across capacitor C_1 , and ΔV_{cb} is the potential difference across capacitor C_2 .



Capacitors in Series II

Capacitors Energy Symbols Circuits

- The difference in potential between points c and a is the potential difference, V , of the battery.

$$\Delta V_{ca} = V(a) - V(c) = V$$


$$\Delta V_{ba} = V(a) - V(b)$$

$$\Delta V_{cb} = V(b) - V(c)$$

$$\Delta V_{ca} = \Delta V_{ba} + \Delta V_{cb}$$

- ΔV_{ba} is the potential difference across capacitor C_1 , and ΔV_{cb} is the potential difference across capacitor C_2 .

$$V = V_1 + V_2$$

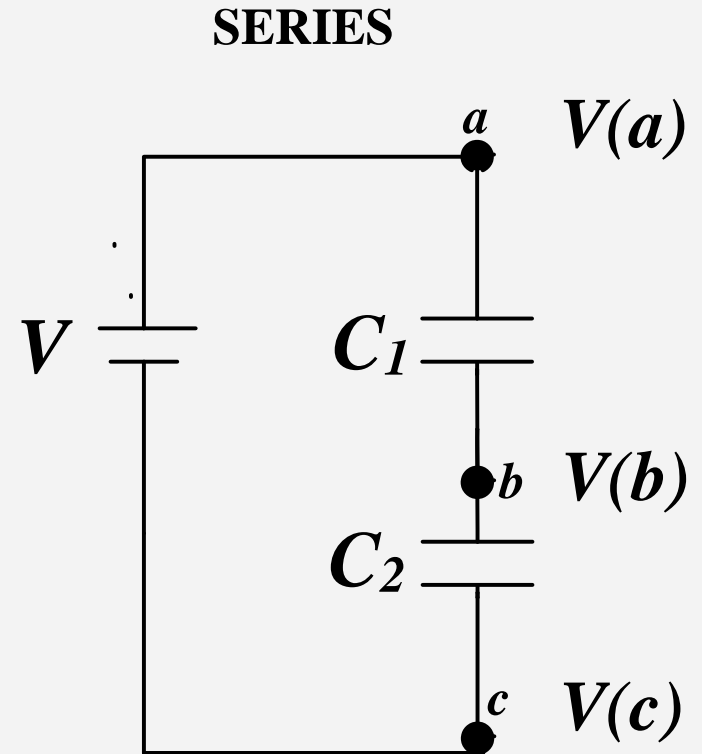


Capacitors in Series III

Capacitors Energy Symbols Circuits

SERIES

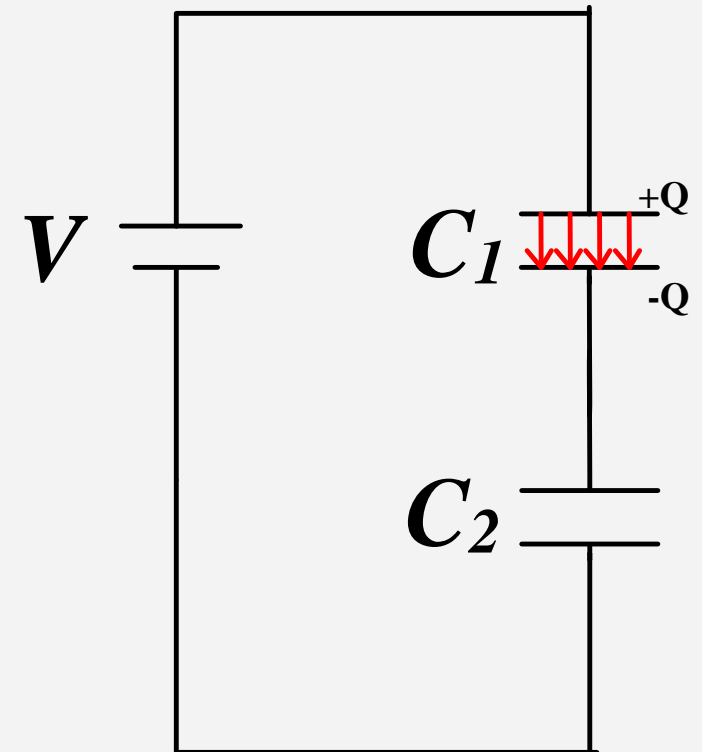- There is a potential difference across C_1 .




Capacitors in Series III

Capacitors Energy Symbols Circuits

- There is a potential difference across C_1 .
- The electric field in C_1 does something to the wire connecting C_1 with C_2 (What is it?).

SERIES

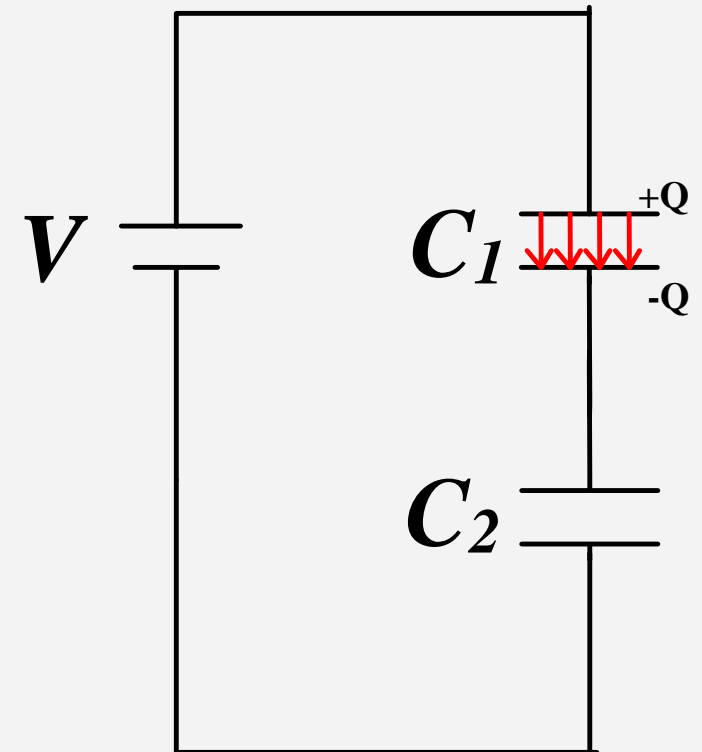


Capacitors in Series III

Capacitors Energy Symbols Circuits

- There is a potential difference across C_1 .
- The electric field in C_1 does something to the wire connecting C_1 with C_2 (What is it?).
- The same magnitude of charge will develop on the top plate of C_2 (due to conservation of charge).

SERIES

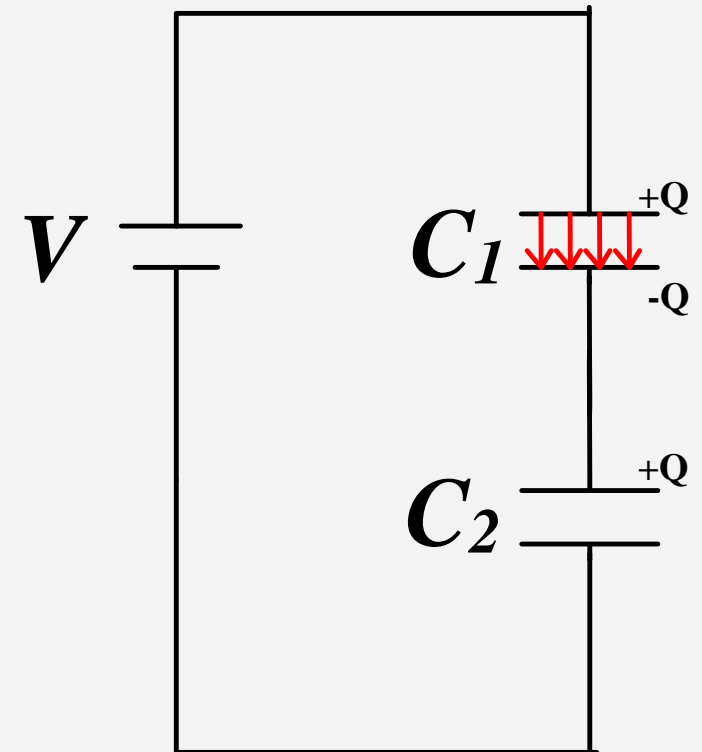


Capacitors in Series III

Capacitors Energy Symbols Circuits

- There is a potential difference across C_1 .
- The electric field in C_1 does something to the wire connecting C_1 with C_2 (What is it?).
- The same magnitude of charge will develop on the top plate of C_2 (due to conservation of charge).
- This charge will create an electric field (but we already knew that - from the previous slide) which will induce a $-Q$ on the bottom plate.

SERIES

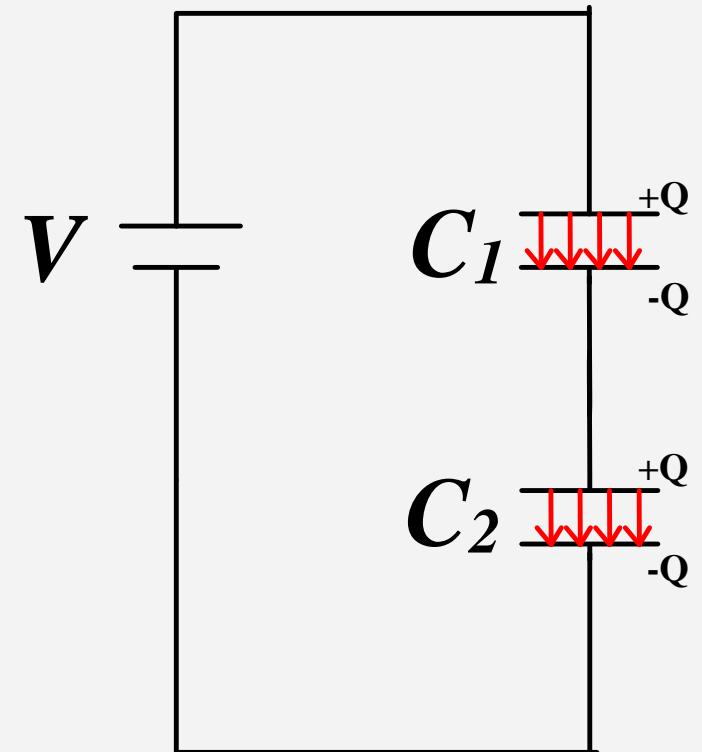


Capacitors in Series III

Capacitors Energy Symbols Circuits

- There is a potential difference across C_1 .
- The electric field in C_1 does something to the wire connecting C_1 with C_2 (What is it?).
- The same magnitude of charge will develop on the top plate of C_2 (due to conservation of charge).
- This charge will create an electric field (but we already knew that - from the previous slide) which will induce a $-Q$ on the bottom plate.
- MORAL OF THE STORY: Capacitors in series have the same amount of charge!!

SERIES

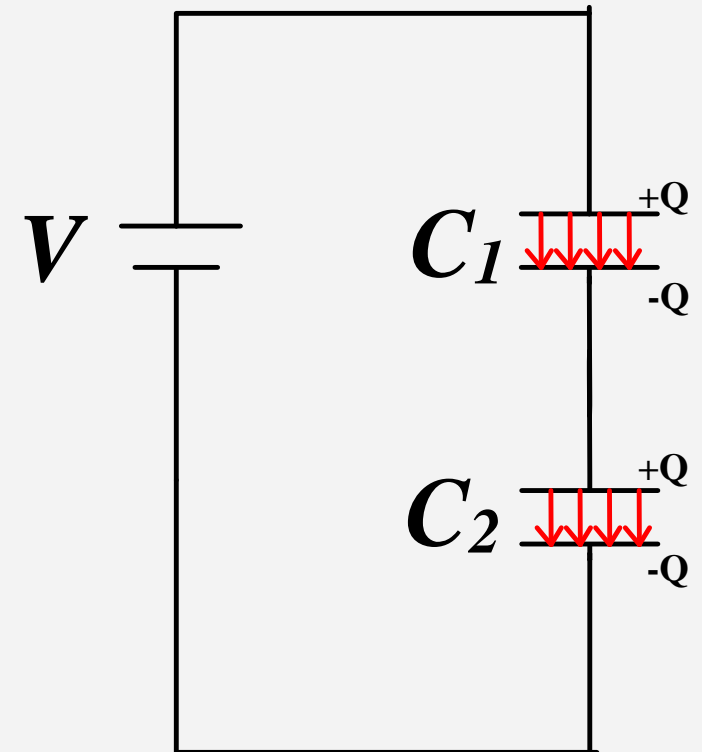


Capacitors in Series IV

Capacitors Energy Symbols Circuits

SERIES

- Starting with:

$$V = V_1 + V_2$$

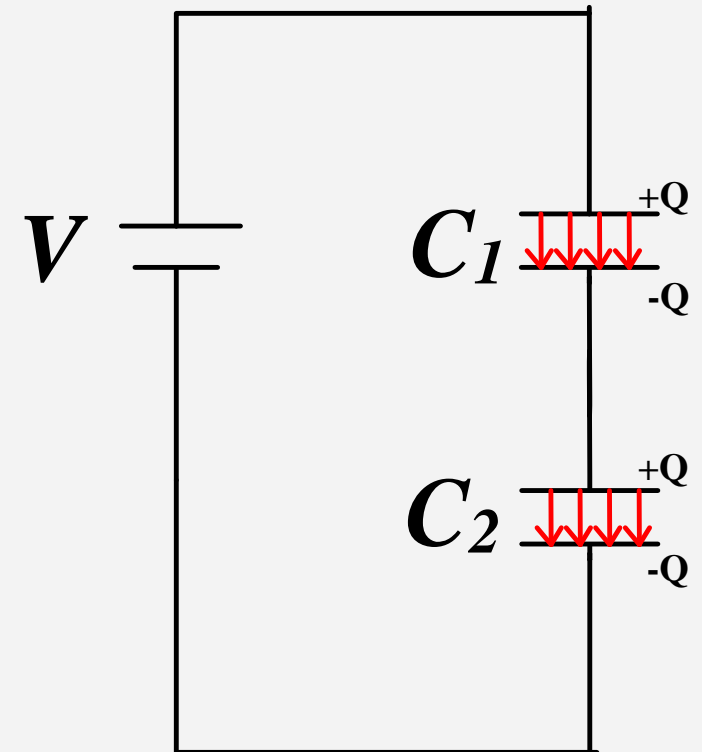


Capacitors in Series IV

Capacitors Energy Symbols Circuits

SERIES

- Starting with:
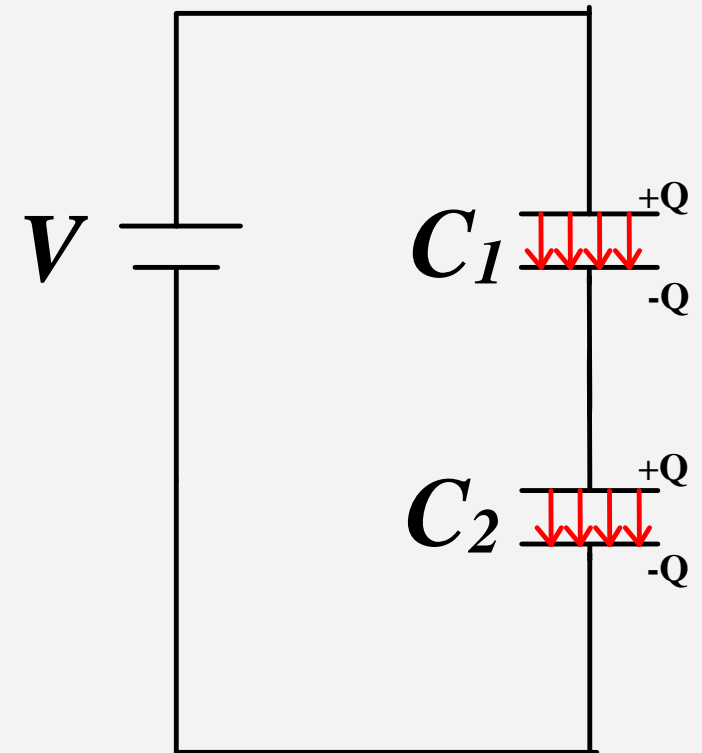
$$V = V_1 + V_2 = \frac{Q_1}{C_1} + \frac{Q_2}{C_2}$$



Capacitors in Series IV


Capacitors Energy Symbols Circuits

SERIES

- Starting with:

$$V = V_1 + V_2 = \frac{Q_1}{C_1} + \frac{Q_2}{C_2}$$
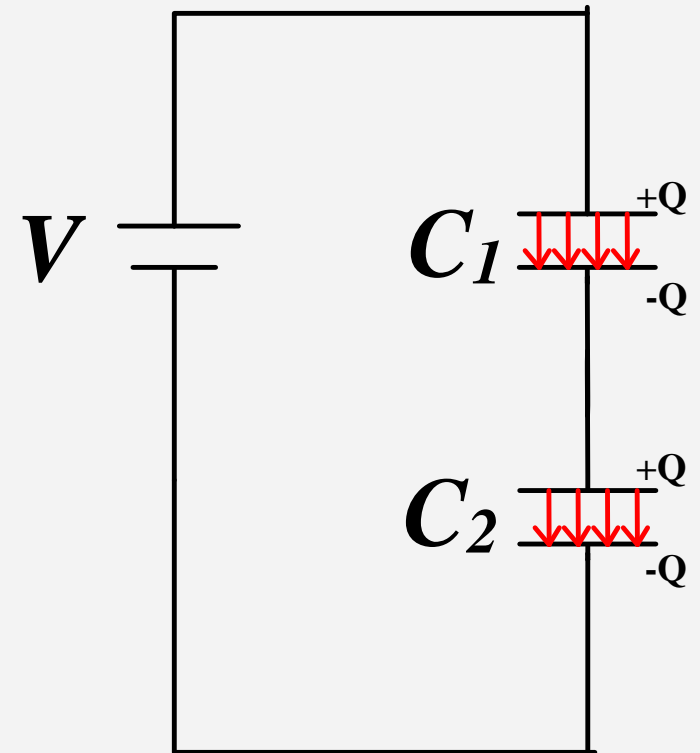
$$V = Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$



Capacitors in Series IV

Capacitors Energy Symbols Circuits


SERIES

- Starting with:

$$V = V_1 + V_2 = \frac{Q_1}{C_1} + \frac{Q_2}{C_2}$$

$$V = Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$
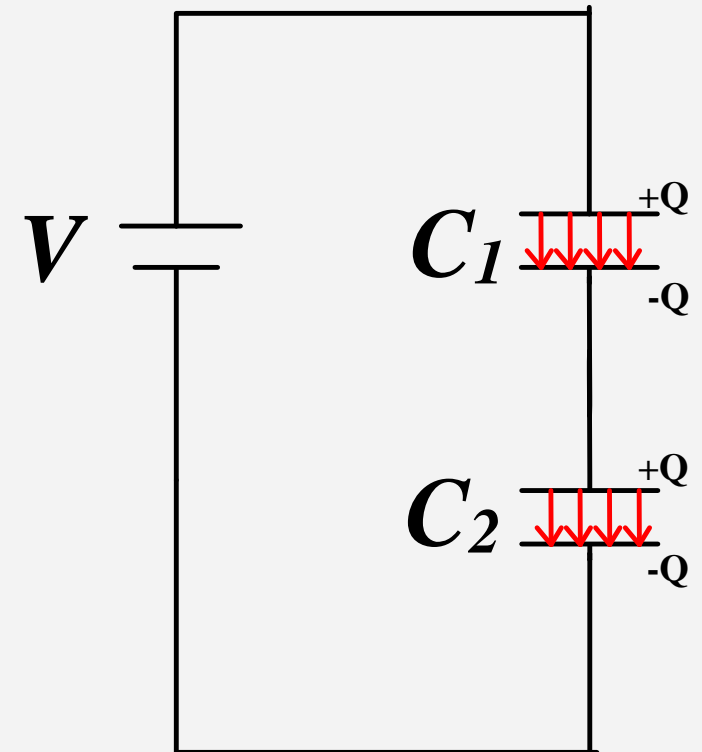
$$V/Q = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$



Capacitors in Series IV

Capacitors Energy Symbols Circuits

SERIES


- Starting with:

$$V = V_1 + V_2 = \frac{Q_1}{C_1} + \frac{Q_2}{C_2}$$

$$V = Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$

$$V/Q = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$
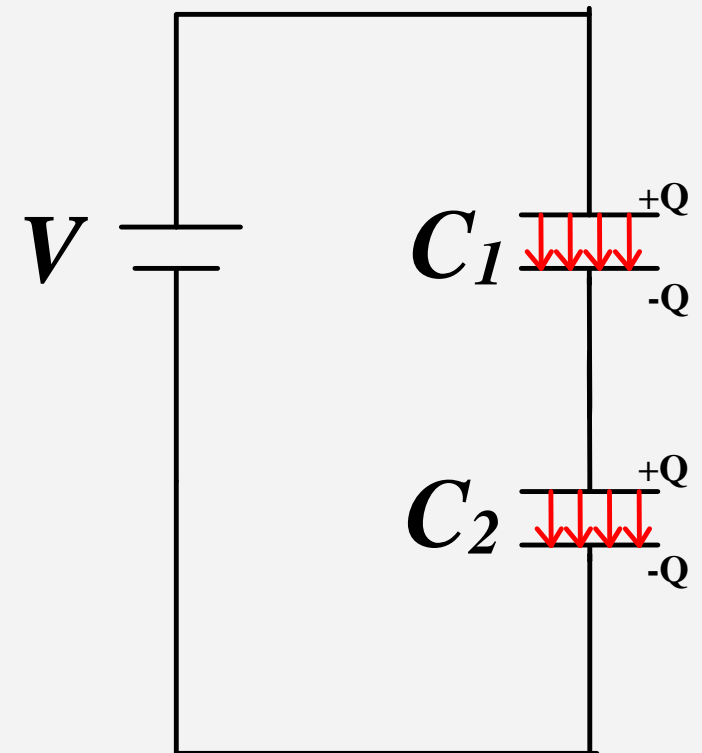
$$1/C = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$




Capacitors in Series V

Capacitors Energy Symbols Circuits

SERIES

$$1/C = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$

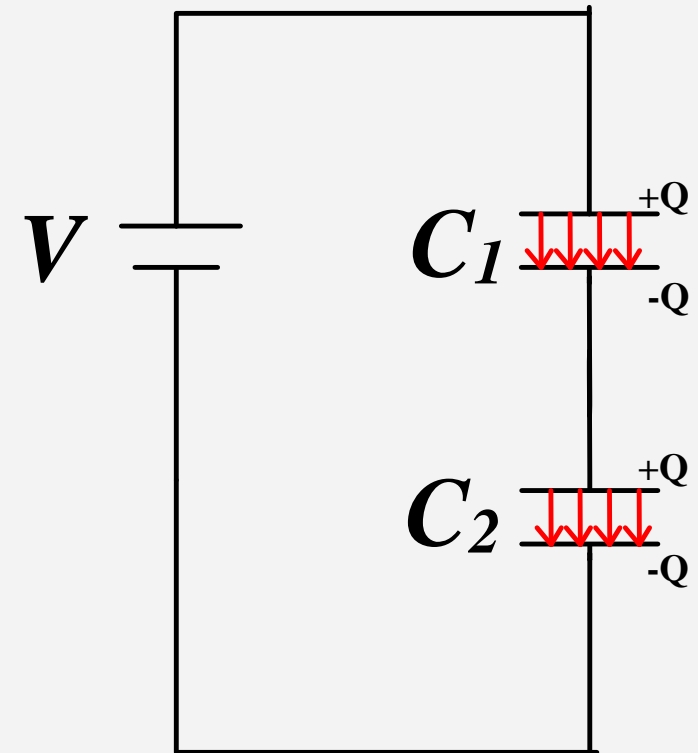- This means that the circuit on the right can be represented by the following circuit.




Capacitors in Series V

Capacitors Energy Symbols Circuits

$$1/C = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$

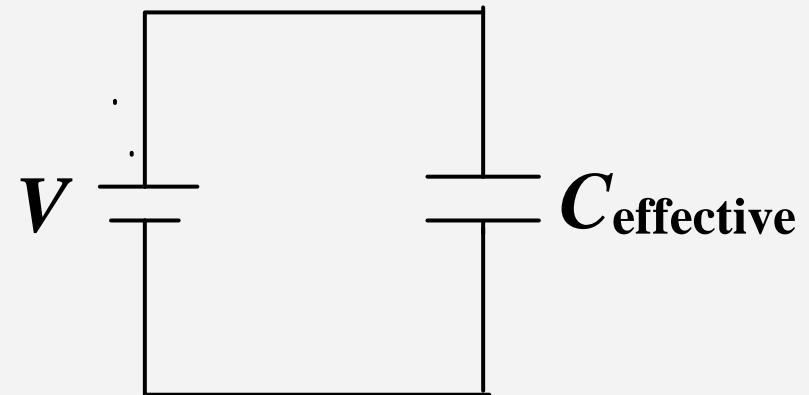- This means that the circuit on the right can be represented by the following circuit.
- Where $1/C_{\text{effective}} = 1/C_1 + 1/C_2$:




Capacitors in Series V

Capacitors Energy Symbols Circuits

$$1/C = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$

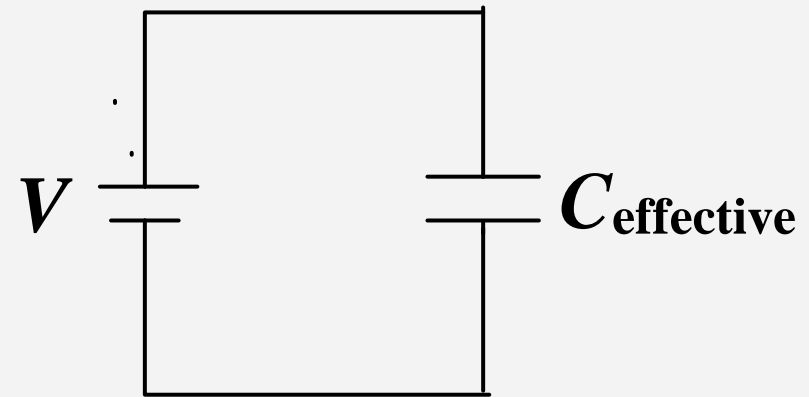- This means that the circuit on the right can be represented by the following circuit.
- Where $1/C_{\text{effective}} = 1/C_1 + 1/C_2$:
- If we generalize for capacitors connected in series:




Capacitors in Series V

Capacitors Energy Symbols Circuits

$$1/C = \left(\frac{1}{C_1} + \frac{1}{C_2}\right)$$

- This means that the circuit on the right can be represented by the following circuit.
- Where $1/C_{\text{effective}} = 1/C_1 + 1/C_2$:
- If we generalize for capacitors connected in series:
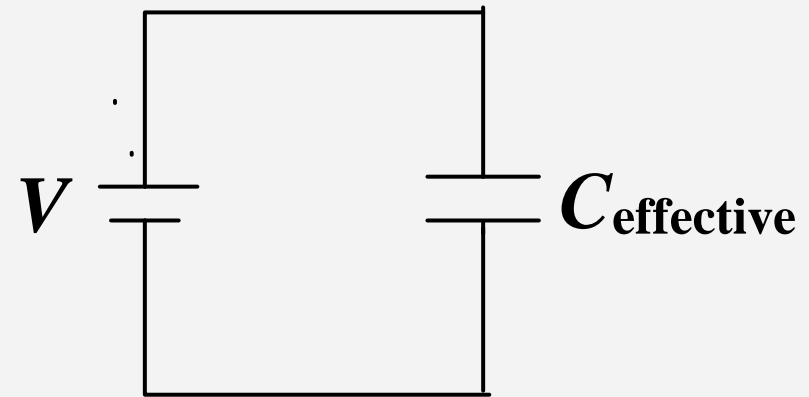
$$\frac{1}{C_{\text{effective}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$





SUMMARY



Capacitors Energy Symbols Circuits

- Parallel circuits:



SUMMARY



Capacitors Energy Symbols Circuits

- Parallel circuits:
 - ◆ Elements in parallel reside at the same potential.



SUMMARY



Capacitors Energy Symbols Circuits

- Parallel circuits:
 - ◆ Elements in parallel reside at the same potential.
 - ◆ For capacitors in parallel, you need to add the capacitance of each capacitor in order to find the effective capacitance.



SUMMARY



Capacitors Energy Symbols Circuits

- Parallel circuits:
 - ◆ Elements in parallel reside at the same potential.
 - ◆ For capacitors in parallel, you need to add the capacitance of each capacitor in order to find the effective capacitance.
- Series circuits:



SUMMARY



Capacitors Energy Symbols Circuits

- Parallel circuits:
 - ◆ Elements in parallel reside at the same potential.
 - ◆ For capacitors in parallel, you need to add the capacitance of each capacitor in order to find the effective capacitance.
- Series circuits:
 - ◆ Capacitors in series have identical charges.



SUMMARY



Capacitors Energy Symbols Circuits

- Parallel circuits:
 - ◆ Elements in parallel reside at the same potential.
 - ◆ For capacitors in parallel, you need to add the capacitance of each capacitor in order to find the effective capacitance.
- Series circuits:
 - ◆ Capacitors in series have identical charges.
 - ◆ For capacitors in series, you need to add the *reciprocal* of the capacitance of each capacitor in order to find the *reciprocal* of the effective capacitance.



Dielectrics



Capacitors Energy Symbols Circuits

Let's move to the chalk board.