

PHYS102
DC-Circuits
with
Inductors

Dr. Suess

April 11, 2007

| | |
|---|----------|
| Induction - Circuits | 2 |
| LR - Circuits | 2 |
| LR - Circuit Conceptually | 3 |
| LR - Circuit Conceptually | 4 |
| Analysis | 5 |
| LR Circuits - Kirchhoff's Rules | 5 |
| Mathematical Equation for Current | 6 |
| Current as a Function of Time | 7 |
| Inductive Time Constant | 8 |
| EMF Through Inductor - Graphing | 9 |

0.1 LR - Circuits - General


LR - Circuits

- We already analyzed the behavior of a solenoid with increasing and decreasing currents.
- Let's now look at circuit containing a resistor and an inductor.
- The circuit still has a direct-current (DC) source i.e., a battery.
- A switch will be used to increase or decrease current through the circuit.

PHYS102

Circuits with Inductors – slide 2

LR - Circuit Conceptually

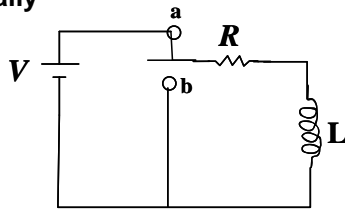


- The magnetic flux through the circuit is initially zero (No current flows in the circuit).
- As soon as the switch is thrown into position (a), a current begins to flow so a magnetic flux through the circuit now exists.
- Initially, the inductor behaves like an infinite resistor “opposes the change in current”.

PHYS102

Circuits with Inductors – slide 3

LR - Circuit Conceptually

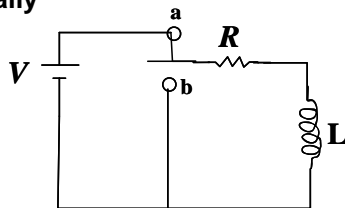

Continuation from last slide.


- After some time, the current in the circuit reaches an equilibrium value.
 - The inductor behaves like a piece of wire ($\epsilon_L = 0$ since $\frac{dI}{dt} = 0$.)

PHYS102

Circuits with Inductors – slide 4

0.2 Ramping Current

LR Circuits - Kirchoff's Rules

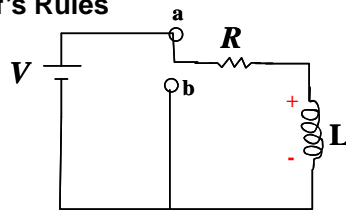

- Begin by applying Kirchoff's rules to the closed circuit.

$$-IR - |\varepsilon_L| + V = 0.$$


$$|\varepsilon_L| = L \frac{dI}{dt}$$

PHYS102

$$\Rightarrow V = IR + L \frac{dI}{dt}$$

Circuits with Inductors – slide 5

Mathematical Equation for Current

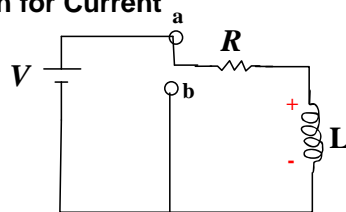

- Continuation from last slide.

$$\Rightarrow V/R = I + L/R \frac{dI}{dt}$$


$$\Rightarrow \frac{dI}{(I - V/R)} = -\frac{R dt}{L}$$

PHYS102

$$\Rightarrow \int \frac{dI}{(I - V/R)} = - \int \frac{R dt}{L}$$

Circuits with Inductors – slide 6

Current as a Function of Time

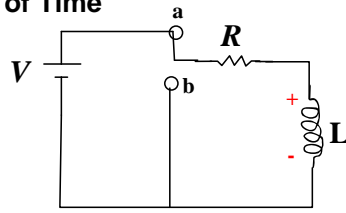

- Continuation from last slide.

$$\Rightarrow \int \frac{dI}{(I - V/R)} = - \int \frac{R dt}{L}$$


$$I = \frac{V}{R} (1 - e^{-Rt/L})$$

PHYS102

Circuits with Inductors – slide 7

NOTE: L/R has units of seconds.

Inductive Time Constant

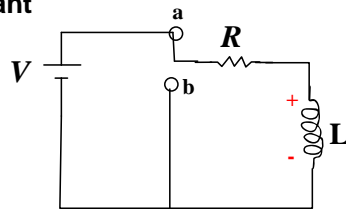

- Continuation from last slide.

$$I = \frac{V}{R} (1 - e^{-Rt/L})$$

$$I = \frac{V}{R} (1 - e^{-t/\tau_L}) \quad (\text{where } \tau_L \equiv L/R)$$


PHYS102

Circuits with Inductors – slide 8

τ_L is called the "inductive" time constant for the circuit.

0.3 Graphing Current and EMF

EMF Through Inductor - Graphing

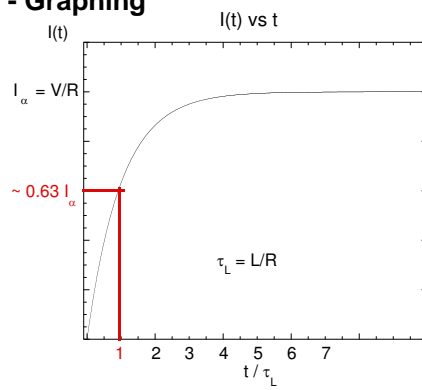

$$I(t) = \frac{V}{R} \left(1 - e^{-Rt/L}\right)$$

- The current through the inductor builds up over time (just like we stated conceptually).

Circuits with Inductors – slide 9

- What happens to the EMF in the inductor?