

PHYS102
DC-Circuits
with
Inductors

Dr. Suess

April 13, 2007


LR Circuit - Equation for Current

- LR Circuit - Equation for Current

- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

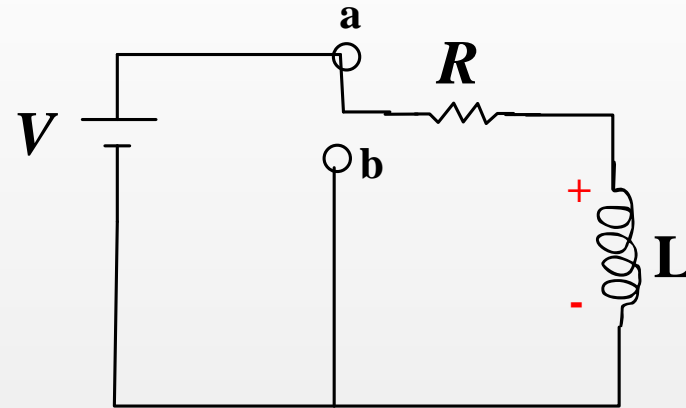


LR Circuit - Equation for Current

- LR Circuit - Equation for Current

- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

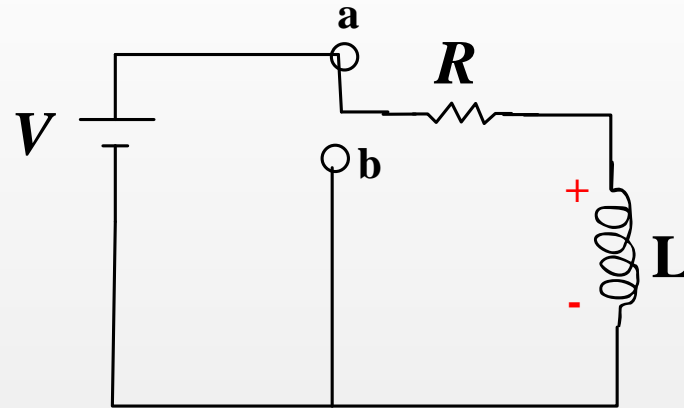


LR Circuit - Equation for Current

- LR Circuit - Equation for Current

- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

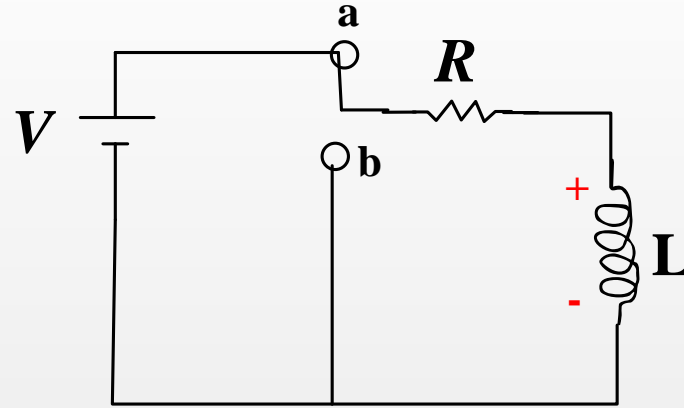

$$\Rightarrow \int \frac{dI}{(I - V/R)} = - \int \frac{R dt}{L}$$


LR Circuit - Equation for Current

- LR Circuit - Equation for Current

- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

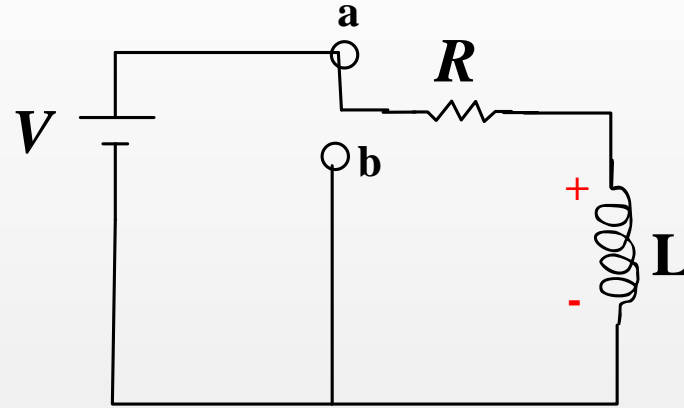

$$\Rightarrow \int \frac{dI}{(I - V/R)} = - \int \frac{R dt}{L}$$

$$I = \frac{V}{R} (1 - e^{-Rt/L})$$


LR Circuit - Equation for Current

- LR Circuit - Equation for Current

- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

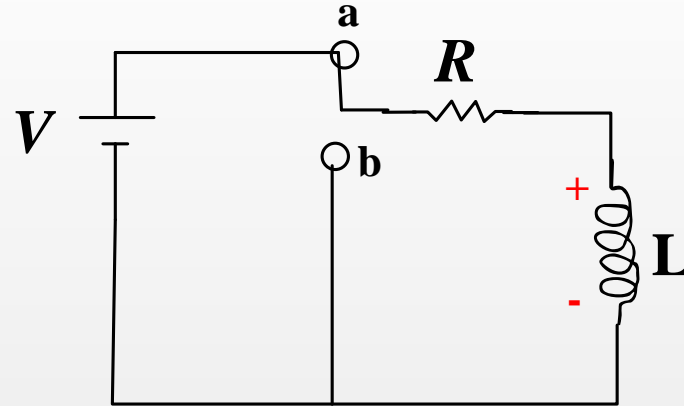

$$\Rightarrow \int \frac{dI}{(I - V/R)} = - \int \frac{R dt}{L}$$

$$I = \frac{V}{R} (1 - e^{-Rt/L})$$

NOTE: L/R has units of seconds.


LR Circuit - Equation for Current

- LR Circuit - Equation for Current

- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

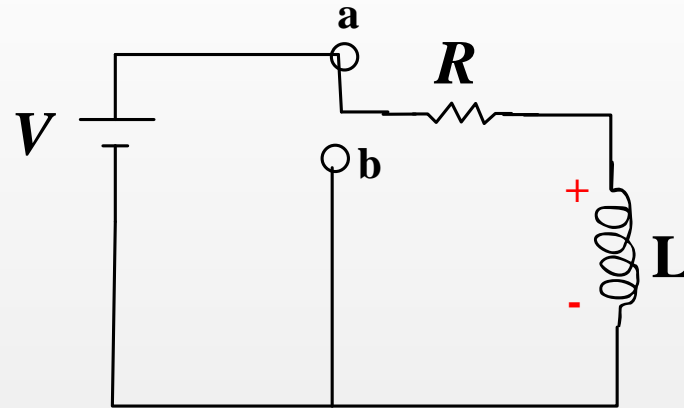

$$\Rightarrow \int \frac{dI}{(I - V/R)} = - \int \frac{R dt}{L}$$

$$I = \frac{V}{R} (1 - e^{-Rt/L})$$


NOTE: L/R has units of **seconds**.

Inductive Time Constant

- LR Circuit - Equation for Current
- **Inductive Time Constant**
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

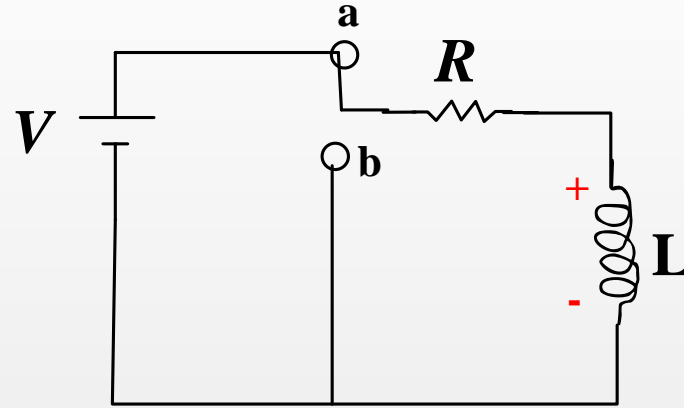


Inductive Time Constant

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

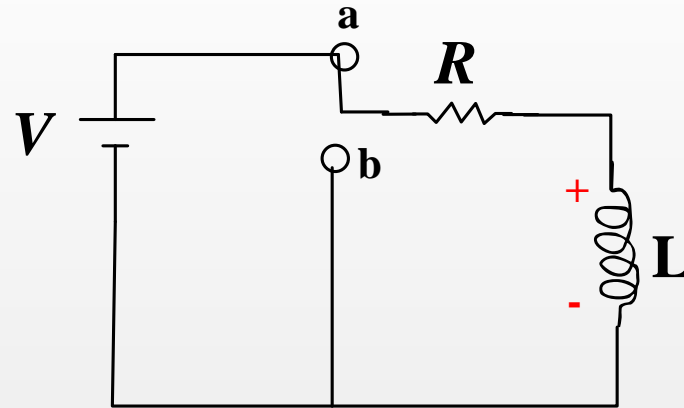

- Continuation from last slide.

Inductive Time Constant

- LR Circuit - Equation for Current

- Inductive Time Constant

- Current Behavior - Graphing

- Graphing - EMF of Inductor


- Disconnecting the Battery

- Current Decay through LR Circuits

- LR - RC Circuit Comparison

Energy

LC - Oscillator

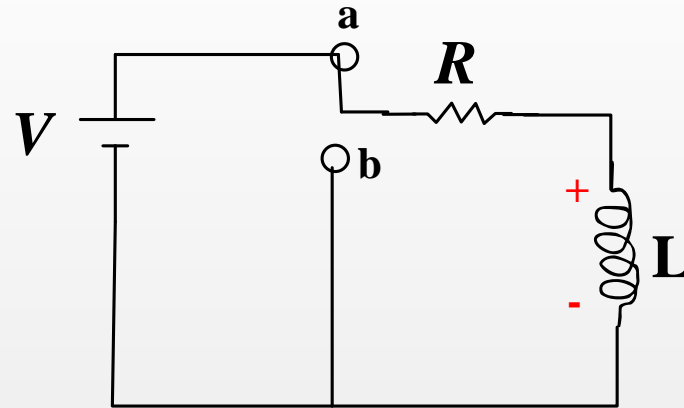

- Continuation from last slide.

$$I = \frac{V}{R} (1 - e^{-Rt/L})$$

Inductive Time Constant

- LR Circuit - Equation for Current

- Inductive Time Constant

- Current Behavior - Graphing

- Graphing - EMF of Inductor


- Disconnecting the Battery

- Current Decay through LR Circuits

- LR - RC Circuit Comparison

Energy

LC - Oscillator

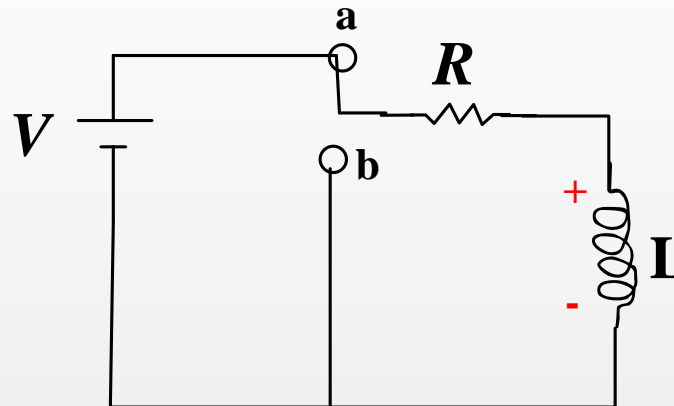

- Continuation from last slide.

$$I = \frac{V}{R} (1 - e^{-Rt/L})$$

$$I = \frac{V}{R} (1 - e^{-t/\tau_L}) \quad (\text{where } \tau_L \equiv L/R)$$

Inductive Time Constant

- LR Circuit - Equation for Current

- Inductive Time Constant

- Current Behavior - Graphing

- Graphing - EMF of Inductor


- Disconnecting the Battery

- Current Decay through LR Circuits

- LR - RC Circuit Comparison

Energy

LC - Oscillator

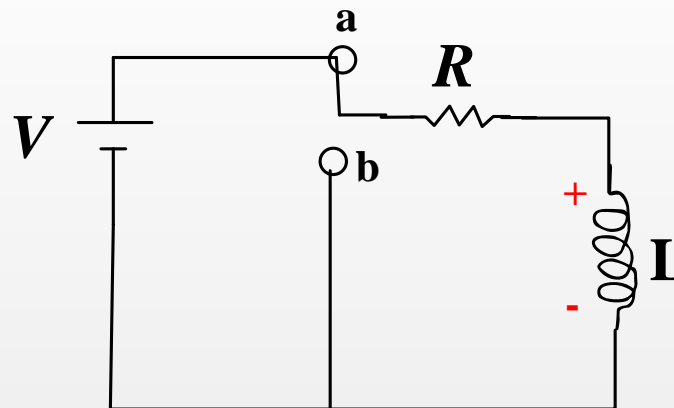

- Continuation from last slide.

$$I = \frac{V}{R} (1 - e^{-Rt/L})$$

$$I = \frac{V}{R} (1 - e^{-t/\tau_L}) \quad (\text{where } \tau_L \equiv L/R)$$

τ_L is called the “inductive” time constant for the circuit.

Inductive Time Constant

- LR Circuit - Equation for Current

- Inductive Time Constant

- Current Behavior - Graphing

- Graphing - EMF of Inductor


- Disconnecting the Battery

- Current Decay through LR Circuits

- LR - RC Circuit Comparison

Energy

LC - Oscillator

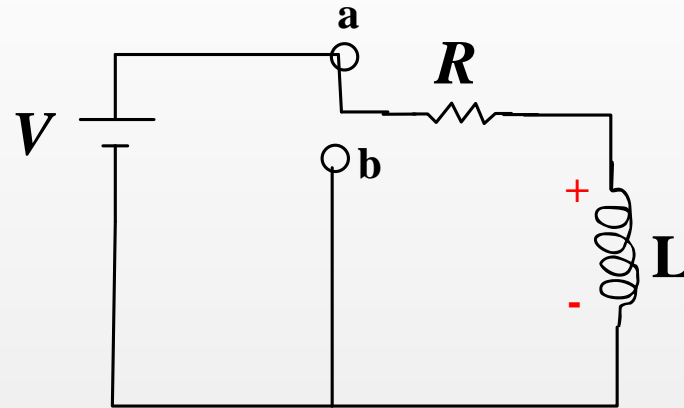

- Continuation from last slide.

$$I = \frac{V}{R} (1 - e^{-Rt/L})$$

$$I = \frac{V}{R} (1 - e^{-t/\tau_L}) \quad (\text{where } \tau_L \equiv L/R)$$


τ_L is called the “inductive” time constant for the circuit.

Current Behavior - Graphing

- LR Circuit - Equation for Current
- Inductive Time Constant
- **Current Behavior - Graphing**
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

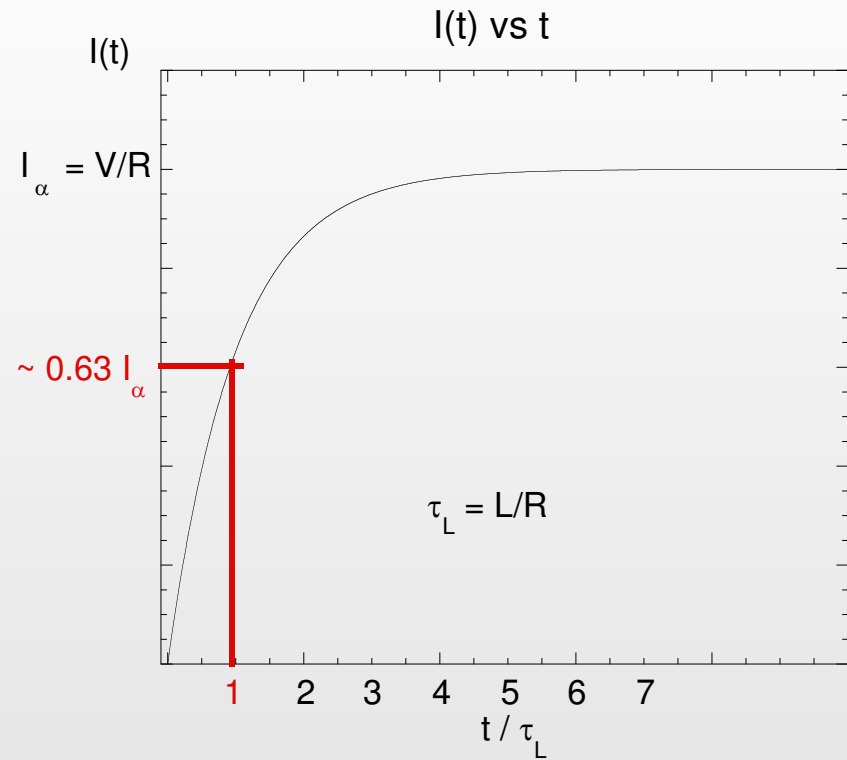


Current Behavior - Graphing

- LR Circuit - Equation for Current
- Inductive Time Constant
- **Current Behavior - Graphing**
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

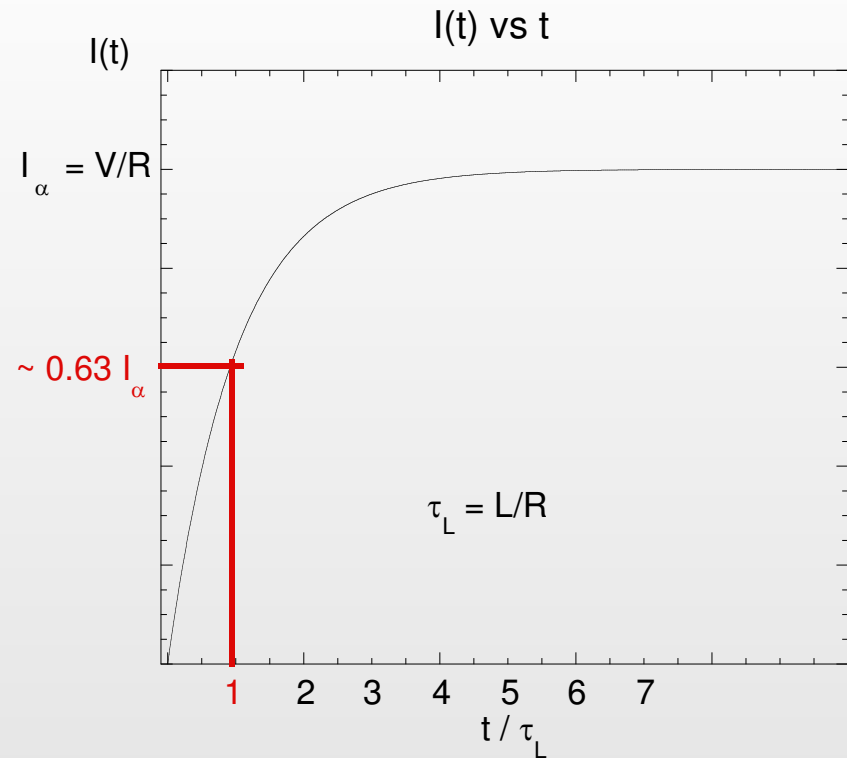


$$I(t) = \frac{V}{R} \left(1 - e^{-Rt/L} \right)$$

Current Behavior - Graphing

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

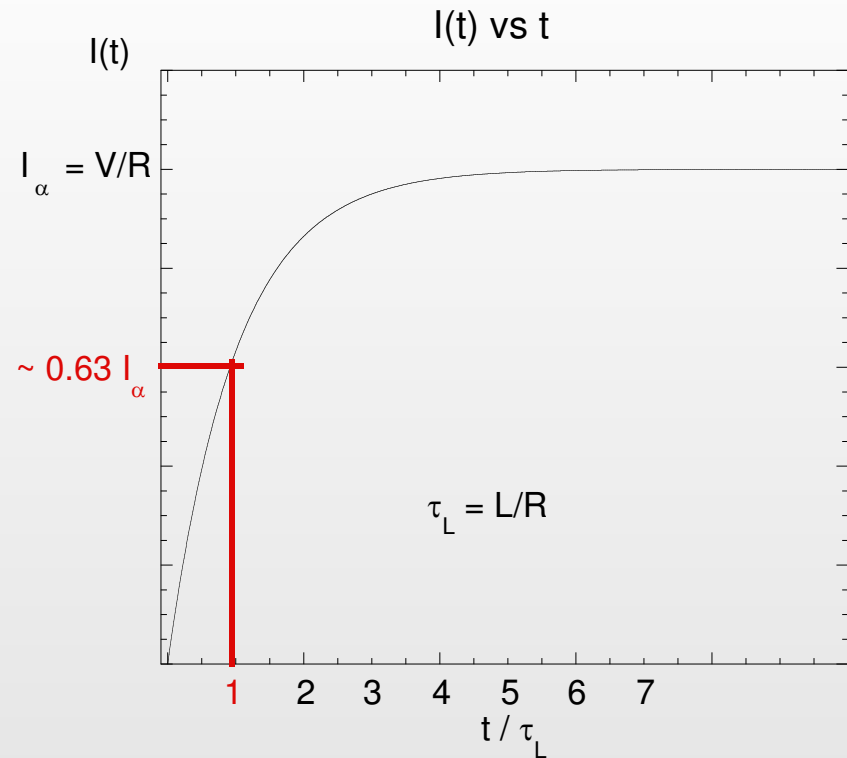

$$I(t) = \frac{V}{R} \left(1 - e^{-Rt/L}\right)$$


- The current through the inductor builds up over time

Current Behavior - Graphing

- LR Circuit - Equation for Current
- Inductive Time Constant
- **Current Behavior - Graphing**
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

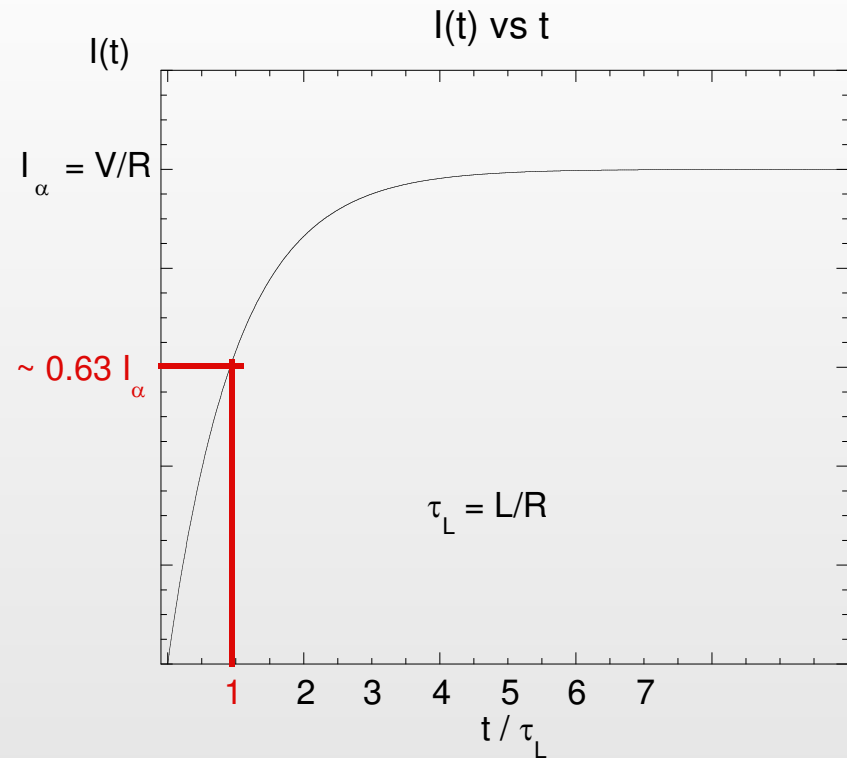

$$I(t) = \frac{V}{R} \left(1 - e^{-Rt/L}\right)$$


- The current through the inductor builds up over time (just like we stated conceptually).

Current Behavior - Graphing

- LR Circuit - Equation for Current
- Inductive Time Constant
- **Current Behavior - Graphing**
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

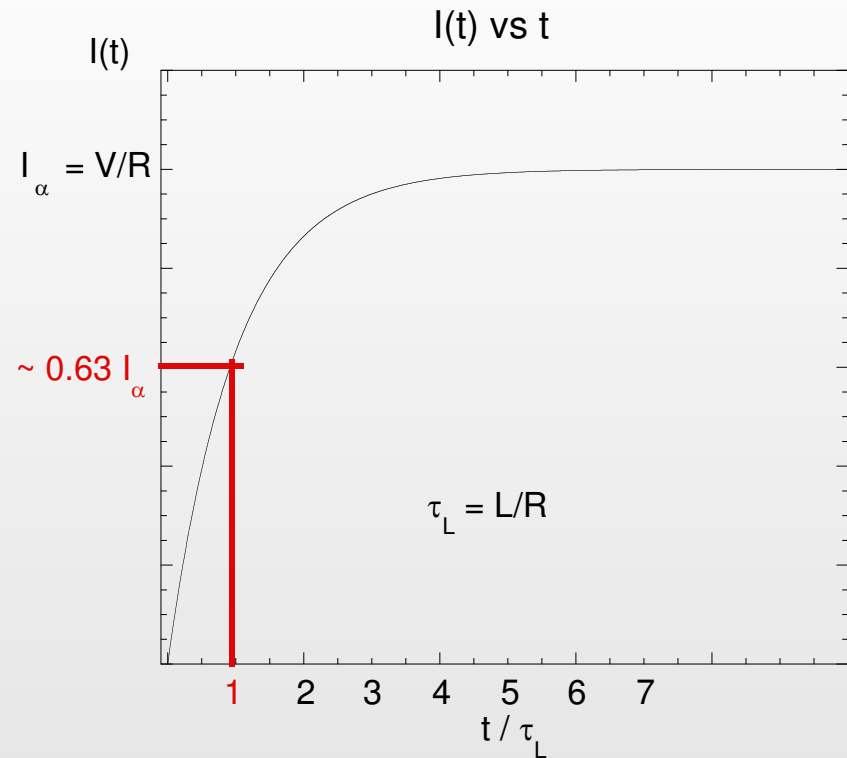

$$I(t) = \frac{V}{R} \left(1 - e^{-Rt/L} \right)$$


- The current through the inductor builds up over time (just like we stated conceptually).
- What happens to the EMF in the inductor?

Graphing - EMF of Inductor

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- **Graphing - EMF of Inductor**
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

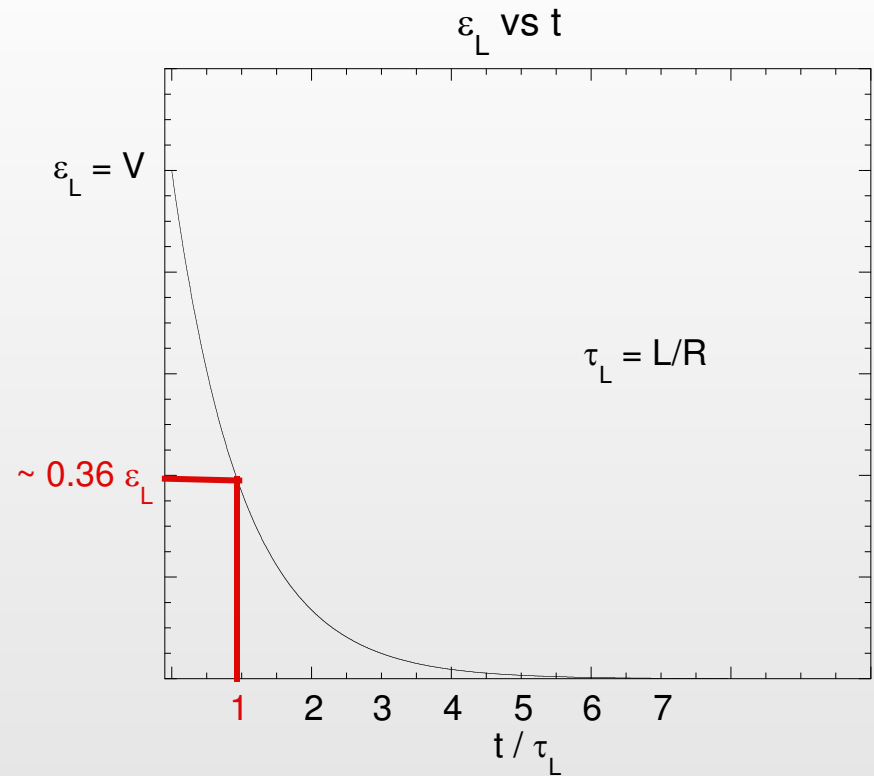


Graphing - EMF of Inductor

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- **Graphing - EMF of Inductor**
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator
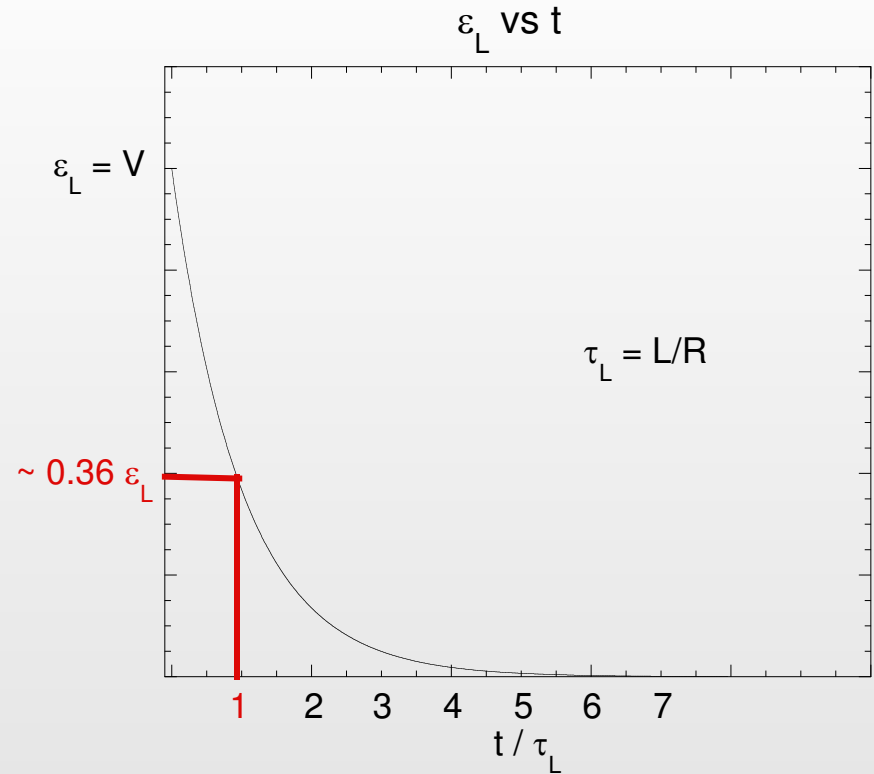
$$I(t) = \frac{V}{R} \left(1 - e^{-Rt/L}\right)$$




Graphing - EMF of Inductor

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- **Graphing - EMF of Inductor**
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator
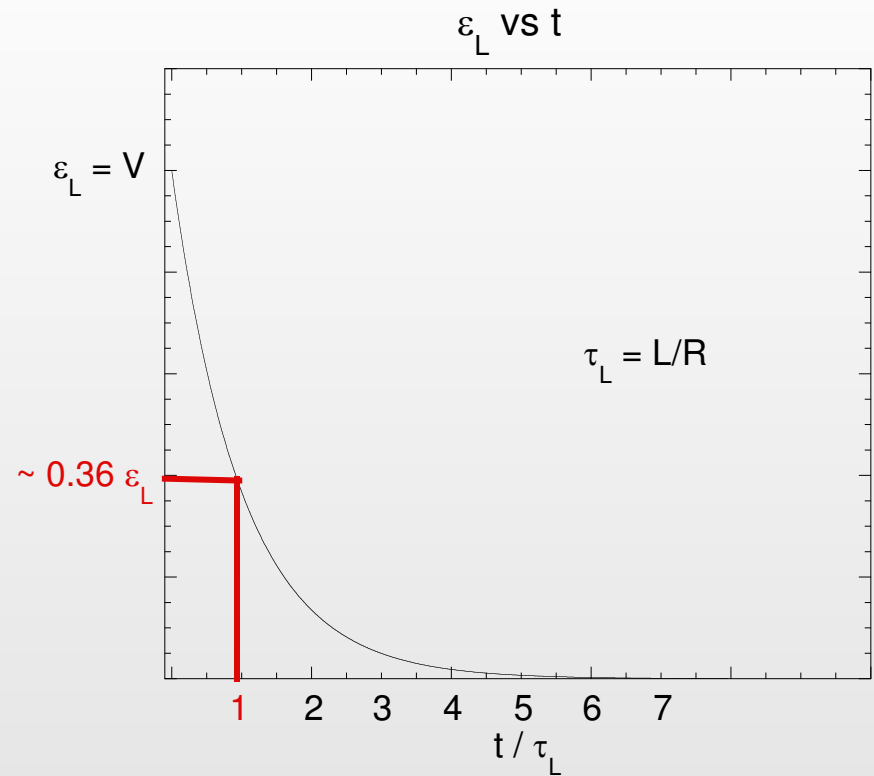
$$I(t) = \frac{V}{R} \left(1 - e^{-Rt/L}\right)$$
$$\varepsilon_L = -L \frac{dI}{dt} = V e^{-Rt/L}$$




Graphing - EMF of Inductor

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- **Graphing - EMF of Inductor**
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

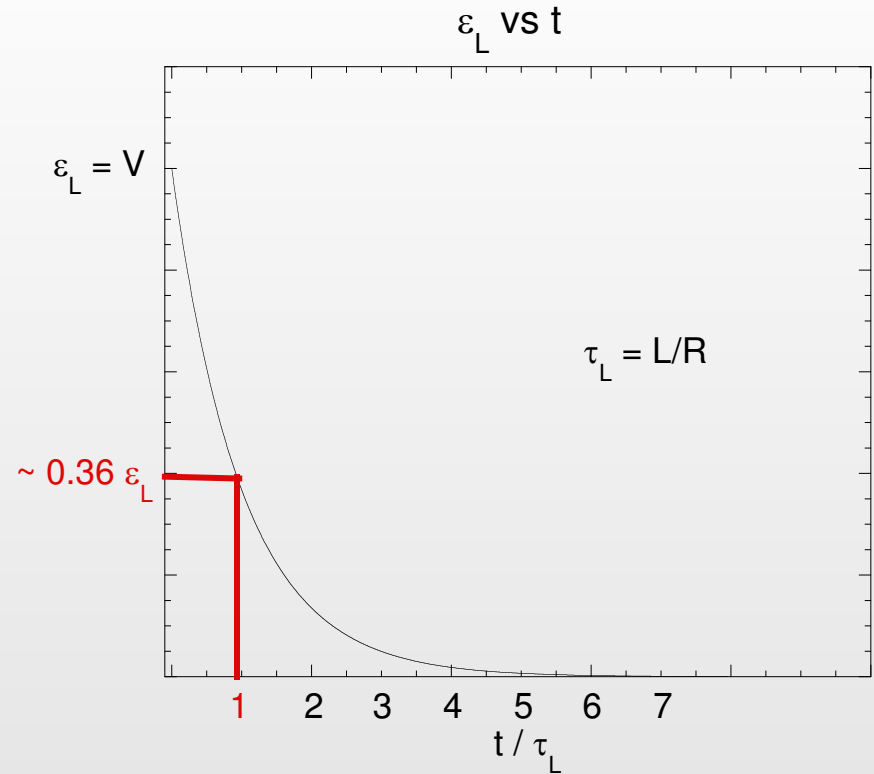

$$I(t) = \frac{V}{R} \left(1 - e^{-Rt/L}\right)$$
$$\varepsilon_L = -L \frac{dI}{dt} = V e^{-Rt/L}$$


- The EMF in the inductor approaches zero as the current in the circuit reaches equilibrium (i.e., current does not fluctuate).

Disconnecting the Battery

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- **Disconnecting the Battery**
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

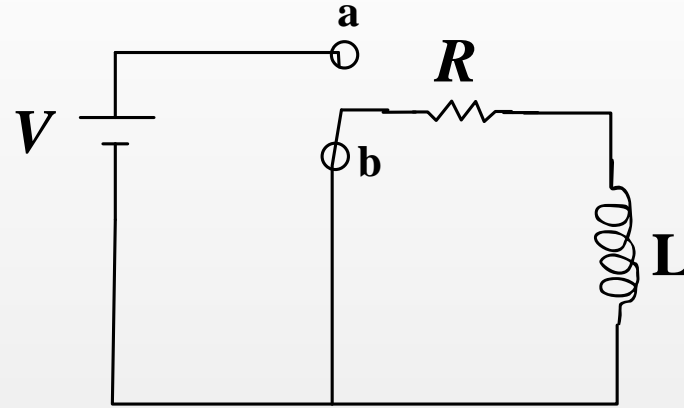


Disconnecting the Battery

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- **Disconnecting the Battery**
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

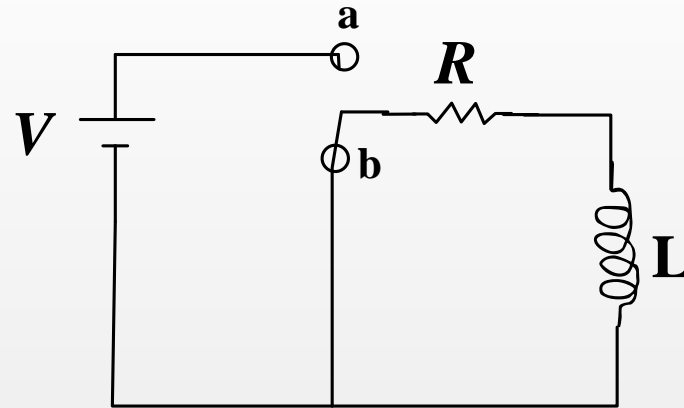


- After a very long time, the switch is thrown into position (b).

Disconnecting the Battery

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- **Disconnecting the Battery**
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

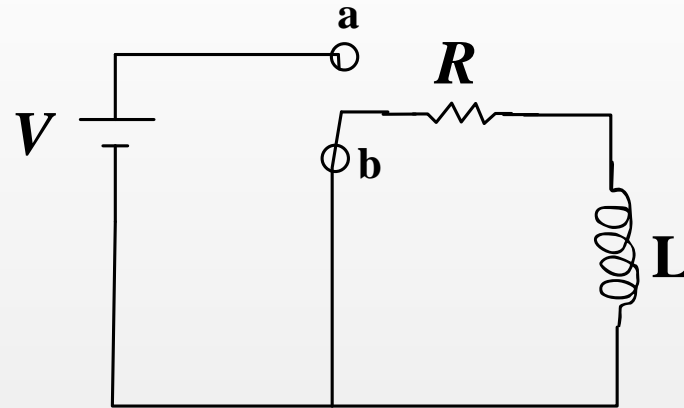


- After a very long time, the switch is thrown into position (b).
 - The battery is disconnected from the rest of the circuit.

Disconnecting the Battery

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- **Disconnecting the Battery**
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

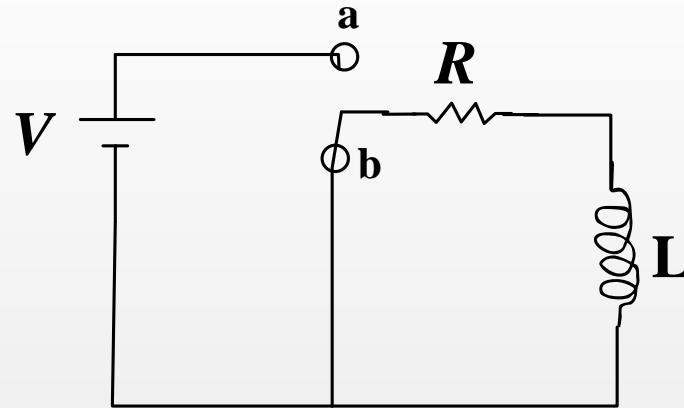


- After a very long time, the switch is thrown into position (b).
 - The battery is disconnected from the rest of the circuit.
- Writing Kirchhoff's Rules for this loop:

Disconnecting the Battery

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- **Disconnecting the Battery**
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

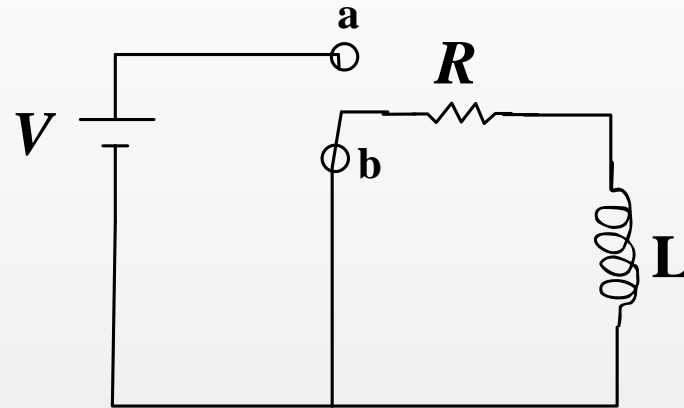

- After a very long time, the switch is thrown into position (b).
 - The battery is disconnected from the rest of the circuit.
- Writing Kirchhoff's Rules for this loop:


$$-I R - |\varepsilon_L| = 0.$$

Disconnecting the Battery

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- **Disconnecting the Battery**
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

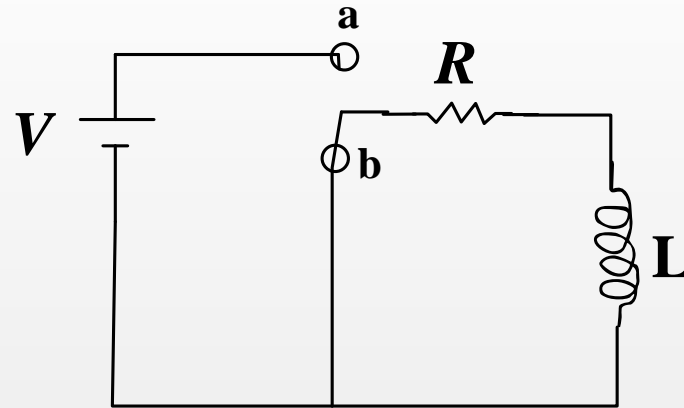

- After a very long time, the switch is thrown into position (b).
 - The battery is disconnected from the rest of the circuit.
- Writing Kirchhoff's Rules for this loop:

$$-I R - |\varepsilon_L| = 0.$$


$$\Rightarrow L \frac{dI}{dt} = -I R$$

Current Decay through LR Circuits

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- **Current Decay through LR Circuits**
- LR - RC Circuit Comparison

Energy

LC - Oscillator

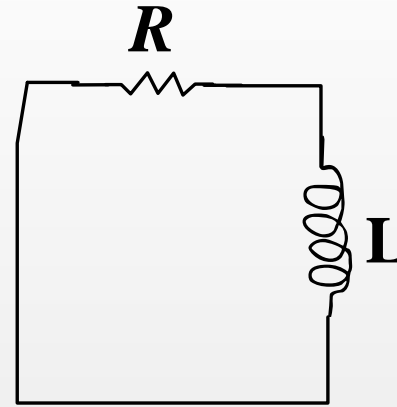


- Continuation from the last slide.

Current Decay through LR Circuits

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- **Current Decay through LR Circuits**
- LR - RC Circuit Comparison

Energy

LC - Oscillator

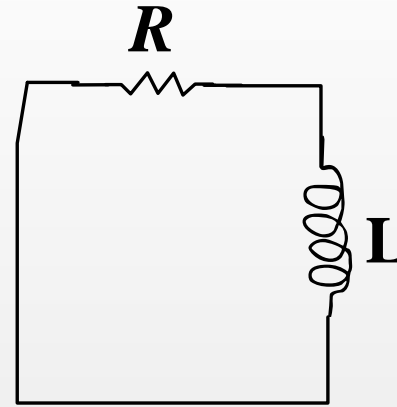

- Continuation from the last slide.


$$L \frac{dI}{dt} = -I R$$

Current Decay through LR Circuits

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- **Current Decay through LR Circuits**
- LR - RC Circuit Comparison

Energy

LC - Oscillator

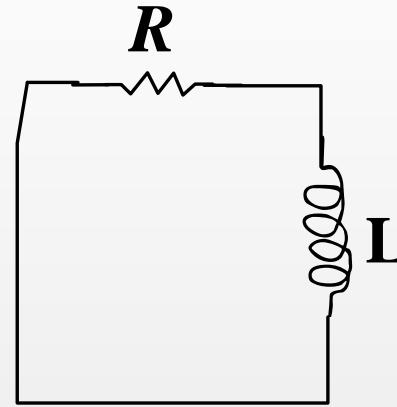

- Continuation from the last slide.

$$L \frac{dI}{dt} = -I R$$


$$\Rightarrow \frac{dI}{I} = - \frac{R}{L} dt$$

Current Decay through LR Circuits

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

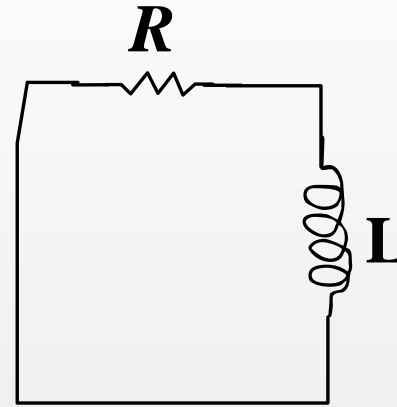

- Continuation from the last slide.

$$L \frac{dI}{dt} = -I R$$

$$\Rightarrow \frac{dI}{I} = - \frac{R}{L} dt$$


$$\Rightarrow I(t) = I_0 e^{-t/\tau_L}$$

Current Decay through LR Circuits

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

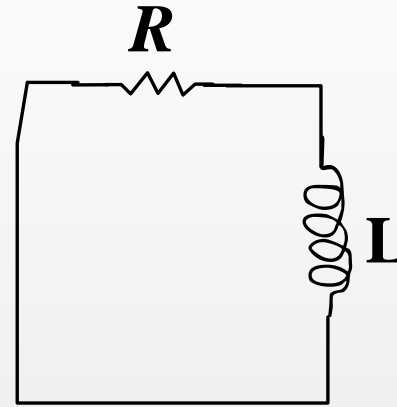

- Continuation from the last slide.

$$L \frac{dI}{dt} = -I R$$
$$\Rightarrow \frac{dI}{I} = - \frac{R}{L} dt$$
$$\Rightarrow I(t) = I_0 e^{-t/\tau_L}$$

- I_0 represents the current through the inductor right before the switch was thrown into position (b).

LR - RC Circuit Comparison

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

- The equations used to describe the current through the inductor (RL circuit) and the charge on a capacitor (RC circuit) look identical in form.

LR - RC Circuit Comparison

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

- The equations used to describe the current through the inductor (RL circuit) and the charge on a capacitor (RC circuit) look identical in form.
- We calculated the energy stored in a capacitor by considering the buildup of charge.

LR - RC Circuit Comparison

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

- The equations used to describe the current through the inductor (RL circuit) and the charge on a capacitor (RC circuit) look identical in form.
- We calculated the energy stored in a capacitor by considering the buildup of charge.
 - What is the energy of an inductor with current flowing through it?

LR - RC Circuit Comparison

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

- The equations used to describe the current through the inductor (RL circuit) and the charge on a capacitor (RC circuit) look identical in form.
- We calculated the energy stored in a capacitor by considering the buildup of charge.
 - What is the energy of an inductor with current flowing through it?
- Start with the circuit first discussed in this lecture!


Energy Stored in Inductors

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- **Energy Stored in Inductors**
- Current and Energy in Inductors
- Magnetic Energy Density

LC - Oscillator

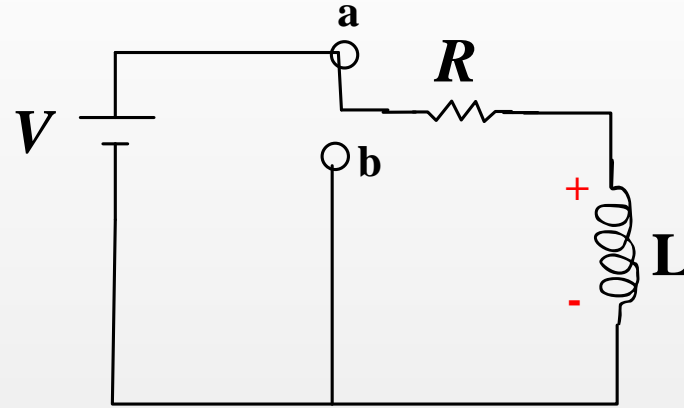

- From Kirchoff's Rules:


Energy Stored in Inductors

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- Magnetic Energy Density

LC - Oscillator

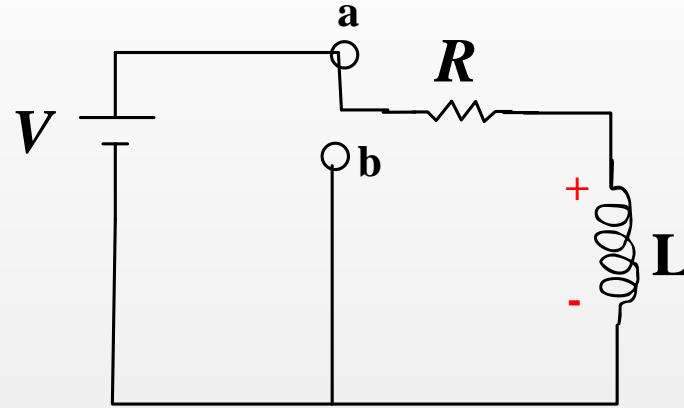

- From Kirchhoff's Rules:

$$\Rightarrow V = IR + L \frac{dI}{dt}$$


Energy Stored in Inductors

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- Magnetic Energy Density

LC - Oscillator

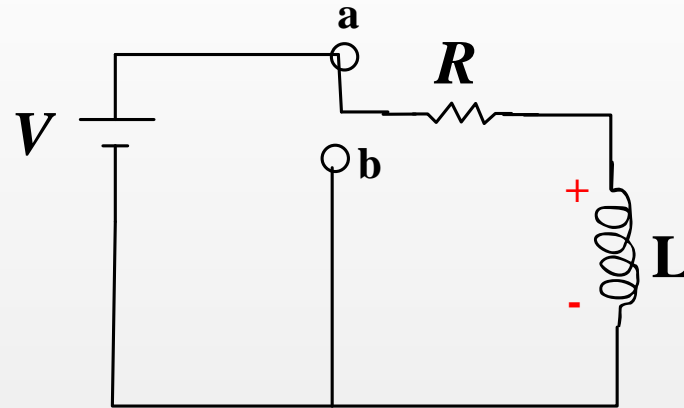

- From Kirchhoff's Rules:

$$\Rightarrow V = IR + L \frac{dI}{dt}$$

- Multiply both sides of the equation by I .


Energy Stored in Inductors

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- Magnetic Energy Density

LC - Oscillator

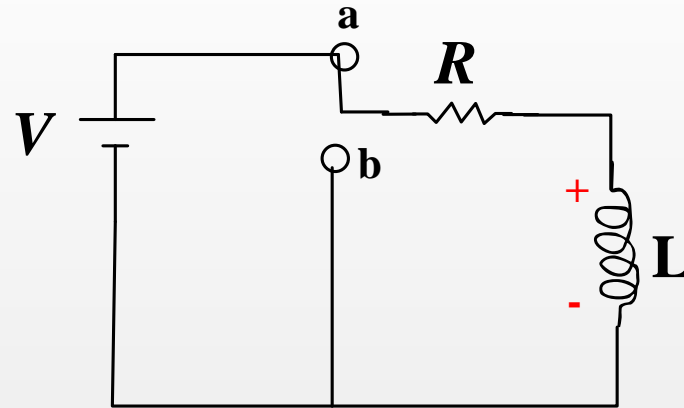

- From Kirchhoff's Rules:

$$\Rightarrow V = IR + L \frac{dI}{dt}$$

- Multiply both sides of the equation by I .

$$\Rightarrow VI = I^2 R + LI \frac{dI}{dt}$$


Energy Stored in Inductors

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- Magnetic Energy Density

LC - Oscillator

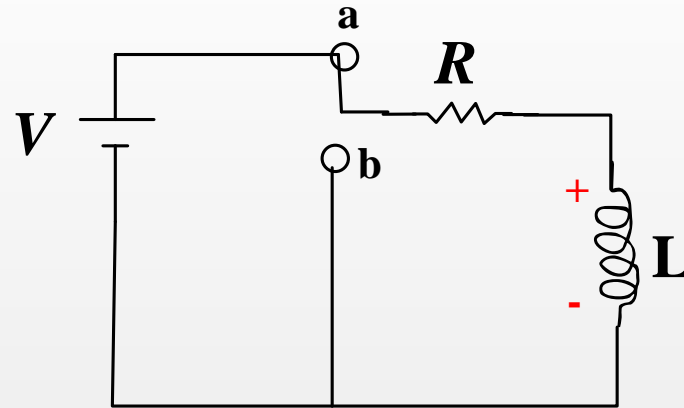

- From Kirchhoff's Rules:

$$\Rightarrow V = IR + L \frac{dI}{dt}$$

- Multiply both sides of the equation by I .

$$\Rightarrow VI = I^2 R + LI \frac{dI}{dt}$$

- The VI term is the power delivered by the battery.


Energy Stored in Inductors

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- Magnetic Energy Density

LC - Oscillator

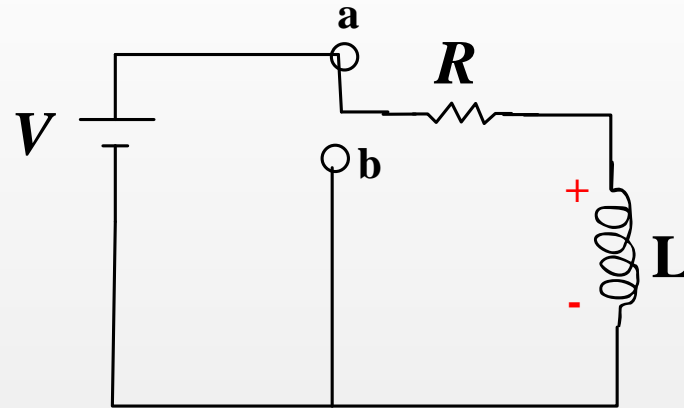

- From Kirchhoff's Rules:

$$\Rightarrow V = IR + L \frac{dI}{dt}$$

- Multiply both sides of the equation by I .

$$\Rightarrow VI = I^2 R + LI \frac{dI}{dt}$$

- The VI term is the power delivered by the battery. The $I^2 R$ term is the power dissipated by the resistor.


Energy Stored in Inductors

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- Magnetic Energy Density

LC - Oscillator

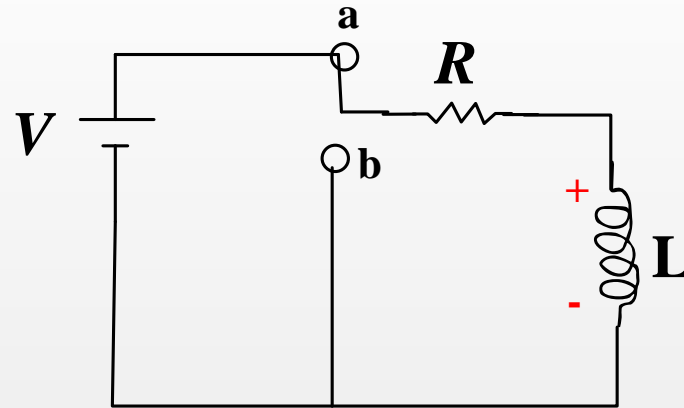

- From Kirchhoff's Rules:

$$\Rightarrow V = IR + L \frac{dI}{dt}$$

- Multiply both sides of the equation by I .

$$\Rightarrow VI = I^2 R + LI \frac{dI}{dt}$$

- The VI term is the power delivered by the battery. The $I^2 R$ term is the power dissipated by the resistor. This means the $LI \frac{dI}{dt}$ term is the power stored in the inductor.

Current and Energy in Inductors

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- **Current and Energy in Inductors**
- Magnetic Energy Density

LC - Oscillator

- Power is the rate of change of Energy per time.

Current and Energy in Inductors

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- **Current and Energy in Inductors**
- Magnetic Energy Density

LC - Oscillator

- Power is the rate of change of Energy per time.

$$P_L = L I \frac{dI}{dt} = \frac{dU}{dt}$$

Current and Energy in Inductors

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- **Current and Energy in Inductors**
- Magnetic Energy Density

LC - Oscillator

- Power is the rate of change of Energy per time.

$$P_L = L I \frac{dI}{dt} = \frac{dU}{dt}$$
$$\Rightarrow dU_L = L I dI$$

Current and Energy in Inductors

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- **Current and Energy in Inductors**
- Magnetic Energy Density

LC - Oscillator

- Power is the rate of change of Energy per time.

$$P_L = L I \frac{dI}{dt} = \frac{dU}{dt}$$

$$\Rightarrow dU_L = L I dI$$

$$\Rightarrow U_L = \int L I dI = \frac{1}{2} L I^2$$

Current and Energy in Inductors

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- **Current and Energy in Inductors**
- Magnetic Energy Density

LC - Oscillator

- Power is the rate of change of Energy per time.

$$P_L = L I \frac{dI}{dt} = \frac{dU}{dt}$$

$$\Rightarrow dU_L = L I dI$$

$$\Rightarrow U_L = \int L I dI = \frac{1}{2} L I^2$$

- The energy stored in the inductor varies as I^2

Current and Energy in Inductors

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- **Current and Energy in Inductors**
- Magnetic Energy Density

LC - Oscillator

- Power is the rate of change of Energy per time.

$$P_L = L I \frac{dI}{dt} = \frac{dU}{dt}$$

$$\Rightarrow dU_L = L I dI$$

$$\Rightarrow U_L = \int L I dI = \frac{1}{2} L I^2$$

- The energy stored in the inductor varies as I^2 (much like Q^2 for a capacitor).

Current and Energy in Inductors

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- **Current and Energy in Inductors**
- Magnetic Energy Density

LC - Oscillator

- Power is the rate of change of Energy per time.

$$P_L = L I \frac{dI}{dt} = \frac{dU}{dt}$$

$$\Rightarrow dU_L = L I dI$$

$$\Rightarrow U_L = \int L I dI = \frac{1}{2} L I^2$$

- The energy stored in the inductor varies as I^2 (much like Q^2 for a capacitor).
- Is there a general expression that does not depend on the self-inductance?

Current and Energy in Inductors

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- **Current and Energy in Inductors**
- Magnetic Energy Density

LC - Oscillator

- Power is the rate of change of Energy per time.

$$P_L = L I \frac{dI}{dt} = \frac{dU}{dt}$$

$$\Rightarrow dU_L = L I dI$$

$$\Rightarrow U_L = \int L I dI = \frac{1}{2} L I^2$$

- The energy stored in the inductor varies as I^2 (much like Q^2 for a capacitor).
- Is there a general expression that does not depend on the self-inductance? In other words, is there a relationship between the amount of energy and the magnetic field?

Magnetic Energy Density

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- **Magnetic Energy Density**

LC - Oscillator

- Consider a solenoid with radius a , length l , and n number of turns per unit length.

Magnetic Energy Density

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- **Magnetic Energy Density**

LC - Oscillator

- Consider a solenoid with radius a , length l , and n number of turns per unit length.

$$B = \mu_0 n I$$

Magnetic Energy Density

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- **Magnetic Energy Density**

LC - Oscillator

- Consider a solenoid with radius a , length l , and n number of turns per unit length.

$$B = \mu_0 n I$$

$$L = n^2 \mu_0 l (\pi a^2)$$

Magnetic Energy Density

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- **Magnetic Energy Density**

LC - Oscillator

- Consider a solenoid with radius a , length l , and n number of turns per unit length.

$$B = \mu_0 n I$$

$$L = n^2 \mu_0 l (\pi a^2) = n^2 \mu_0 (A l)$$

Magnetic Energy Density

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- **Magnetic Energy Density**

LC - Oscillator

- Consider a solenoid with radius a , length l , and n number of turns per unit length.

$$B = \mu_0 n I$$

$$L = n^2 \mu_0 l (\pi a^2) = n^2 \mu_0 (A l)$$

$$\Rightarrow U_B = \frac{1}{2} L I^2$$

Magnetic Energy Density

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- **Magnetic Energy Density**

LC - Oscillator

- Consider a solenoid with radius a , length l , and n number of turns per unit length.

$$B = \mu_0 n I$$

$$L = n^2 \mu_0 l (\pi a^2) = n^2 \mu_0 (A l)$$

$$\Rightarrow U_B = \frac{1}{2} L I^2 = \frac{1}{2} n^2 \mu_0 (A l) \left(\frac{B}{\mu_0 n} \right)^2$$

Magnetic Energy Density

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- **Magnetic Energy Density**

LC - Oscillator

- Consider a solenoid with radius a , length l , and n number of turns per unit length.

$$B = \mu_0 n I$$

$$L = n^2 \mu_0 l (\pi a^2) = n^2 \mu_0 (A l)$$

$$\Rightarrow U_B = \frac{1}{2} L I^2 = \frac{1}{2} n^2 \mu_0 (A l) \left(\frac{B}{\mu_0 n} \right)^2$$

$$\Rightarrow U_B = \frac{1}{2 \mu_0} B^2 (A l)$$

Magnetic Energy Density

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- **Magnetic Energy Density**

LC - Oscillator

- Consider a solenoid with radius a , length l , and n number of turns per unit length.

$$B = \mu_0 n I$$

$$L = n^2 \mu_0 l (\pi a^2) = n^2 \mu_0 (A l)$$

$$\Rightarrow U_B = \frac{1}{2} L I^2 = \frac{1}{2} n^2 \mu_0 (A l) \left(\frac{B}{\mu_0 n} \right)^2$$

$$\Rightarrow U_B = \frac{1}{2 \mu_0} B^2 (A l)$$

- $(A l)$ is the volume where the magnetic field exists.

Magnetic Energy Density

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- **Magnetic Energy Density**

LC - Oscillator

- Consider a solenoid with radius a , length l , and n number of turns per unit length.

$$B = \mu_0 n I$$

$$L = n^2 \mu_0 l (\pi a^2) = n^2 \mu_0 (A l)$$

$$\Rightarrow U_B = \frac{1}{2} L I^2 = \frac{1}{2} n^2 \mu_0 (A l) \left(\frac{B}{\mu_0 n} \right)^2$$

$$\Rightarrow U_B = \frac{1}{2 \mu_0} B^2 (A l)$$

- $(A l)$ is the volume where the magnetic field exists. Think energy per volume.

Magnetic Energy Density

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

- Energy Stored in Inductors
- Current and Energy in Inductors
- **Magnetic Energy Density**

LC - Oscillator

- Consider a solenoid with radius a , length l , and n number of turns per unit length.

$$B = \mu_0 n I$$

$$L = n^2 \mu_0 l (\pi a^2) = n^2 \mu_0 (A l)$$

$$\Rightarrow U_B = \frac{1}{2} L I^2 = \frac{1}{2} n^2 \mu_0 (A l) \left(\frac{B}{\mu_0 n} \right)^2$$

$$\Rightarrow U_B = \frac{1}{2 \mu_0} B^2 (A l)$$

- $(A l)$ is the volume where the magnetic field exists. Think energy per volume.

$$u_B = U_B / V = \frac{B^2}{2 \mu_0}$$

Energy Oscillations

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

- **Energy Oscillations**
- LC - Circuit
- Charge Oscillations

- Since capacitors store electrical energy and inductors store magnetic energy, we could place a fully charged capacitor in series with an inductor.

Energy Oscillations

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

- **Energy Oscillations**
- LC - Circuit
- Charge Oscillations

- Since capacitors store electrical energy and inductors store magnetic energy, we could place a fully charged capacitor in series with an inductor.
- The electrical energy should be transferred to magnetic energy

Energy Oscillations

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

- **Energy Oscillations**
- LC - Circuit
- Charge Oscillations

- Since capacitors store electrical energy and inductors store magnetic energy, we could place a fully charged capacitor in series with an inductor.
- The electrical energy should be transferred to magnetic energy ,and then the magnetic energy should get transferred back into electrical energy.

Energy Oscillations

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

- **Energy Oscillations**
- LC - Circuit
- Charge Oscillations

- Since capacitors store electrical energy and inductors store magnetic energy, we could place a fully charged capacitor in series with an inductor.
- The electrical energy should be transferred to magnetic energy, and then the magnetic energy should get transferred back into electrical energy. This cycle should repeat itself.

Energy Oscillations

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

- **Energy Oscillations**
- LC - Circuit
- Charge Oscillations

- Since capacitors store electrical energy and inductors store magnetic energy, we could place a fully charged capacitor in series with an inductor.
- The electrical energy should be transferred to magnetic energy ,and then the magnetic energy should get transferred back into electrical energy. This cycle should repeat itself. Let's prove it.

Energy Oscillations

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

- **Energy Oscillations**
- LC - Circuit
- Charge Oscillations

- Since capacitors store electrical energy and inductors store magnetic energy, we could place a fully charged capacitor in series with an inductor.
- The electrical energy should be transferred to magnetic energy, and then the magnetic energy should get transferred back into electrical energy. This cycle should repeat itself. Let's prove it.
- Since energy stored in a capacitor is proportional to Q^2 , it suffices to prove that the charge on the capacitor "oscillate".


LC - Circuit

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

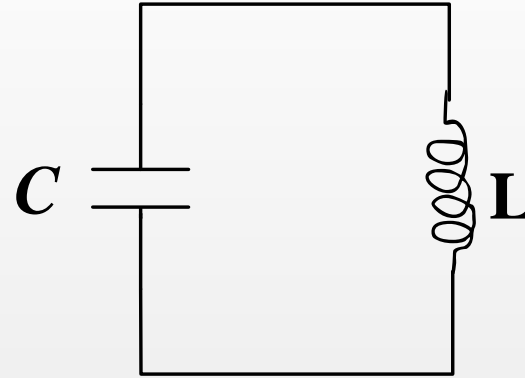- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations



- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.


LC - Circuit

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

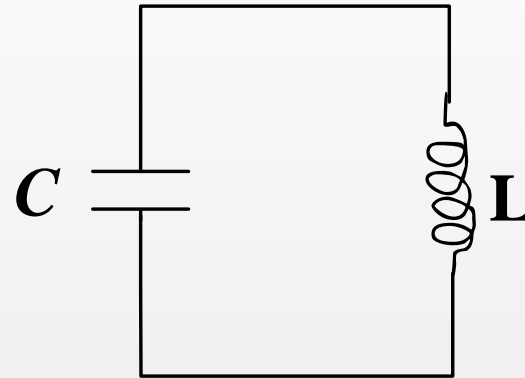- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations



- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.
- Write down the total energy of the system at some time t after the capacitor is connected to the inductor.


LC - Circuit

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

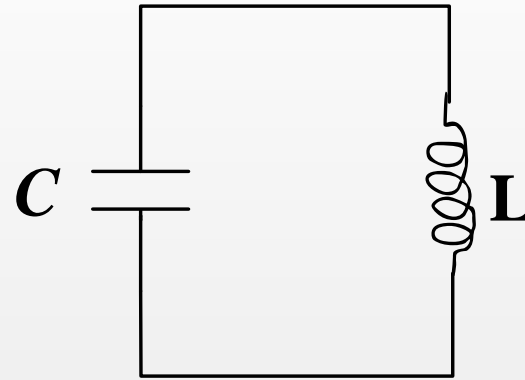- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations



- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.
- Write down the total energy of the system at some time t after the capacitor is connected to the inductor.

$$U_T = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L I^2$$


LC - Circuit

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

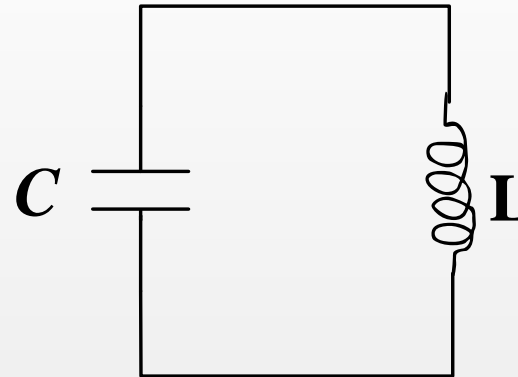- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations



- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.
- Write down the total energy of the system at some time t after the capacitor is connected to the inductor.

$$U_T = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L I^2$$
$$\frac{dU_T}{dt}$$


LC - Circuit

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

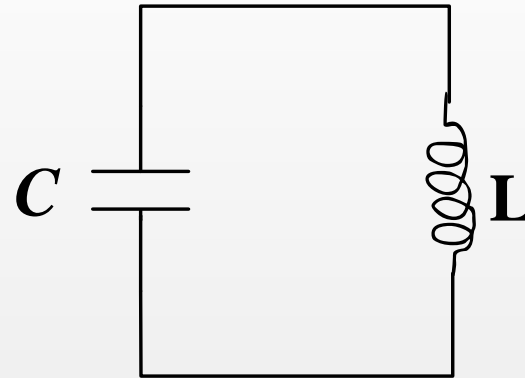- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations



- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.
- Write down the total energy of the system at some time t after the capacitor is connected to the inductor.

$$U_T = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L I^2$$
$$\frac{dU_T}{dt} = 0$$


LC - Circuit

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

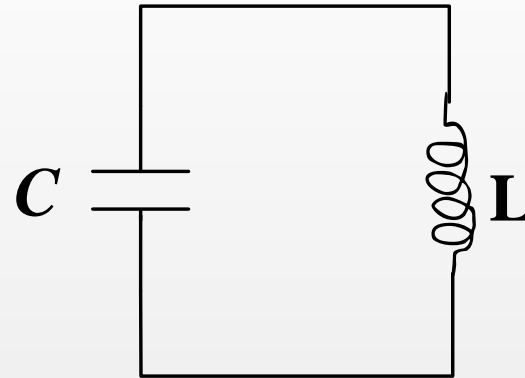- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations



- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.
- Write down the total energy of the system at some time t after the capacitor is connected to the inductor.

$$U_T = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L I^2$$
$$\frac{dU_T}{dt} = 0 = \frac{Q}{C} \frac{dQ}{dt}$$


LC - Circuit

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

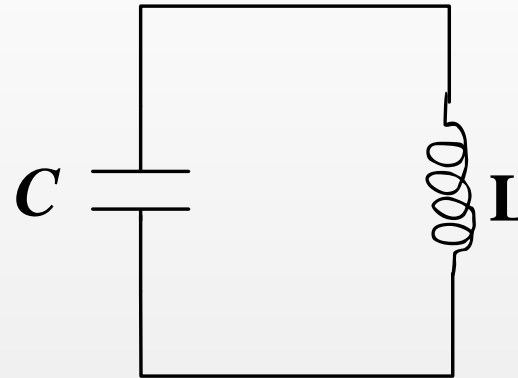- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations



- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.
- Write down the total energy of the system at some time t after the capacitor is connected to the inductor.

$$U_T = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L I^2$$

$$\frac{dU_T}{dt} = 0 = \frac{Q}{C} \frac{dQ}{dt} + L I \frac{dI}{dt}$$


LC - Circuit

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

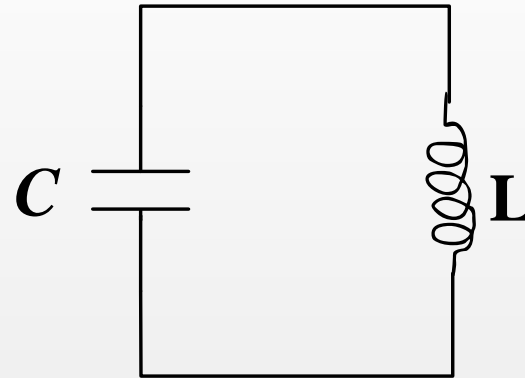- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations



- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.
- Write down the total energy of the system at some time t after the capacitor is connected to the inductor.

$$U_T = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L I^2$$

$$\frac{dU_T}{dt} = 0 = \frac{Q}{C} \frac{dQ}{dt} + L I \frac{dI}{dt}$$

$$0 = \frac{Q}{C} + L \frac{d^2 Q}{dt^2}$$


Charge Oscillations

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

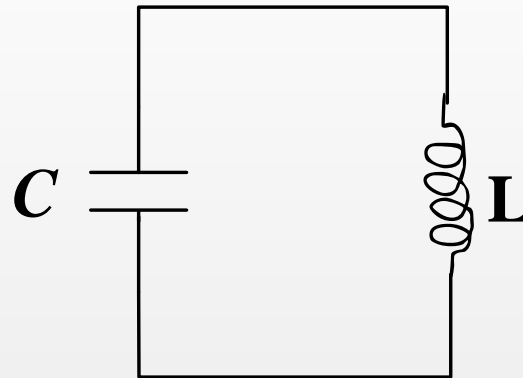- Energy Oscillations
- LC - Circuit
- **Charge Oscillations**



$$\frac{d^2 Q}{dt^2} = -Q/LC = -\omega^2 Q$$


Charge Oscillations

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

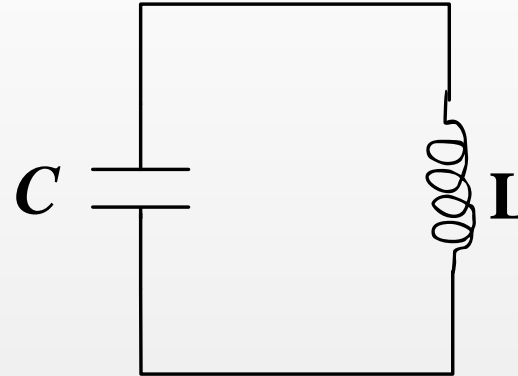- Energy Oscillations
- LC - Circuit
- **Charge Oscillations**



$$\frac{d^2 Q}{dt^2} = -Q/LC = -\omega^2 Q$$

- This equation defines simple harmonic motion with an angular frequency $\omega = \frac{1}{\sqrt{LC}}$.


Charge Oscillations

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

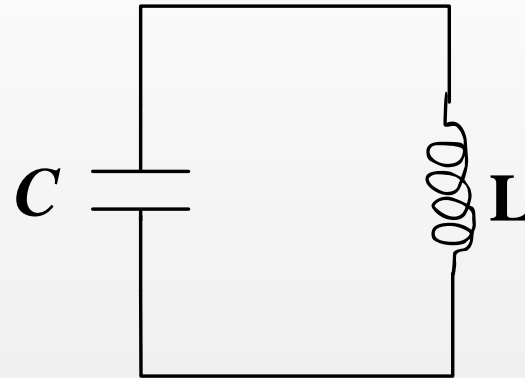- Energy Oscillations
- LC - Circuit
- **Charge Oscillations**



$$\frac{d^2 Q}{dt^2} = -Q/LC = -\omega^2 Q$$

- This equation defines simple harmonic motion with an angular frequency $\omega = \frac{1}{\sqrt{LC}}$. The charge on the capacitor, Q , is undergoing simple harmonic motion.


Charge Oscillations

- LR Circuit - Equation for Current
- Inductive Time Constant
- Current Behavior - Graphing
- Graphing - EMF of Inductor
- Disconnecting the Battery
- Current Decay through LR Circuits
- LR - RC Circuit Comparison

Energy

LC - Oscillator

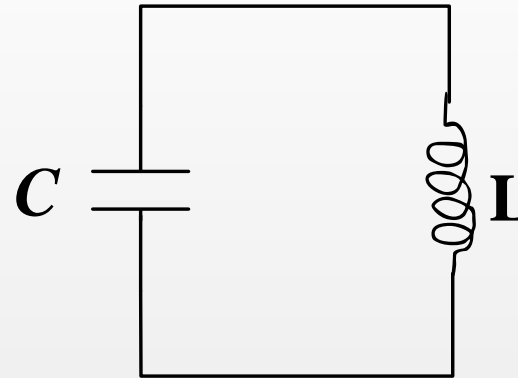- Energy Oscillations
- LC - Circuit
- **Charge Oscillations**



$$\frac{d^2 Q}{dt^2} = -Q/LC = -\omega^2 Q$$

- This equation defines simple harmonic motion with an angular frequency $\omega = \frac{1}{\sqrt{LC}}$. The charge on the capacitor, Q , is undergoing simple harmonic motion.
- From mechanics, we know a solution for $Q(t)$:

$$Q(t) = Q_0 \sin(\omega t + \phi)$$