

PHYS102
AC-Circuits

Dr. Suess

April 16, 2007

Energy Oscillations

LC - Oscillator

- **Energy Oscillations**
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

- Since capacitors store electrical energy and inductors store magnetic energy, we could place a fully charged capacitor in series with an inductor.

Energy Oscillations

LC - Oscillator

- **Energy Oscillations**

- LC - Circuit

- Charge Oscillations

- Effects of Resistance on LC Circuits

- RLC - Damped

- Oscillations

- RLC - DC - Situation

- RLC - AC -

- Introduction

Alternating Current

Circuits

- Since capacitors store electrical energy and inductors store magnetic energy, we could place a fully charged capacitor in series with an inductor.
- The electrical energy should be transferred to magnetic energy

Energy Oscillations

LC - Oscillator

- **Energy Oscillations**

- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

- Since capacitors store electrical energy and inductors store magnetic energy, we could place a fully charged capacitor in series with an inductor.
- The electrical energy should be transferred to magnetic energy ,and then the magnetic energy should get transferred back into electrical energy.

Energy Oscillations

LC - Oscillator

- **Energy Oscillations**

- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

- Since capacitors store electrical energy and inductors store magnetic energy, we could place a fully charged capacitor in series with an inductor.
- The electrical energy should be transferred to magnetic energy ,and then the magnetic energy should get transferred back into electrical energy. This cycle should repeat itself.

Energy Oscillations

LC - Oscillator

- **Energy Oscillations**

- LC - Circuit

- Charge Oscillations

- Effects of Resistance on LC Circuits

- RLC - Damped

- Oscillations

- RLC - DC - Situation

- RLC - AC -

- Introduction

Alternating Current

Circuits

- Since capacitors store electrical energy and inductors store magnetic energy, we could place a fully charged capacitor in series with an inductor.
- The electrical energy should be transferred to magnetic energy ,and then the magnetic energy should get transferred back into electrical energy. This cycle should repeat itself. Let's prove it.

Energy Oscillations

LC - Oscillator

- **Energy Oscillations**

- LC - Circuit

- Charge Oscillations

- Effects of Resistance on LC Circuits

- RLC - Damped

- Oscillations

- RLC - DC - Situation

- RLC - AC -

- Introduction

Alternating Current Circuits


- Since capacitors store electrical energy and inductors store magnetic energy, we could place a fully charged capacitor in series with an inductor.
- The electrical energy should be transferred to magnetic energy ,and then the magnetic energy should get transferred back into electrical energy. This cycle should repeat itself. Let's prove it.
- Since energy stored in a capacitor is proportional to Q^2 , it suffices to prove that the charge on the capacitor “oscillate”.

LC - Circuit

LC - Oscillator

- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

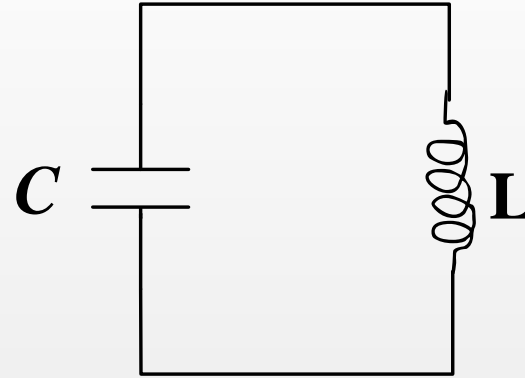


- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.

LC - Circuit

LC - Oscillator

- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

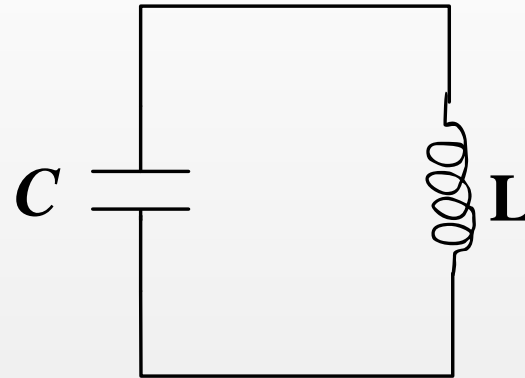


- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.
- Write down the total energy of the system at some time t after the capacitor is connected to the inductor.

LC - Circuit

LC - Oscillator

- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

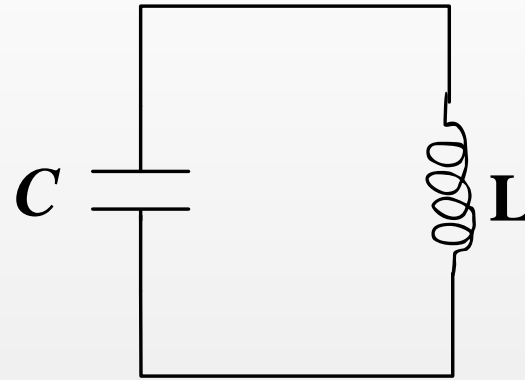

- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.
- Write down the total energy of the system at some time t after the capacitor is connected to the inductor.


$$U_T = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L I^2$$

LC - Circuit

LC - Oscillator

- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

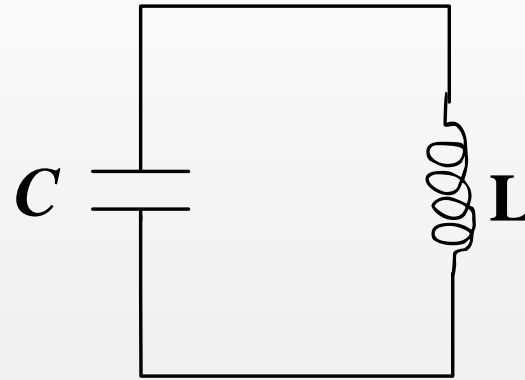

- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.
- Write down the total energy of the system at some time t after the capacitor is connected to the inductor.


$$U_T = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L I^2$$
$$\frac{dU_T}{dt}$$

LC - Circuit

LC - Oscillator

- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

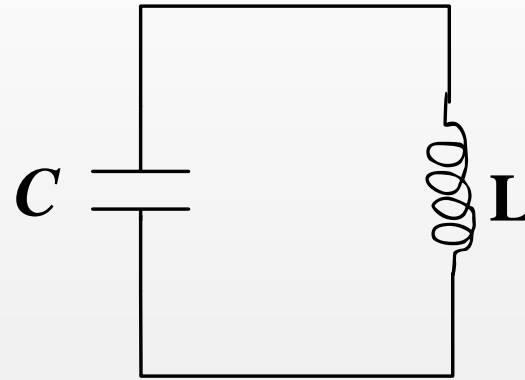

- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.
- Write down the total energy of the system at some time t after the capacitor is connected to the inductor.


$$U_T = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L I^2$$
$$\frac{dU_T}{dt} = 0$$

LC - Circuit

LC - Oscillator

- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

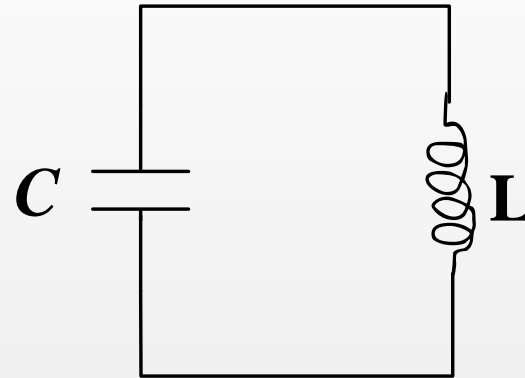

- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.
- Write down the total energy of the system at some time t after the capacitor is connected to the inductor.


$$U_T = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L I^2$$
$$\frac{dU_T}{dt} = 0 = \frac{Q}{C} \frac{dQ}{dt}$$

LC - Circuit

LC - Oscillator

- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

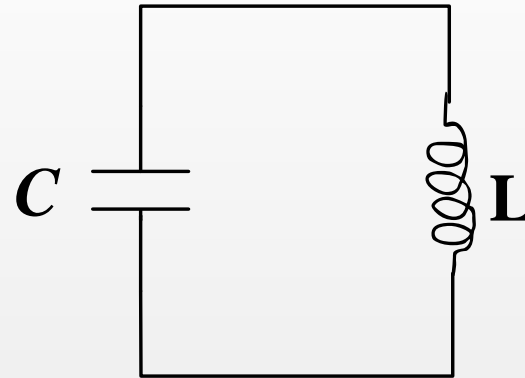

- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.
- Write down the total energy of the system at some time t after the capacitor is connected to the inductor.

$$U_T = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L I^2$$


$$\frac{dU_T}{dt} = 0 = \frac{Q}{C} \frac{dQ}{dt} + L I \frac{dI}{dt}$$

LC - Circuit

LC - Oscillator

- Energy Oscillations
- **LC - Circuit**
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

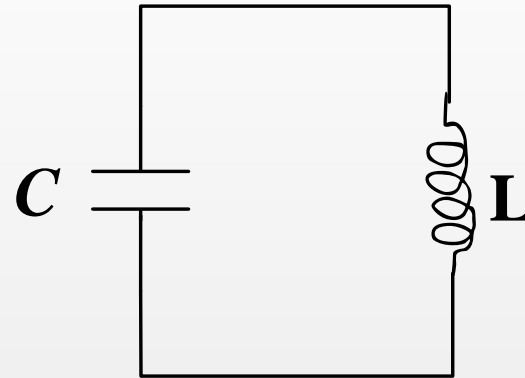

- Start with a *fully charged capacitor* and place it in series with an inductor as shown above.
- Write down the total energy of the system at some time t after the capacitor is connected to the inductor.

$$U_T = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L I^2$$

$$\frac{dU_T}{dt} = 0 = \frac{Q}{C} \frac{dQ}{dt} + L I \frac{dI}{dt}$$


$$0 = \frac{Q}{C} + L \frac{d^2 Q}{dt^2}$$

Charge Oscillations

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- **Charge Oscillations**
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

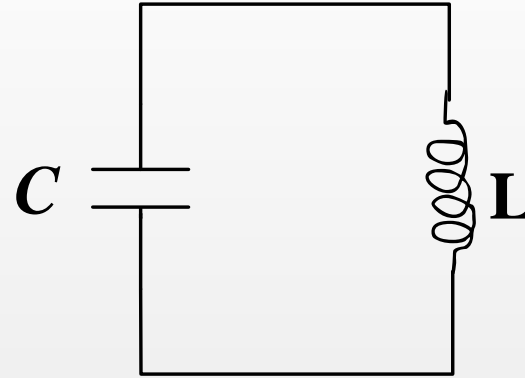


$$\frac{d^2 Q}{dt^2} = -Q/LC = -\omega^2 Q$$

Charge Oscillations

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- **Charge Oscillations**
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

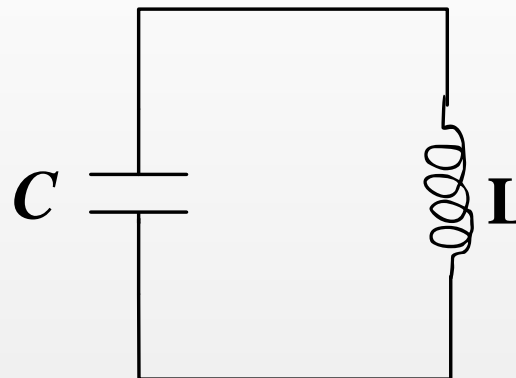

$$\frac{d^2 Q}{dt^2} = -Q/LC = -\omega^2 Q$$


- This equation defines simple harmonic motion with an angular frequency $\omega = \frac{1}{\sqrt{LC}}$.

Charge Oscillations

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- **Charge Oscillations**
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

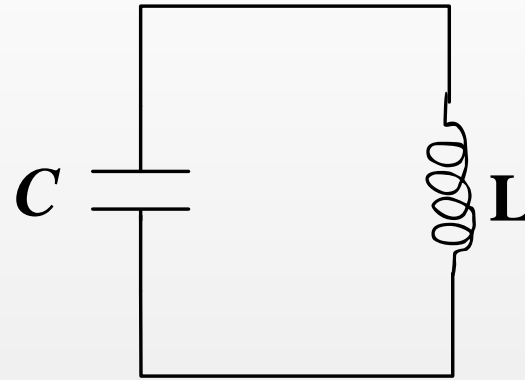

$$\frac{d^2 Q}{dt^2} = -Q/LC = -\omega^2 Q$$


- This equation defines simple harmonic motion with an angular frequency $\omega = \frac{1}{\sqrt{LC}}$. The charge on the capacitor, Q , is undergoing simple harmonic motion.

Charge Oscillations

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- **Charge Oscillations**
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

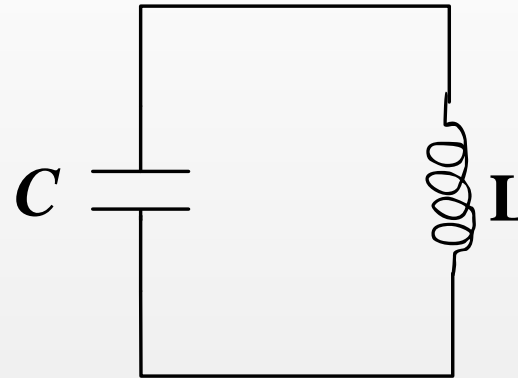

$$\frac{d^2 Q}{dt^2} = -Q/LC = -\omega^2 Q$$

- This equation defines simple harmonic motion with an angular frequency $\omega = \frac{1}{\sqrt{LC}}$. The charge on the capacitor, Q , is undergoing simple harmonic motion.
- From mechanics, we know a solution for $Q(t)$:


$$Q(t) = Q_0 \sin(\omega t + \phi)$$

Effects of Resistance on LC Circuits

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- **Effects of Resistance on LC Circuits**
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

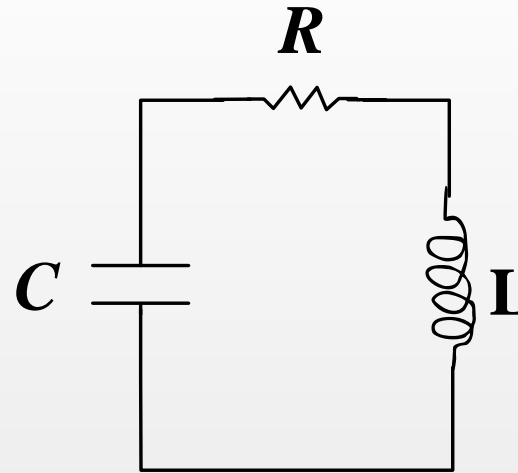


Effects of Resistance on LC Circuits

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

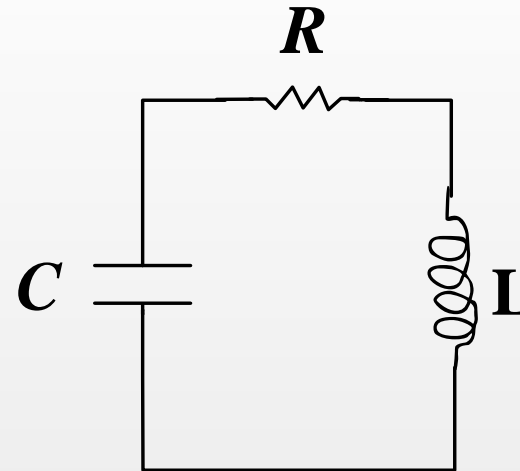


- The charge on the capacitor, Q , will undergo simple harmonic motion when the capacitor is directly connected across an inductor.

Effects of Resistance on LC Circuits

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

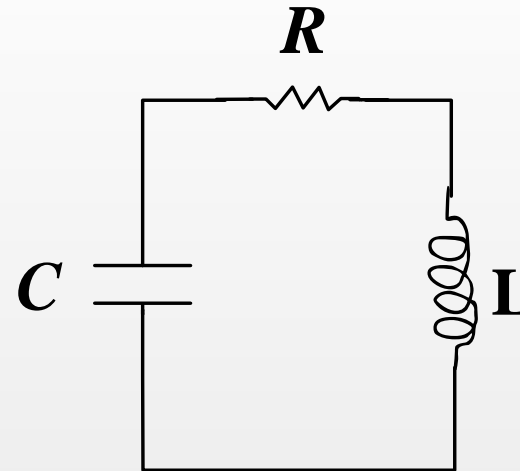


- The charge on the capacitor, Q , will undergo simple harmonic motion when the capacitor is directly connected across an inductor.
- What if we were to consider the finite resistance R of the wires connecting the inductor and the capacitor?

Effects of Resistance on LC Circuits

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

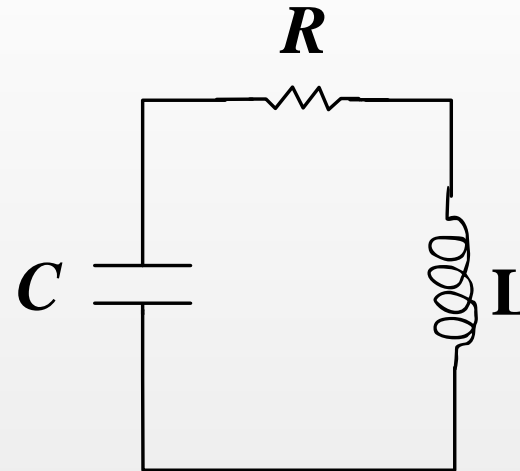


- The charge on the capacitor, Q , will undergo simple harmonic motion when the capacitor is directly connected across an inductor.
- What if we were to consider the finite resistance R of the wires connecting the inductor and the capacitor?
 - What would happen to the period of oscillation?

Effects of Resistance on LC Circuits

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

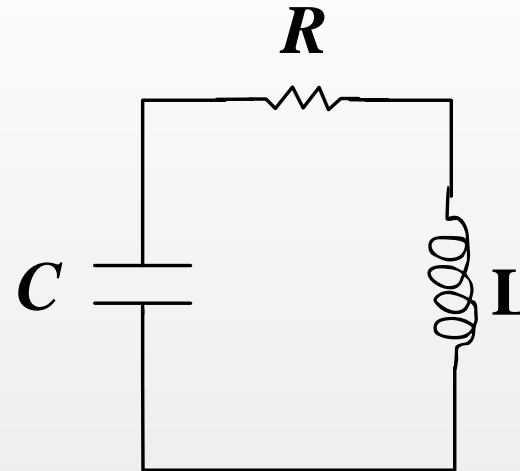


- The charge on the capacitor, Q , will undergo simple harmonic motion when the capacitor is directly connected across an inductor.
- What if we were to consider the finite resistance R of the wires connecting the inductor and the capacitor?
 - What would happen to the period of oscillation?
 - What would happen to the current in the circuit after a very long time?

RLC - Damped Oscillations

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- **RLC - Damped Oscillations**
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

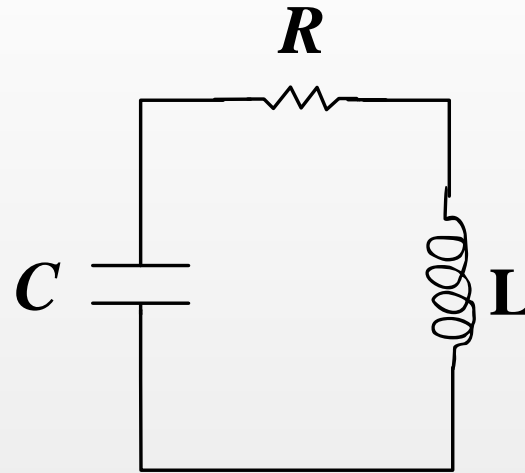


RLC - Damped Oscillations

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- **RLC - Damped Oscillations**
- RLC - DC - Situation
- RLC - AC -

Introduction

Alternating Current Circuits

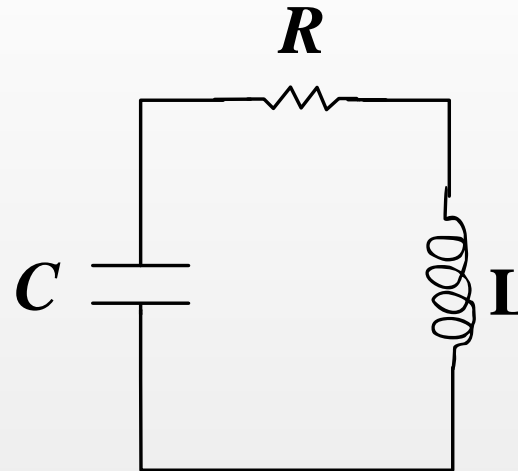

- The overall behavior of the charge oscillation will be affected because the resistance of the wire will cause energy loss (due to heating).


RLC - Damped Oscillations

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- **RLC - Damped Oscillations**
- RLC - DC - Situation
- RLC - AC -

Introduction

Alternating Current Circuits

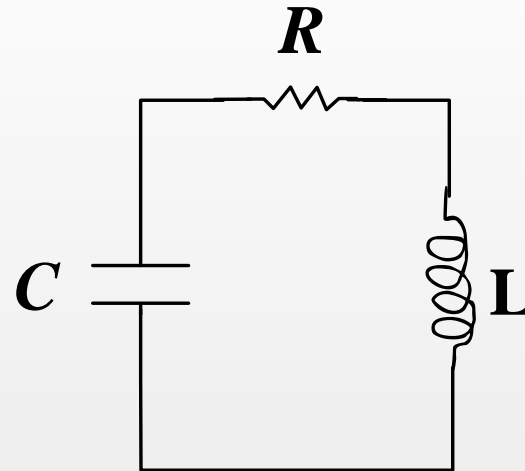

- The overall behavior of the charge oscillation will be affected because the resistance of the wire will cause energy loss (due to heating). The larger the resistance, the faster energy gets dissipated (and the longer the period of oscillation becomes).


RLC - Damped Oscillations

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- **RLC - Damped Oscillations**
- RLC - DC - Situation
- RLC - AC -

Introduction

Alternating Current Circuits

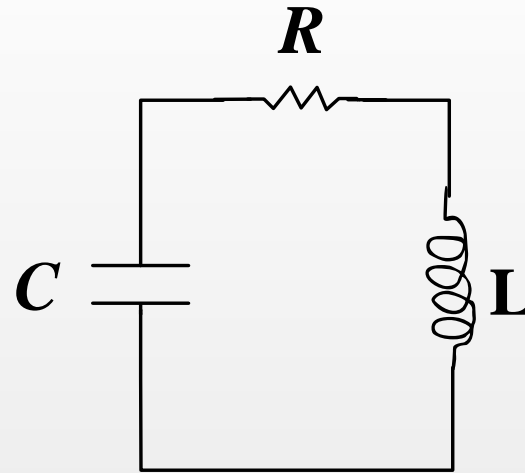

- The overall behavior of the charge oscillation will be affected because the resistance of the wire will cause energy loss (due to heating). The larger the resistance, the faster energy gets dissipated (and the longer the period of oscillation becomes).

$$P_R = I^2 R$$


RLC - Damped Oscillations

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC -

Introduction

Alternating Current Circuits

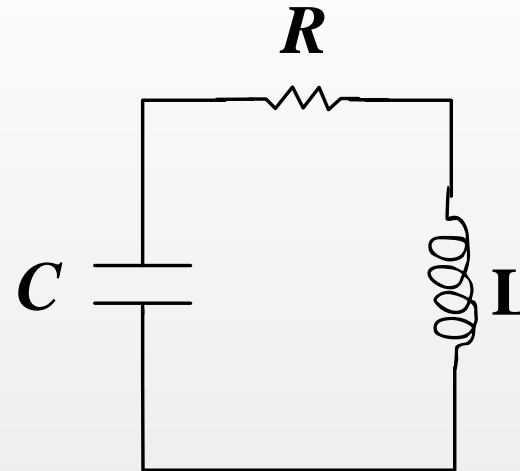

- The overall behavior of the charge oscillation will be affected because the resistance of the wire will cause energy loss (due to heating). The larger the resistance, the faster energy gets dissipated (and the longer the period of oscillation becomes).

$$P_R = I^2 R$$


- Since the charge (or current) oscillations decrease over time, this type of oscillation behavior is termed a “*damped oscillation*”.

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- **RLC - DC - Situation**
- RLC - AC - Introduction

Alternating Current Circuits

RLC - DC - Situation

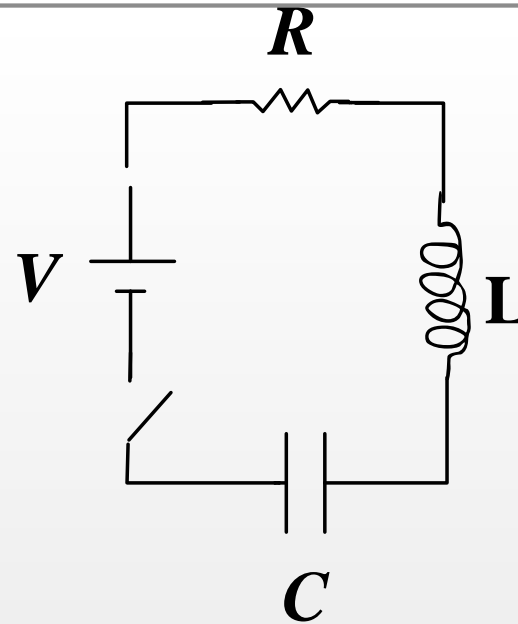

- What would happen if we connected a battery, a resistor, an inductor, and a capacitor in series with a switch?

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations


● RLC - DC - Situation

- RLC - AC -

Introduction

Alternating Current Circuits

RLC - DC - Situation

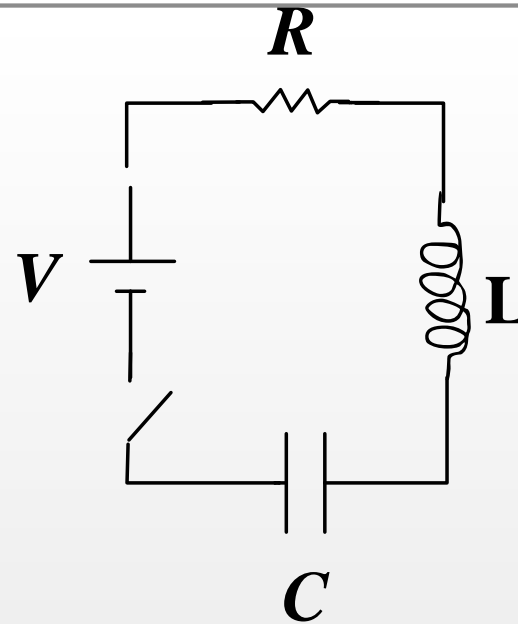

- What would happen if we connected a battery, a resistor, an inductor, and a capacitor in series with a switch?
- There would be NO current at the moment the switch is closed (WHY?)

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations


● RLC - DC - Situation

- RLC - AC -

Introduction

Alternating Current Circuits

RLC - DC - Situation

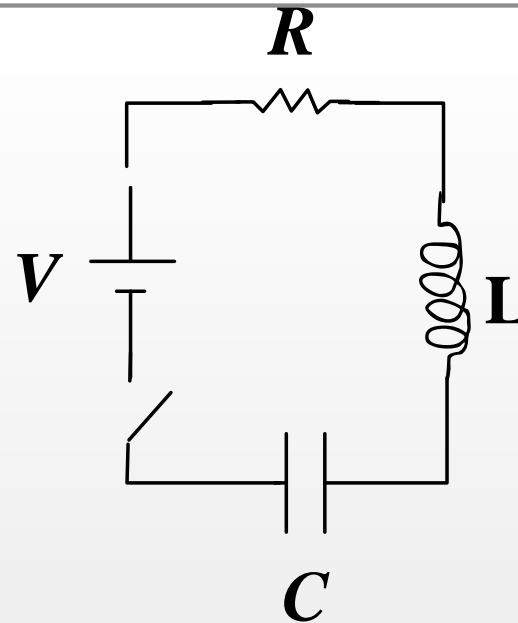

- What would happen if we connected a battery, a resistor, an inductor, and a capacitor in series with a switch?
- There would be NO current at the moment the switch is closed (WHY?) and the current would be zero after a very long time after the switch is closed (WHY?).

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations


● RLC - DC - Situation

- RLC - AC -

Introduction

Alternating Current Circuits

RLC - DC - Situation

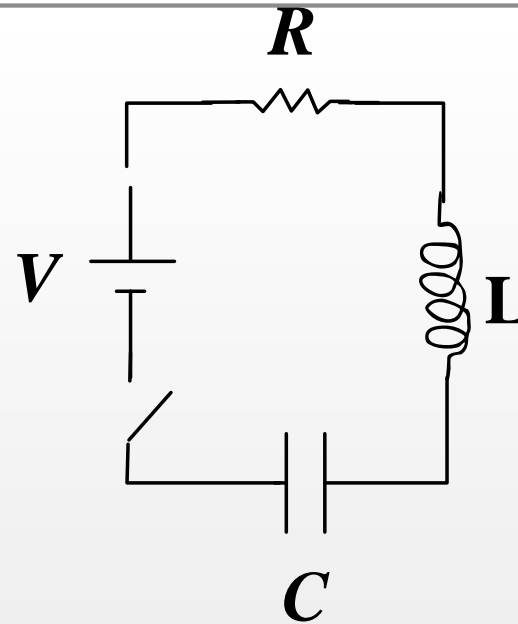

- What would happen if we connected a battery, a resistor, an inductor, and a capacitor in series with a switch?
- There would be NO current at the moment the switch is closed (WHY?) and the current would be zero after a very long time after the switch is closed (WHY?).
- Not very interesting is it.

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations


● RLC - DC - Situation

- RLC - AC -

Introduction

Alternating Current Circuits

RLC - DC - Situation

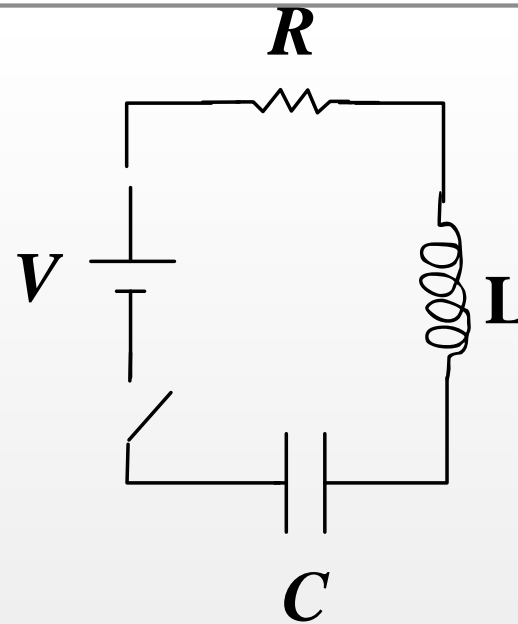


- What would happen if we connected a battery, a resistor, an inductor, and a capacitor in series with a switch?
- There would be NO current at the moment the switch is closed (WHY?) and the current would be zero after a very long time after the switch is closed (WHY?).
- Not very interesting is it.

RLC - AC - Introduction

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

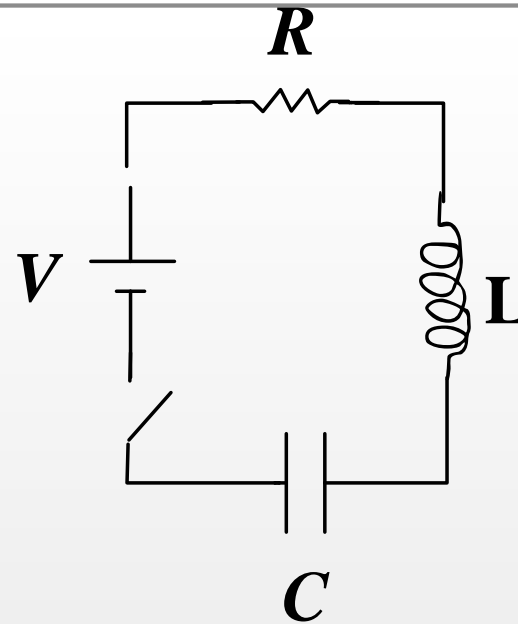


- What if we connected the inductor, capacitor, and resistor in series with a time varying voltage source (like the wall socket in this room)?

RLC - AC - Introduction

LC - Oscillator

- Energy Oscillations
- LC - Circuit
- Charge Oscillations
- Effects of Resistance on LC Circuits
- RLC - Damped Oscillations
- RLC - DC - Situation
- RLC - AC - Introduction

Alternating Current Circuits

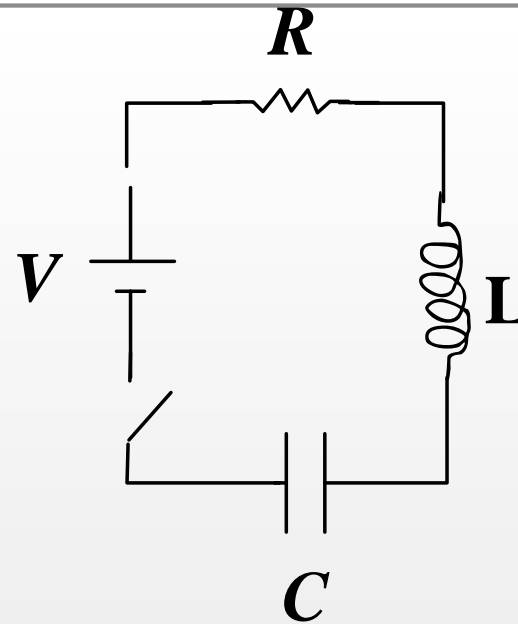

- What if we connected the inductor, capacitor, and resistor in series with a time varying voltage source (like the wall socket in this room)?
- I would say that we need to understand the behavior of each component individually under a time varying voltage.

Introduction

LC - Oscillator

Alternating Current
Circuits

- **Introduction**
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- So far all of the circuits mentioned in this course have been **Direct Current (DC)** circuits.

Introduction

LC - Oscillator

Alternating Current
Circuits

- **Introduction**
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- So far all of the circuits mentioned in this course have been **Direct Current (DC)** circuits.
- **Alternating Current (AC)** circuits are circuits that have time varying currents.

Introduction

LC - Oscillator

Alternating Current
Circuits

- **Introduction**
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- So far all of the circuits mentioned in this course have been **Direct Current (DC)** circuits.
- **Alternating Current (AC)** circuits are circuits that have time varying currents.
- Time varying currents are produced by time varying voltage sources.

Introduction

LC - Oscillator

Alternating Current
Circuits

- **Introduction**
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- So far all of the circuits mentioned in this course have been **Direct Current (DC)** circuits.
- **Alternating Current (AC)** circuits are circuits that have time varying currents.
- Time varying currents are produced by time varying voltage sources.
- We use a new symbol to indicate time varying voltages.

Introduction

LC - Oscillator

Alternating Current
Circuits

- **Introduction**
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- So far all of the circuits mentioned in this course have been **Direct Current (DC)** circuits.
- **Alternating Current (AC)** circuits are circuits that have time varying currents.
- Time varying currents are produced by time varying voltage sources.
- We use a new symbol to indicate time varying voltages.



Time Varying Voltages

LC - Oscillator

Alternating Current
Circuits

- Introduction
- **Time Varying Voltages**
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- We will restrict discussion to sinusoidally varying voltages of the form

Time Varying Voltages

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- We will restrict discussion to sinusoidally varying voltages of the form

$$V(t) = V_P \sin(\omega t + \phi)$$

Time Varying Voltages

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- We will restrict discussion to sinusoidally varying voltages of the form

$$V(t) = V_P \sin(\omega t + \phi)$$

where V_P is the “peak” voltage (amplitude), ω is the angular frequency, and ϕ is the phase.


Time Varying Voltages and Resistors

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- **Time Varying Voltages and Resistors**
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

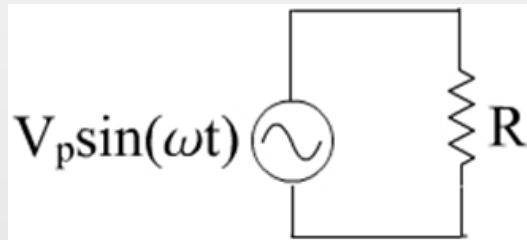- Consider a resistor (R) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.



Time Varying Voltages and Resistors


LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- Consider a resistor (R) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.

- Applying Kirchhoff's rules:

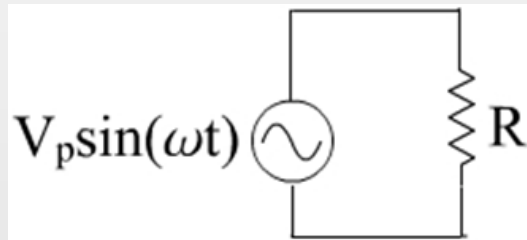

Time Varying Voltages and Resistors


LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- **Time Varying Voltages and Resistors**
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- Consider a resistor (R) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.

- Applying Kirchhoff's rules:

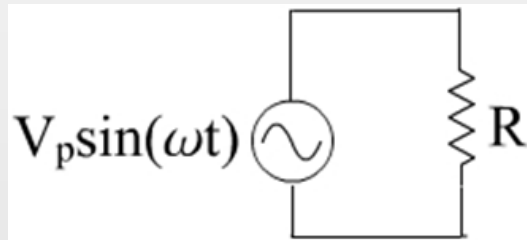

$$V(t) = I(t) R$$

Time Varying Voltages and Resistors


LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- **Time Varying Voltages and Resistors**
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- Consider a resistor (R) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.

- Applying Kirchhoff's rules:

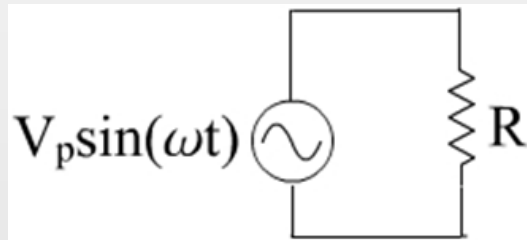

$$V(t) = I(t) R$$

$$I(t) = \frac{V(t)}{R}$$

Time Varying Voltages and Resistors


LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- **Time Varying Voltages and Resistors**
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- Consider a resistor (R) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.

- Applying Kirchhoff's rules:

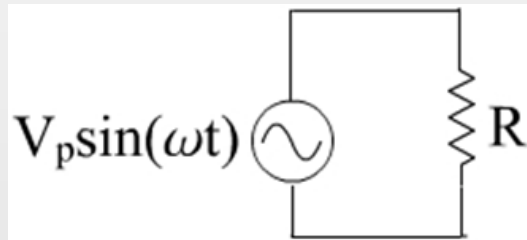

$$V(t) = I(t) R$$

$$I(t) = \frac{V(t)}{R} = \frac{V_P \sin \omega t}{R}$$

Time Varying Voltages and Resistors


LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- **Time Varying Voltages and Resistors**
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- Consider a resistor (R) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.

- Applying Kirchhoff's rules:

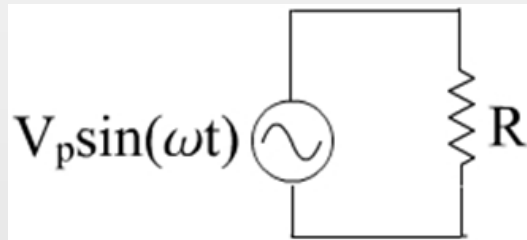

$$V(t) = I(t) R$$

$$I(t) = \frac{V(t)}{R} = \frac{V_P \sin \omega t}{R}$$

- The current through a resistor is “in-phase” with the driving voltage source.


Time Varying Voltages and Capacitors

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- **Time Varying Voltages and Capacitors**
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

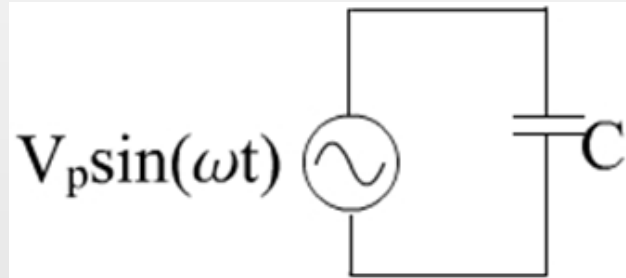- Consider a capacitor (C) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.




Time Varying Voltages and Capacitors

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- **Time Varying Voltages and Capacitors**
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

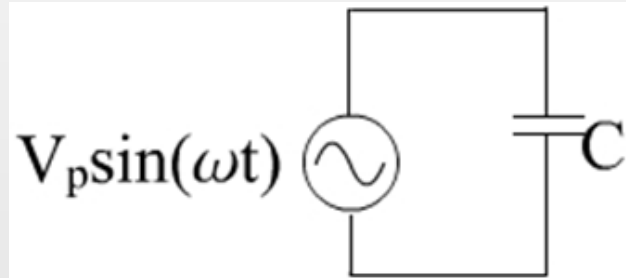- Consider a capacitor (C) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.
 - Let's calculate the current through the capacitor:



Time Varying Voltages and Capacitors


LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- **Time Varying Voltages and Capacitors**
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- Consider a capacitor (C) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.

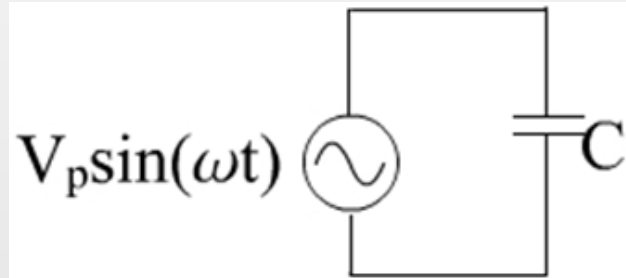- Let's calculate the current through the capacitor:



$$q(t) = C V(t)$$

Time Varying Voltages and Capacitors


LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- **Time Varying Voltages and Capacitors**
- "Out-of-Phase?"
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- Consider a capacitor (C) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.

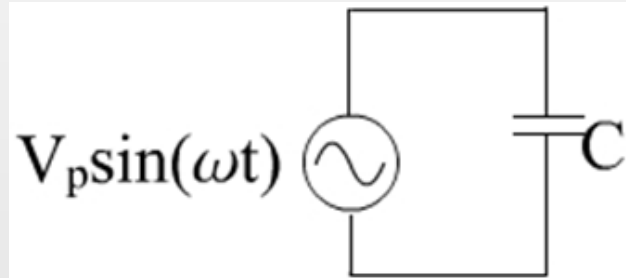- Let's calculate the current through the capacitor:



$$q(t) = C V(t)$$

$$I(t) = \frac{dq}{dt}$$

Time Varying Voltages and Capacitors


LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- **Time Varying Voltages and Capacitors**
- "Out-of-Phase?"
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- Consider a capacitor (C) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.

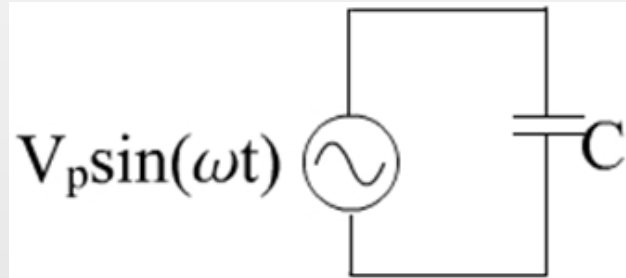- Let's calculate the current through the capacitor:



$$q(t) = C V(t)$$

$$I(t) = \frac{dq}{dt} = C \frac{dV}{dt}$$


Time Varying Voltages and Capacitors

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- **Time Varying Voltages and Capacitors**
- "Out-of-Phase?"
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

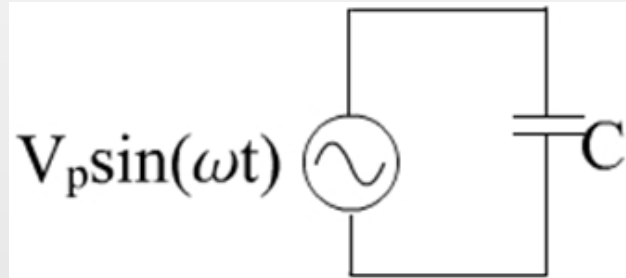- Consider a capacitor (C) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.
 - Let's calculate the current through the capacitor:



$$q(t) = C V(t)$$

$$I(t) = \frac{dq}{dt} = C \frac{dV}{dt}$$

$$I(t) = C \omega V_P \cos \omega t$$

Time Varying Voltages and Capacitors


LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- **Time Varying Voltages and Capacitors**
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- Consider a capacitor (C) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.

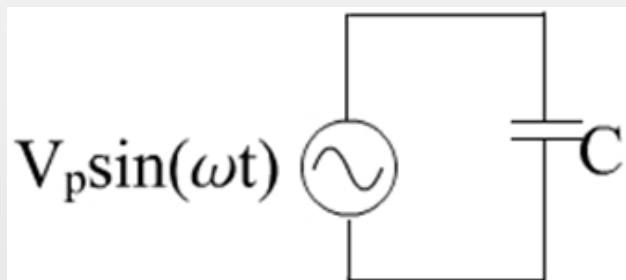- Let's calculate the current through the capacitor:



$$q(t) = C V(t)$$

$$I(t) = \frac{dq}{dt} = C \frac{dV}{dt}$$

$$I(t) = C \omega V_P \cos \omega t$$

- The current through a capacitor is “out-of-phase” with the driving voltage source.

“Out-of-Phase?”

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The time dependent voltage was given by

“Out-of-Phase?”

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The time dependent voltage was given by

$$V(t) = V_P \sin \omega t$$

“Out-of-Phase?”

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The time dependent voltage was given by

$$V(t) = V_P \sin \omega t$$

- The current through the capacitor is given by

“Out-of-Phase?”

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The time dependent voltage was given by

$$V(t) = V_P \sin \omega t$$

- The current through the capacitor is given by

$$I(t) = C \omega V_P \cos \omega t$$

“Out-of-Phase?”

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The time dependent voltage was given by

$$V(t) = V_P \sin \omega t$$

- The current through the capacitor is given by

$$I(t) = C \omega V_P \cos \omega t$$

- From trigonometry:

“Out-of-Phase?”

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The time dependent voltage was given by

$$V(t) = V_P \sin \omega t$$

- The current through the capacitor is given by

$$I(t) = C \omega V_P \cos \omega t$$

- From trigonometry:

$$\cos \omega t = \sin \left(\omega t + \frac{\pi}{2} \right)$$

“Out-of-Phase?”

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The time dependent voltage was given by

$$V(t) = V_P \sin \omega t$$

- The current through the capacitor is given by

$$I(t) = C \omega V_P \cos \omega t \rightarrow C \omega V_P \sin \left(\omega t + \frac{\pi}{2} \right)$$

- From trigonometry:

$$\cos \omega t = \sin \left(\omega t + \frac{\pi}{2} \right)$$

Capacitive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- **Capacitive Reactance**
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The current through the capacitor is

$$I(t) = C \omega V_P \sin \left(\omega t + \frac{\pi}{2} \right)$$

Capacitive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- **Capacitive Reactance**
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The current through the capacitor is

$$I(t) = C \omega V_P \sin \left(\omega t + \frac{\pi}{2} \right)$$

- The current through the capacitor is $\frac{\pi}{2}$ out of phase with the driving voltage.

Capacitive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- **Capacitive Reactance**
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The current through the capacitor is

$$I(t) = C \omega V_P \sin \left(\omega t + \frac{\pi}{2} \right)$$

- The current through the capacitor is $\frac{\pi}{2}$ out of phase with the driving voltage.
 - Current leads the voltage by 90° .

Capacitive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- **Capacitive Reactance**
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The current through the capacitor is

$$I(t) = C \omega V_P \sin \left(\omega t + \frac{\pi}{2} \right)$$

- The current through the capacitor is $\frac{\pi}{2}$ out of phase with the driving voltage.
 - Current leads the voltage by 90° .
- The peak current through the capacitor is $I_P = C \omega V_P$

Capacitive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- **Capacitive Reactance**
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The current through the capacitor is

$$I(t) = C \omega V_P \sin \left(\omega t + \frac{\pi}{2} \right)$$

- The current through the capacitor is $\frac{\pi}{2}$ out of phase with the driving voltage.
 - Current leads the voltage by 90° .
- The peak current through the capacitor is $I_P = C \omega V_P$
 - This resembles Ohm's Law with $I_P = \frac{V_P}{X_C}$

Capacitive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- **Capacitive Reactance**
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The current through the capacitor is

$$I(t) = C \omega V_P \sin \left(\omega t + \frac{\pi}{2} \right)$$

- The current through the capacitor is $\frac{\pi}{2}$ out of phase with the driving voltage.
 - Current leads the voltage by 90° .
- The peak current through the capacitor is $I_P = C \omega V_P$
 - This resembles Ohm's Law with $I_P = \frac{V_P}{\chi_c}$
 - The term $\chi_c = 1/(C \omega)$ has a unit of Ohm

Capacitive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- **Capacitive Reactance**
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The current through the capacitor is

$$I(t) = C \omega V_P \sin \left(\omega t + \frac{\pi}{2} \right)$$

- The current through the capacitor is $\frac{\pi}{2}$ out of phase with the driving voltage.
 - Current leads the voltage by 90° .
- The peak current through the capacitor is $I_P = C \omega V_P$
 - This resembles Ohm's Law with $I_P = \frac{V_P}{\chi_c}$
 - The term $\chi_c = 1/(C \omega)$ has a unit of Ohm and is called capacitive reactance (χ_c)

Capacitive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- **Capacitive Reactance**
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The current through the capacitor is

$$I(t) = C \omega V_P \sin \left(\omega t + \frac{\pi}{2} \right)$$

- The current through the capacitor is $\frac{\pi}{2}$ out of phase with the driving voltage.
 - Current leads the voltage by 90° .
- The peak current through the capacitor is $I_P = C \omega V_P$
 - This resembles Ohm's Law with $I_P = \frac{V_P}{\chi_c}$
 - The term $\chi_c = 1/(C \omega)$ has a unit of Ohm and is called capacitive reactance (χ_c)

Please note this correction.

Properties of Capacitive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The reactance for a capacitor describes the behavior of a capacitor placed in a circuit with a time-varying voltage source.

Properties of Capacitive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The reactance for a capacitor describes the behavior of a capacitor placed in a circuit with a time-varying voltage source.

$$\chi_c = \frac{1}{C\omega}$$

- When ω is large, χ_c is small so the capacitor offers little “resistance” to current flow.

Properties of Capacitive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The reactance for a capacitor describes the behavior of a capacitor placed in a circuit with a time-varying voltage source.

$$\chi_c = \frac{1}{C\omega}$$

- When ω is large, χ_c is small so the capacitor offers little “resistance” to current flow.
- When ω is small, χ_c is large so the capacitor offers greater “resistance” to current flow.

Properties of Capacitive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The reactance for a capacitor describes the behavior of a capacitor placed in a circuit with a time-varying voltage source.

$$\chi_c = \frac{1}{C\omega}$$

- When ω is large, χ_c is small so the capacitor offers little “resistance” to current flow.
- When ω is small, χ_c is large so the capacitor offers greater “resistance” to current flow.
- χ_c is NOT the same as resistance because NO POWER IS DISSIPATED THROUGH A CAPACITOR.


Time Varying Voltages and Inductors

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- **Time Varying Voltages and Inductors**
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

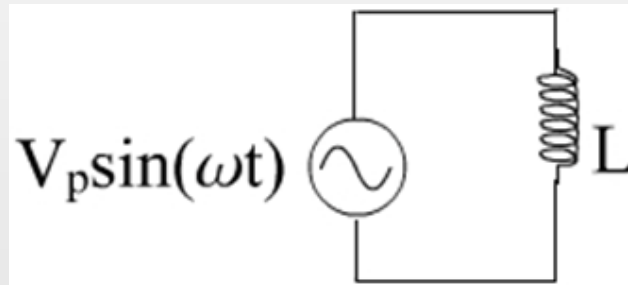- Consider an inductor (L) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.




Time Varying Voltages and Inductors

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- Capacitive Reactance
- Properties of Capacitive Reactance
- **Time Varying Voltages and Inductors**
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

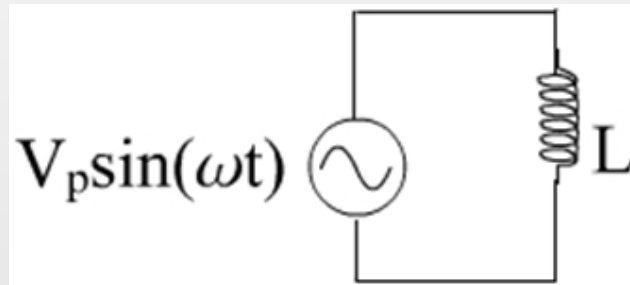- Consider an inductor (L) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.
 - Let's calculate the current through the inductor:



Time Varying Voltages and Inductors


LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- Capacitive Reactance
- Properties of Capacitive Reactance
- **Time Varying Voltages and Inductors**
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- Consider an inductor (L) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.

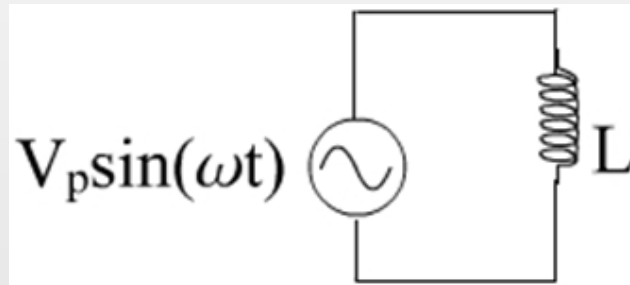- Let's calculate the current through the inductor:



$$V(t) = L \frac{dI}{dt}$$


Time Varying Voltages and Inductors

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- Capacitive Reactance
- Properties of Capacitive Reactance
- **Time Varying Voltages and Inductors**
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

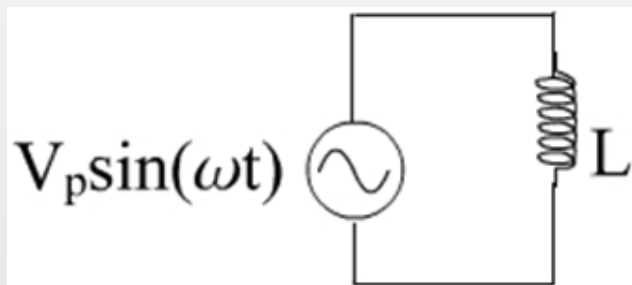- Consider an inductor (L) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.
 - Let's calculate the current through the inductor:



$$V(t) = L \frac{dI}{dt}$$

$$L I(t) = \int V_P \sin \omega t dt$$

Time Varying Voltages and Inductors


LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- Capacitive Reactance
- Properties of Capacitive Reactance
- **Time Varying Voltages and Inductors**
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- Consider an inductor (L) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.

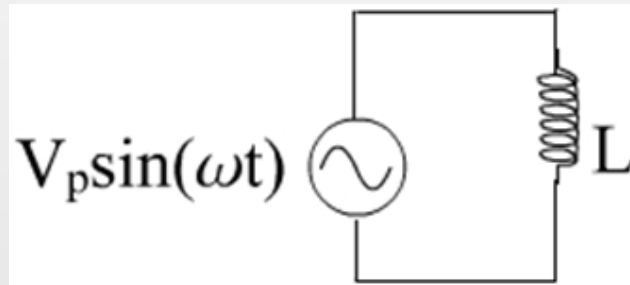- Let's calculate the current through the inductor:



$$V(t) = L \frac{dI}{dt}$$

$$L I(t) = \int V_P \sin \omega t dt$$

$$I(t) = -\frac{V_P}{\omega L} \cos \omega t$$


Time Varying Voltages and Inductors

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- Capacitive Reactance
- Properties of Capacitive Reactance
- **Time Varying Voltages and Inductors**
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

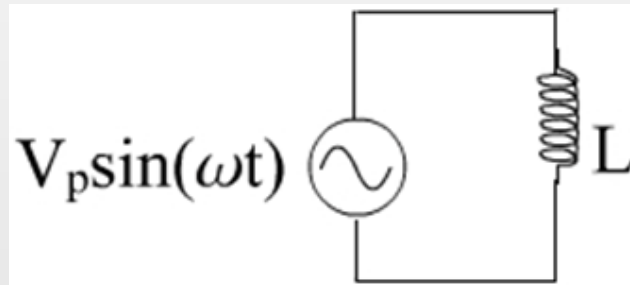- Consider an inductor (L) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.
 - Let's calculate the current through the inductor:



$$V(t) = L \frac{dI}{dt}$$

$$L I(t) = \int V_P \sin \omega t dt$$

$$I(t) = -\frac{V_P}{\omega L} \cos \omega t$$

Time Varying Voltages and Inductors


LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- Consider an inductor (L) connected in series with an alternating voltage ($V_P \sin \omega t$) as shown below.

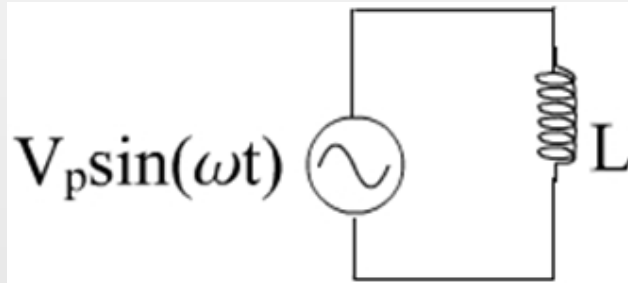- Let's calculate the current through the inductor:



$$V(t) = L \frac{dI}{dt}$$

$$L I(t) = \int V_P \sin \omega t dt$$

$$I(t) = -\frac{V_P}{\omega L} \cos \omega t$$

- The current through a inductor is "out-of-phase" with the driving voltage source.

“Out-of-Phase?” for Inductor

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The time dependent voltage was given by

“Out-of-Phase?” for Inductor

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The time dependent voltage was given by

$$V(t) = V_P \sin \omega t$$

“Out-of-Phase?” for Inductor

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The time dependent voltage was given by

$$V(t) = V_P \sin \omega t$$

- The current through the inductor is given by

“Out-of-Phase?” for Inductor

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The time dependent voltage was given by

$$V(t) = V_P \sin \omega t$$

- The current through the inductor is given by

$$I(t) = -\frac{V_P}{\omega L} \cos \omega t$$

“Out-of-Phase?” for Inductor

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The time dependent voltage was given by

$$V(t) = V_P \sin \omega t$$

- The current through the inductor is given by

$$I(t) = -\frac{V_P}{\omega L} \cos \omega t$$

- From trigonometry:

“Out-of-Phase?” for Inductor

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The time dependent voltage was given by

$$V(t) = V_P \sin \omega t$$

- The current through the inductor is given by

$$I(t) = -\frac{V_P}{\omega L} \cos \omega t$$

- From trigonometry:

$$-\cos \omega t = \sin \left(\omega t - \frac{\pi}{2} \right)$$

“Out-of-Phase?” for Inductor

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- Properties of Inductive Reactance

- The time dependent voltage was given by

$$V(t) = V_P \sin \omega t$$

- The current through the inductor is given by

$$I(t) = \frac{V_P}{\omega L} (-\cos \omega t) \rightarrow \frac{V_P}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)$$

- From trigonometry:

$$-\cos \omega t = \sin \left(\omega t - \frac{\pi}{2} \right)$$

Inductive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- **Inductive Reactance**
- Properties of Inductive Reactance

- The current through the inductor is

$$I(t) = \frac{V_P}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right)$$

Inductive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- **Inductive Reactance**
- Properties of Inductive Reactance

- The current through the inductor is

$$I(t) = \frac{V_P}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right)$$

- The current through the inductor is $\frac{\pi}{2}$ out of phase with the driving voltage.

Inductive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- **Inductive Reactance**
- Properties of Inductive Reactance

- The current through the inductor is

$$I(t) = \frac{V_P}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right)$$

- The current through the inductor is $\frac{\pi}{2}$ out of phase with the driving voltage.
 - Current lags behind the driving voltage by 90° .

Inductive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- **Inductive Reactance**
- Properties of Inductive Reactance

- The current through the inductor is

$$I(t) = \frac{V_P}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right)$$

- The current through the inductor is $\frac{\pi}{2}$ out of phase with the driving voltage.
 - Current lags behind the driving voltage by 90° .
- The peak current through the capacitor is $I_P = \frac{V_P}{\omega L}$

Inductive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- **Inductive Reactance**
- Properties of Inductive Reactance

- The current through the inductor is

$$I(t) = \frac{V_P}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right)$$

- The current through the inductor is $\frac{\pi}{2}$ out of phase with the driving voltage.
 - Current lags behind the driving voltage by 90° .
- The peak current through the capacitor is $I_P = \frac{V_P}{\omega L}$
 - This resembles Ohm's Law with $I_P = \frac{V_P}{\chi_L}$

Inductive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- **Inductive Reactance**
- Properties of Inductive Reactance

- The current through the inductor is

$$I(t) = \frac{V_P}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right)$$

- The current through the inductor is $\frac{\pi}{2}$ out of phase with the driving voltage.
 - Current lags behind the driving voltage by 90° .
- The peak current through the capacitor is $I_P = \frac{V_P}{\omega L}$
 - This resembles Ohm's Law with $I_P = \frac{V_P}{\chi_L}$
 - The term $\chi_L = \omega L$ has a unit of Ohm

Inductive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- "Out-of-Phase?"
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- "Out-of-Phase?" for Inductor
- **Inductive Reactance**
- Properties of Inductive Reactance

- The current through the inductor is

$$I(t) = \frac{V_P}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right)$$

- The current through the inductor is $\frac{\pi}{2}$ out of phase with the driving voltage.
 - Current lags behind the driving voltage by 90° .
- The peak current through the capacitor is $I_P = \frac{V_P}{\omega L}$
 - This resembles Ohm's Law with $I_P = \frac{V_P}{\chi_L}$
 - The term $\chi_L = \omega L$ has a unit of Ohm and is called inductive reactance (χ_L)

Properties of Inductive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- **Properties of Inductive Reactance**

- The reactance for an inductor describes the behavior of a inductor placed in a circuit with a time-varying voltage source.

Properties of Inductive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- **Properties of Inductive Reactance**

- The reactance for an inductor describes the behavior of a inductor placed in a circuit with a time-varying voltage source.

$$\chi_L = \omega L$$

- When ω is large, χ_L is large so the inductor offers greater “resistance” to current flow.

Properties of Inductive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- **Properties of Inductive Reactance**

- The reactance for an inductor describes the behavior of an inductor placed in a circuit with a time-varying voltage source.

$$\chi_L = \omega L$$

- When ω is large, χ_L is large so the inductor offers greater “resistance” to current flow.
- When ω is small, χ_L is small so the inductor offers less “resistance” to current flow.

Properties of Inductive Reactance

LC - Oscillator

Alternating Current
Circuits

- Introduction
- Time Varying Voltages
- Time Varying Voltages and Resistors
- Time Varying Voltages and Capacitors
- “Out-of-Phase?”
- Capacitive Reactance
- Properties of Capacitive Reactance
- Time Varying Voltages and Inductors
- “Out-of-Phase?” for Inductor
- Inductive Reactance
- **Properties of Inductive Reactance**

- The reactance for an inductor describes the behavior of a inductor placed in a circuit with a time-varying voltage source.

$$\chi_L = \omega L$$

- When ω is large, χ_L is large so the inductor offers greater “resistance” to current flow.
- When ω is small, χ_L is small so the inductor offers less “resistance” to current flow.
- χ_L is NOT the same as resistance because NO POWER IS DISSIPATED THROUGH A INDUCTOR.