

**Clicker Session –
Currents, DC Circuits**

Wires

A wire of resistance R is stretched uniformly (keeping its volume constant) until it is twice its original length. What happens to the resistance?

- 1) it decreases by a factor 4
- 2) it decreases by a factor 2
- 3) it stays the same
- 4) it increases by a factor 2
- 5) it increases by a factor 4

Wires

A wire of resistance R is stretched uniformly (keeping its volume constant) until it is twice its original length. What happens to the resistance?

- 1) it decreases by a factor 4
- 2) it decreases by a factor 2
- 3) it stays the same
- 4) it increases by a factor 2
- 5) it increases by a factor 4


Keeping the volume (= area x length) constant means that if the length is **doubled**, the area is **halved**.

Since $R = \rho \frac{L}{A}$, this increases the resistance by **four**.

Series Resistors I

Assume that the voltage of the battery is **9 V** and that the three resistors are **identical**. What is the potential difference across each resistor?

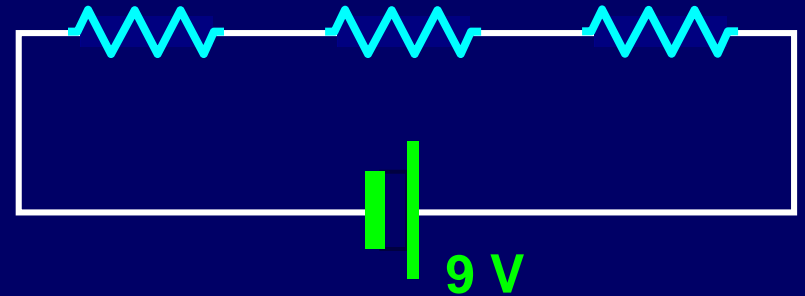- 1) 12 V
- 2) zero
- 3) 3 V
- 4) 4 V
- 5) you need to know the actual value of R



Series Resistors I

Assume that the voltage of the battery is **9 V** and that the three resistors are **identical**. What is the potential difference across each resistor?

1) 12 V


2) zero

3) 3 V

4) 4 V

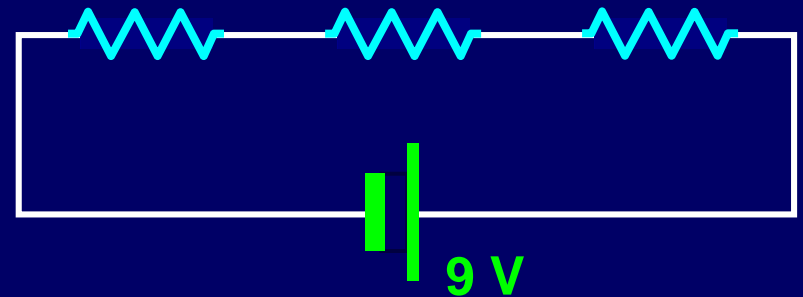5) you need to know the actual value of R

Since the resistors are all **equal**, the voltage will drop **evenly** across the 3 resistors, with $1/3$ of 9 V across each one. So we get a **3 V drop** across each.




Follow-up: What would be the potential difference if $R = 1 \Omega, 2 \Omega, 3 \Omega$

Series Resistors II

In the circuit below, what is the voltage across R_1 ?

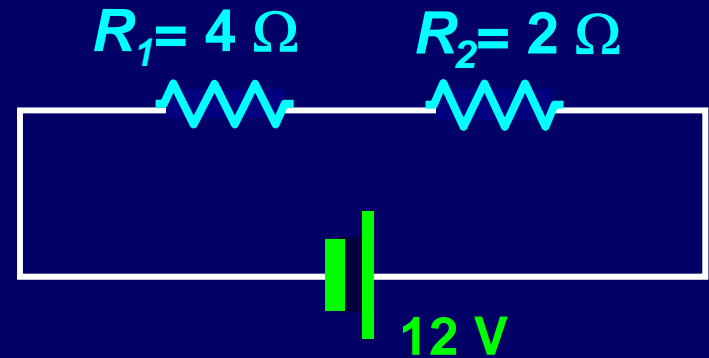- 1) 12 V
- 2) zero
- 3) 6 V
- 4) 8 V
- 5) 4 V



Series Resistors II

In the circuit below, what is the voltage across R_1 ?

1) 12 V


2) zero

3) 6 V

4) 8 V

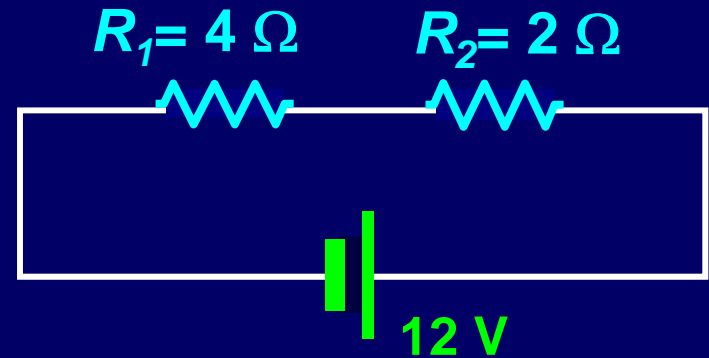5) 4 V


The voltage drop across R_1 has to be twice as big as the drop across R_2 . This means that $V_1 = 8\text{ V}$ and $V_2 = 4\text{ V}$. Or else you could find the current $I = V/R = (12\text{ V})/(6\ \Omega) = 2\text{ A}$, then use Ohm's Law to get voltages.



Parallel Resistors I

In the circuit below, what is the current through R_1 ?

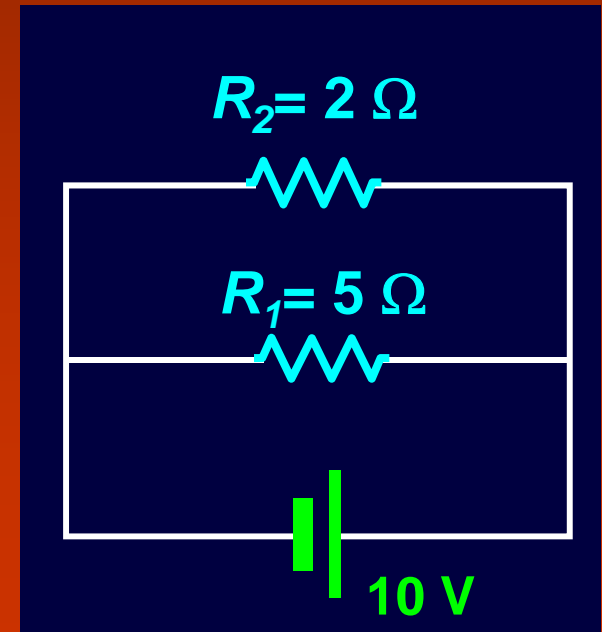- 1) 10 A
- 2) zero
- 3) 5 A
- 4) 2 A
- 5) 7 A



Parallel Resistors I

In the circuit below, what is the current through R_1 ?

1) 10 A


2) zero

3) 5 A

4) 2 A

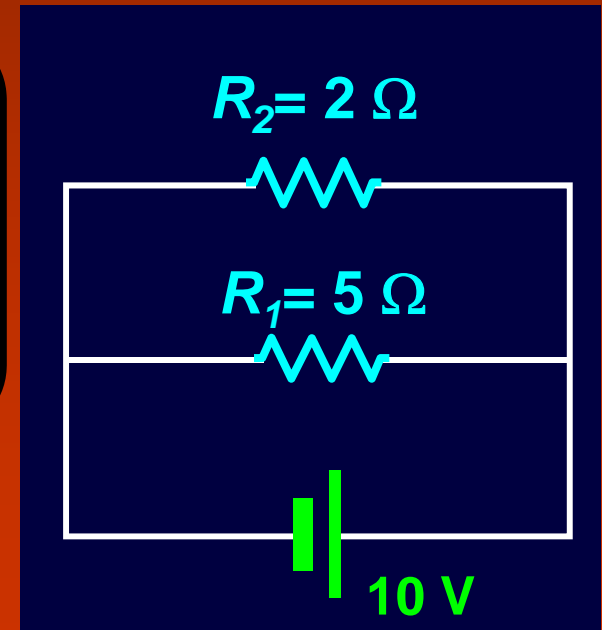5) 7 A

The **voltage** is the **same** (10 V) across each resistor because they are in parallel. Thus, we can use Ohm's Law, $V_1 = I_1 R_1$ to find the current $I_1 = 2 \text{ A}$.




Follow-up: What is the total current through the battery?

Parallel Resistors II

Points P and Q are connected to a battery of fixed voltage. As more resistors R are added to the parallel circuit, what happens to the **total current** in the circuit?

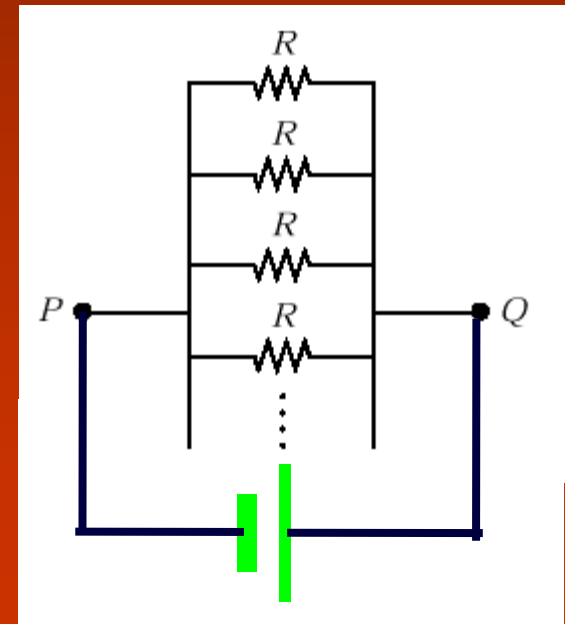- 1) increases
- 2) remains the same
- 3) decreases
- 4) drops to zero




Parallel Resistors II

Points P and Q are connected to a battery of fixed voltage. As more resistors R are added to the parallel circuit, what happens to the **total current** in the circuit?

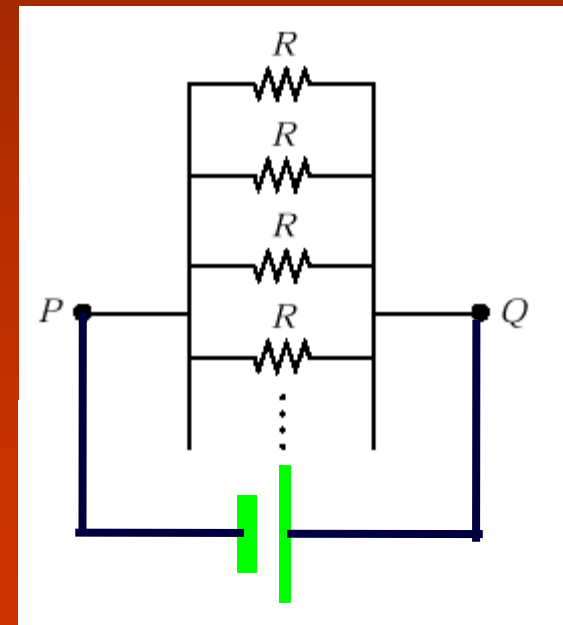- 1) increases
- 2) remains the same
- 3) decreases
- 4) drops to zero

As we add parallel resistors, the overall **resistance of the circuit drops**. Since $V = IR$, and V is held constant by the battery, when **resistance decreases**, the **current must increase**.




Follow-up: What happens to the current through each resistor?

Diagrams

Which of these diagrams represent the same circuit?

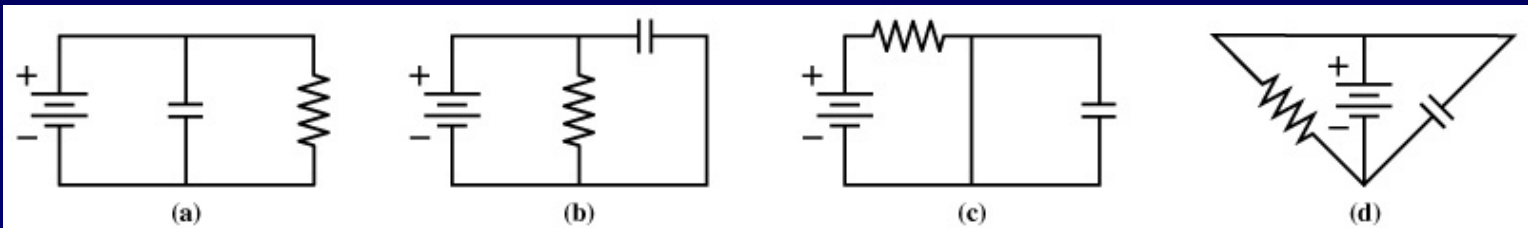
- A. a and b
- B. a and c
- C. b and c
- D. a, b, and c
- E. a, b, and d



Diagrams

Which of these diagrams represent the same circuit?

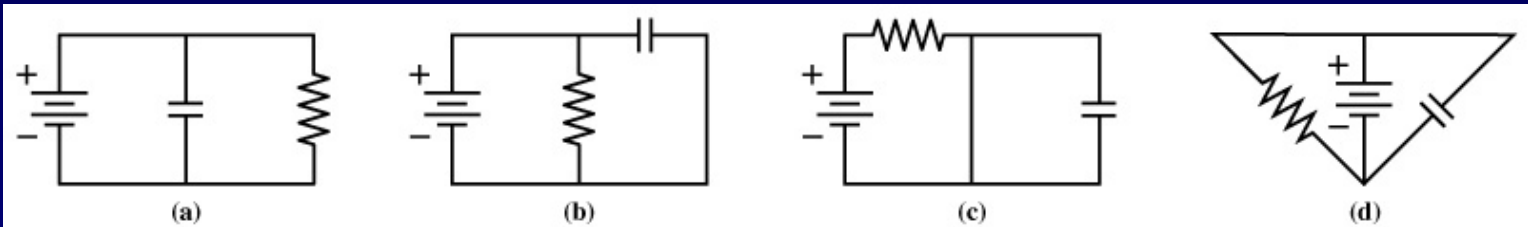- A. a and b
- B. a and c
- C. b and c
- D. a, b, and c
- E. a, b, and d




The three elements are **in parallel** – their ends are connected by conducting wires. The order of the elements and length of the connecting wires are immaterial.

Circuit I

Three lightbulbs, A, B and C are in the circuit shown. When the switch is closed, lightbulb A will:

- 1) glow brighter than before
- 2) glow just the same as before
- 3) glow dimmer than before
- 4) go out completely
- 5) explode

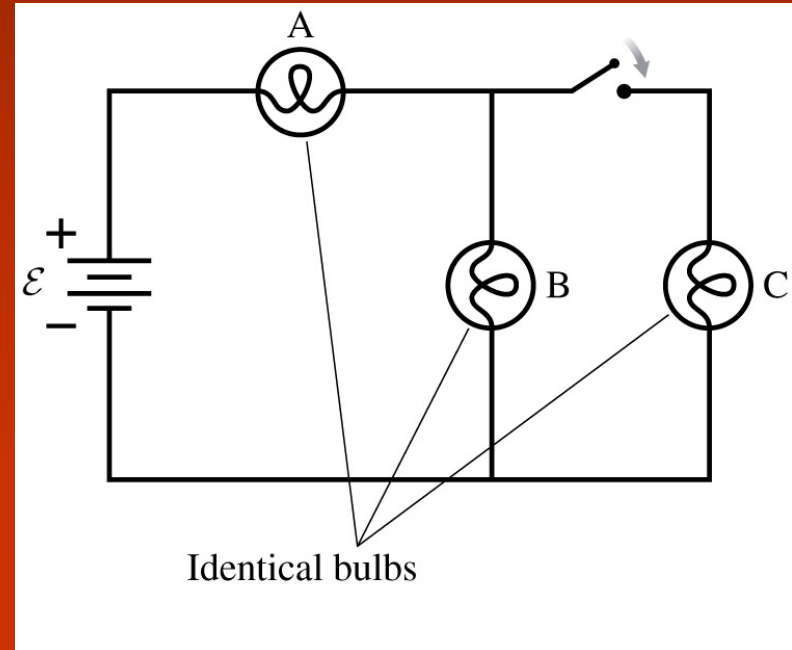


Circuit I

Three lightbulbs, A, B and C are in the circuit shown. When the switch is closed, lightbulb A will:

- 1) glow brighter than before
- 2) glow just the same as before
- 3) glow dimmer than before
- 4) go out completely
- 5) explode

Since the total resistance through bulbs B and C is now less than the resistance through B alone, the **total resistance of the circuit decreases**. This means that the **current through bulb A increases**.


Follow-up: What happens to bulb B?

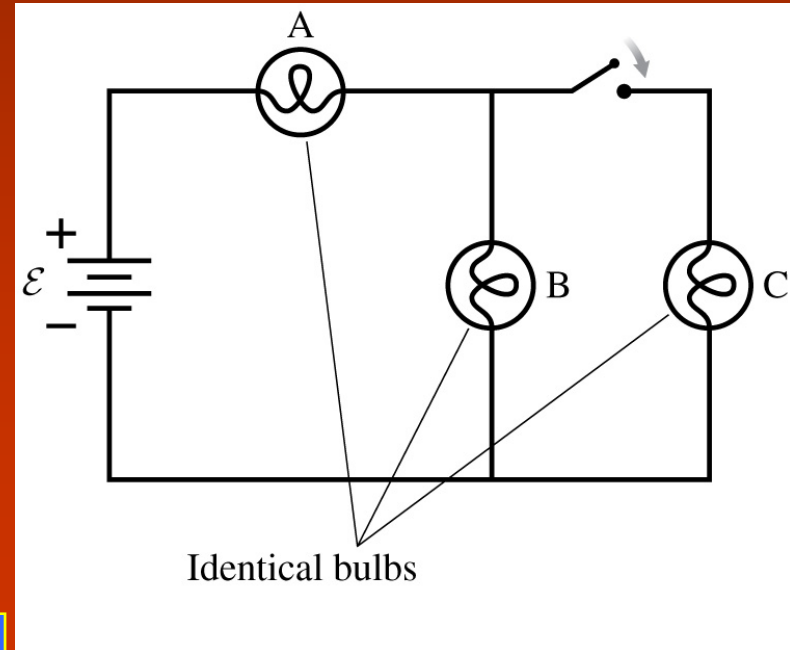

Circuits II

The lightbulbs in the circuit below are identical with the same resistance R . Which circuit produces more light? (brightness \iff power)

- 1) circuit 1
- 2) circuit 2
- 3) both the same
- 4) it depends on R

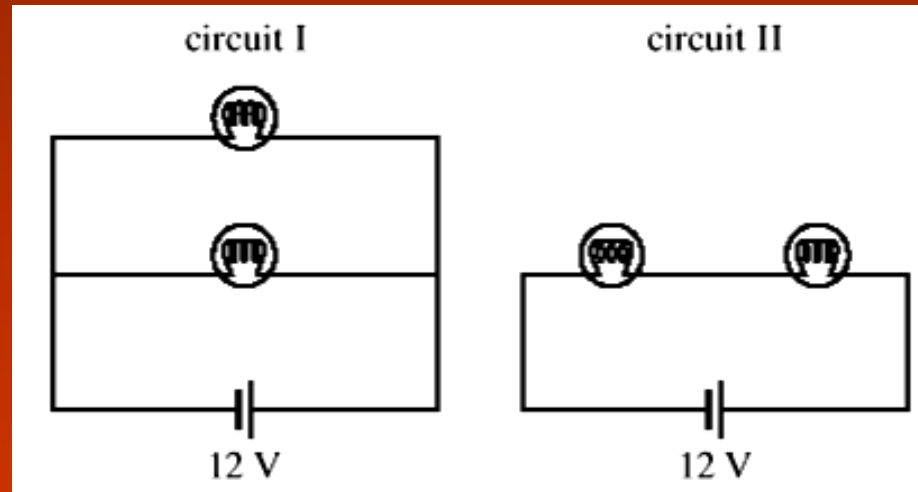


Circuits II

The lightbulbs in the circuit below are identical with the same resistance R . Which circuit produces more light? (brightness \iff power)


- 1) circuit 1
- 2) circuit 2
- 3) both the same
- 4) it depends on R

In #1, the bulbs are in **parallel**, lowering the total resistance of the circuit. Thus, circuit #1 will draw a higher current, which leads to more light, because $P = IV$.

circuit I

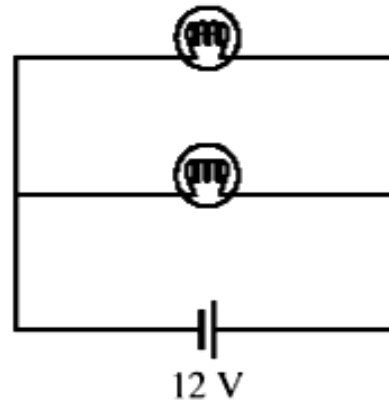


circuit II

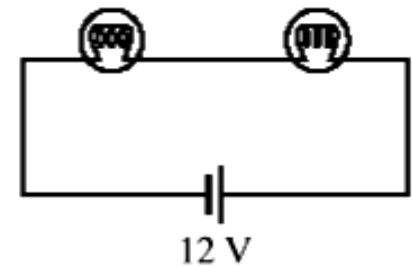

More Circuits I

What happens to the voltage across the resistor R_1 when the switch is closed? The voltage will:

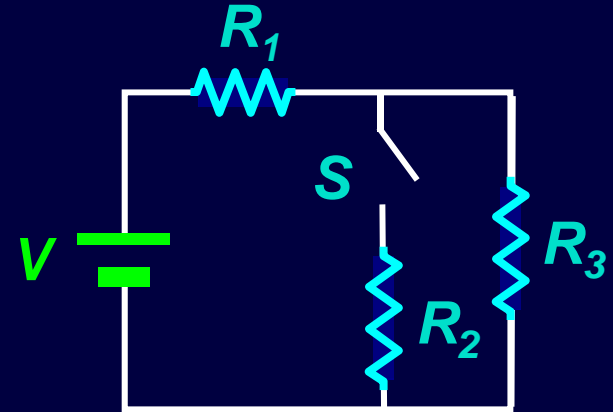- 1) increase
- 2) decrease
- 3) stay the same




More Circuits I

What happens to the voltage across the resistor R_1 when the switch is closed? The voltage will:

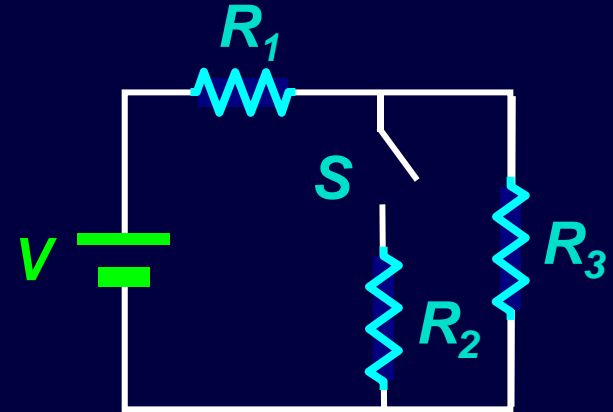- 1) increase
- 2) decrease
- 3) stay the same

With the switch closed, the addition of R_2 to R_3 decreases the equivalent resistance, so the current from the battery increases. This will cause an increase in the voltage across R_1 .




Follow-up: What happens to the current through R_3 ?

More Circuits II

What happens to the voltage across the resistor R_4 when the switch is closed?

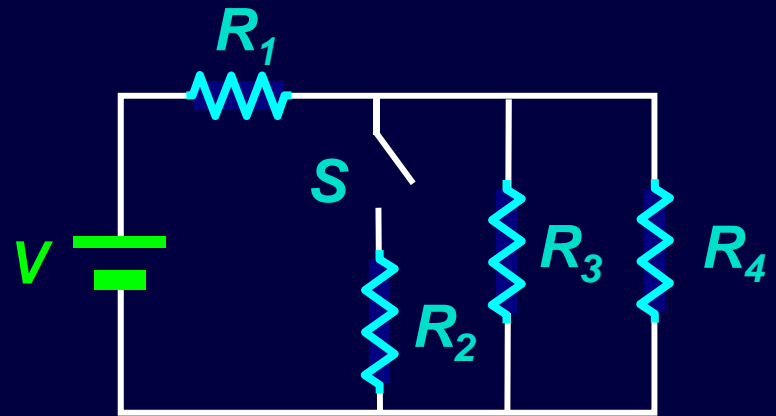- 1) increases
- 2) decreases
- 3) stays the same



More Circuits II


What happens to the voltage across the resistor R_4 when the switch is closed?

1) increases

2) decreases

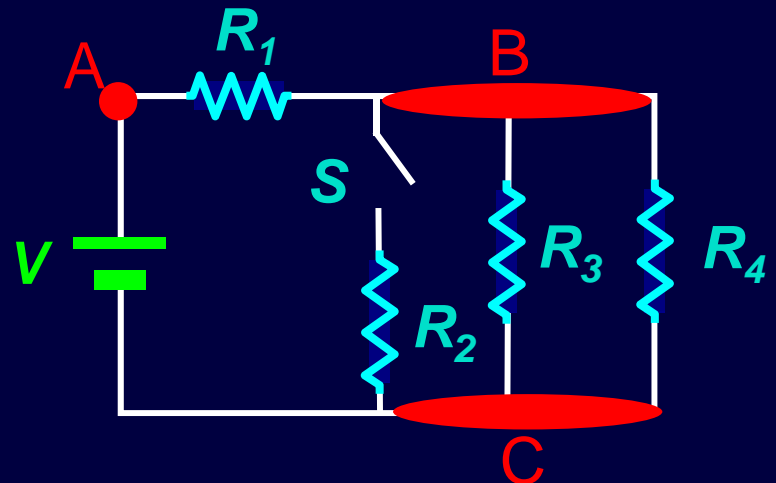3) stays the same

We just saw that closing the switch causes an increase in the voltage across R_1 (which is V_{AB}). The voltage of the battery is constant, so if V_{AB} increases, then V_{BC} must decrease!




Follow-up: What happens to the current through R_4 ?

Even More Circuits

Which resistor has the greatest current going through it? Assume that all the resistors are equal.

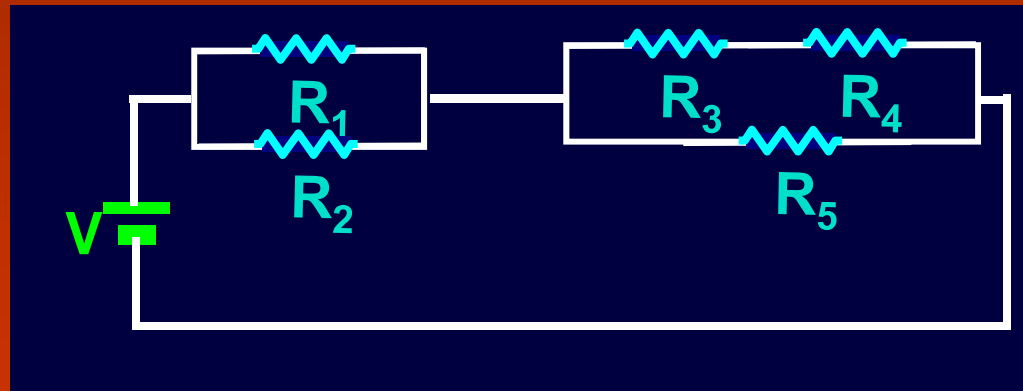- 1) R_1
- 2) both R_1 and R_2 equally
- 3) R_3 and R_4
- 4) R_5
- 5) all the same




Even More Circuits

Which resistor has the greatest current going through it? Assume that all the resistors are equal.

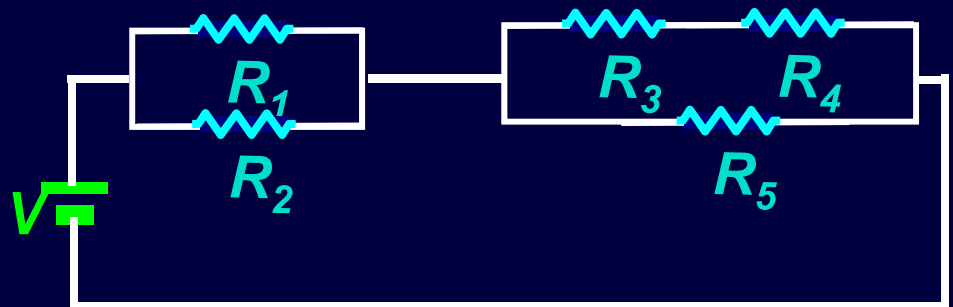- 1) R_1
- 2) both R_1 and R_2 equally
- 3) R_3 and R_4
- 4) R_5
- 5) all the same

The same current must flow through left and right combinations of resistors. On the LEFT, the current splits equally, so $I_1 = I_2$. On the RIGHT, more current will go through R_5 than $R_3 + R_4$ since the branch containing R_5 has less resistance.



Follow-up: Which one has the smallest voltage drop?

Dimmer

When you rotate the knob of a light dimmer, what is being changed in the electric circuit?

- 1) the power
- 2) the current
- 3) the voltage
- 4) both (1) and (2)
- 5) both (2) and (3)

Dimmer

When you rotate the knob of a light dimmer, what is being changed in the electric circuit?

- 1) the power
- 2) the current
- 3) the voltage
- 4) both (1) and (2)
- 5) both (2) and (3)

The voltage is provided at 120 V from the outside. The light dimmer **increases the resistance** and therefore **decreases the current** that flows through the lightbulb.

Follow-up: Why does the voltage not change?

Space Heaters

Two space heaters in your living room are operated at 120 V.

Heater 1 has **twice** the resistance of heater 2. Which one will give off more heat?

- 1) heater 1
- 2) heater 2
- 3) both equally

Space Heaters

Two space heaters in your living room are operated at 120 V.

Heater 1 has **twice** the resistance of heater 2. Which one will give off more heat?

1) heater 1

2) heater 2

3) both equally

Using $P = V^2 / R$, the heater with the **smaller resistance** will have the **larger power** output. Thus, heater 2 will give off more heat.

Follow-up: Which one carries the greater current?

Junction Rule

What is the current in branch P?


1) 2 A

2) 3 A

3) 5 A

4) 6 A

5) 10 A

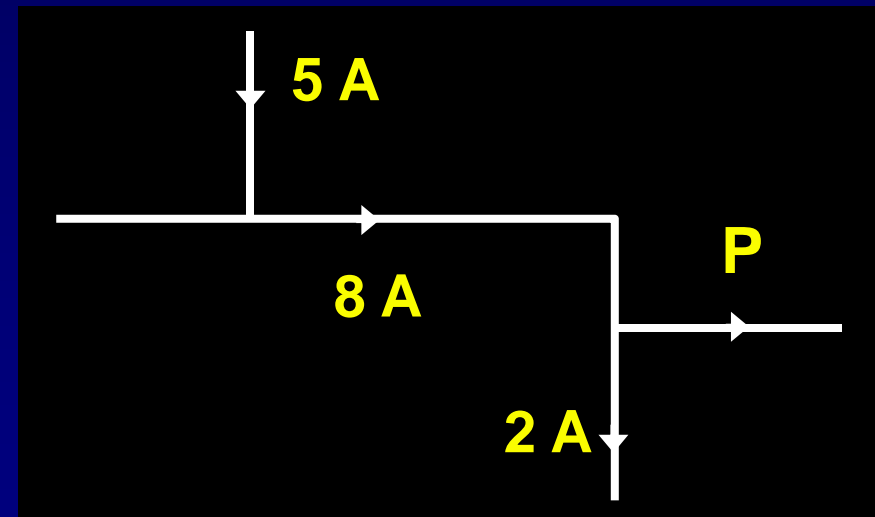

Junction Rule

What is the current in branch P?

1) 2 A


2) 3 A

3) 5 A

4) 6 A

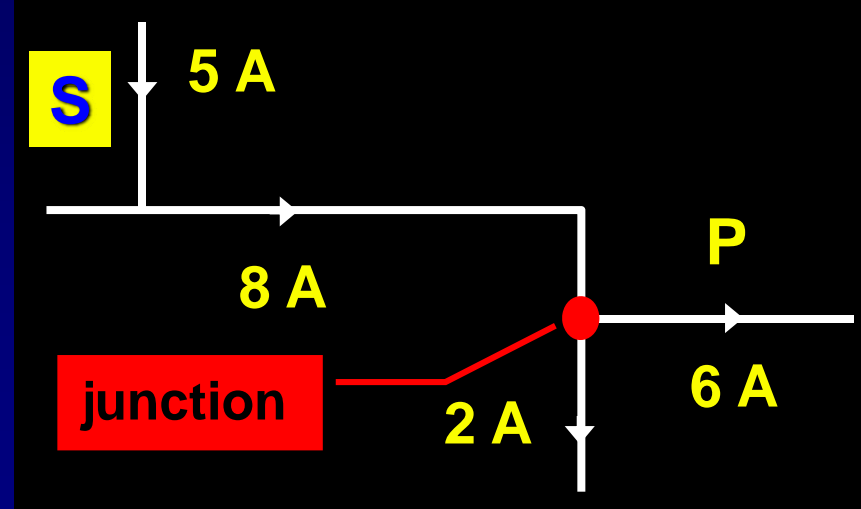5) 10 A

The current entering the junction in **red** is 8 A, so the current leaving must also be 8 A. **One exiting branch has 2 A**, so the other branch (at P) must have 6 A.



Kirchhoff's Rules

Which of the equations is valid for the circuit below?


1) $2 - I_1 - 2I_2 = 0$

2) $2 - 2I_1 - 2I_2 - 4I_3 = 0$

3) $2 - I_1 - 4 - 2I_2 = 0$

4) $I_3 - 4 - 2I_2 + 6 = 0$

5) $2 - I_1 - 3I_3 - 6 = 0$

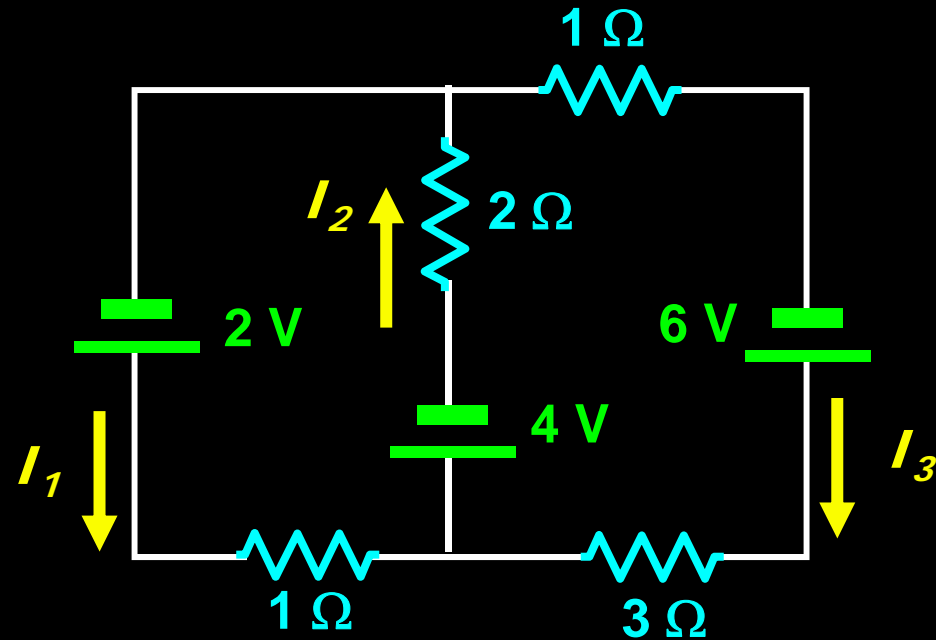

Kirchhoff's Rules

Which of the equations is valid for the circuit below?

1) $2 - I_1 - 2I_2 = 0$


2) $2 - 2I_1 - 2I_2 - 4I_3 = 0$

3) $2 - I_1 - 4 - 2I_2 = 0$

4) $I_3 - 4 - 2I_2 + 6 = 0$

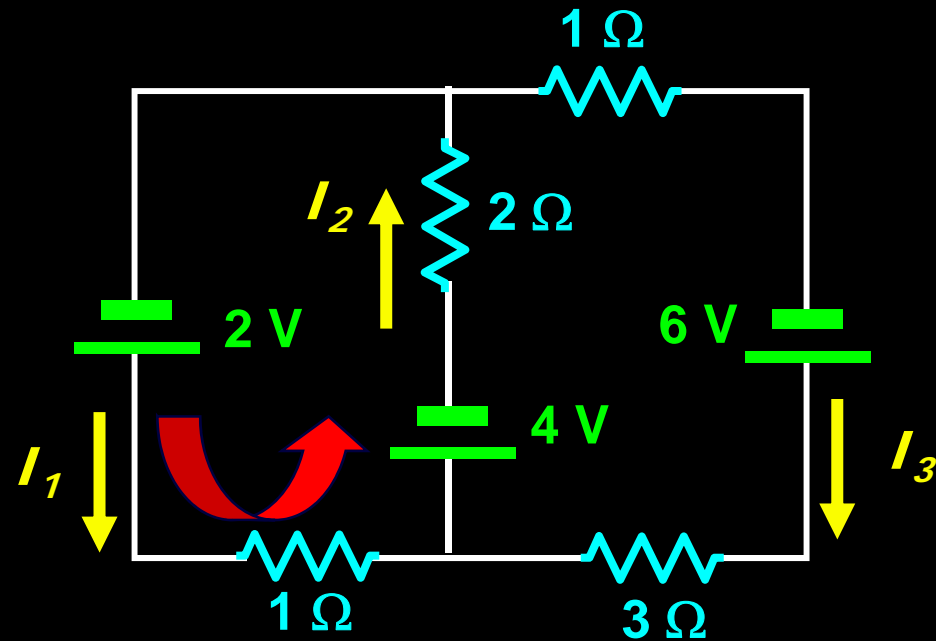5) $2 - I_1 - 3I_3 - 6 = 0$


Eqn. 3 is valid for the left loop:
The left battery gives +2V, then there is a drop through a 1Ω resistor with current I_1 flowing. Then we go through the middle battery (but from + to -!), which gives -4V. Finally, there is a drop through a 2Ω resistor with current I_2 .



RC Circuits

The time constant for the discharge of this capacitor is

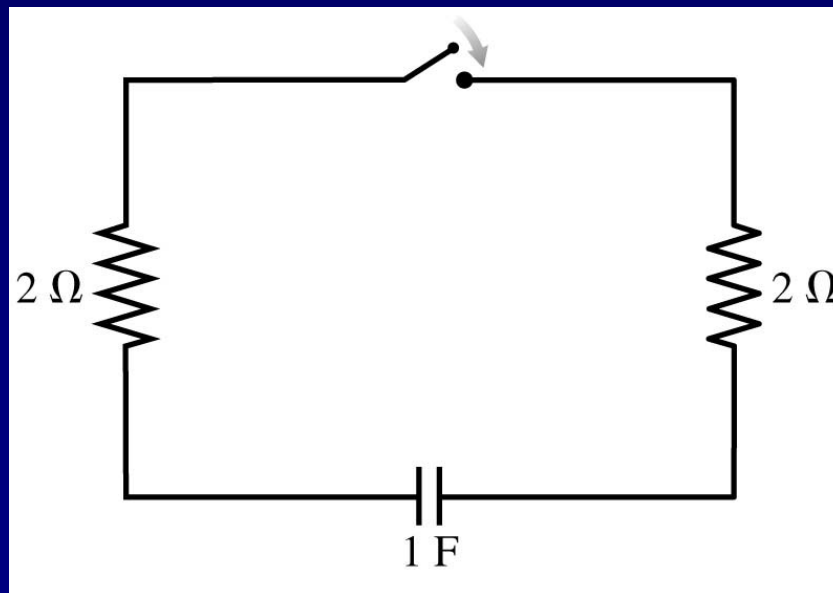- A. 1 s.
- B. 2 s.
- C. 4 s.
- D. 5 s.
- E. The capacitor doesn't discharge because the resistors cancel each other.



RC Circuits

The time constant for the discharge of this capacitor is


A. 1 s.

B. 2 s.

C. 4 s.

D. 5 s.


E. The capacitor doesn't discharge because the resistors cancel each other.

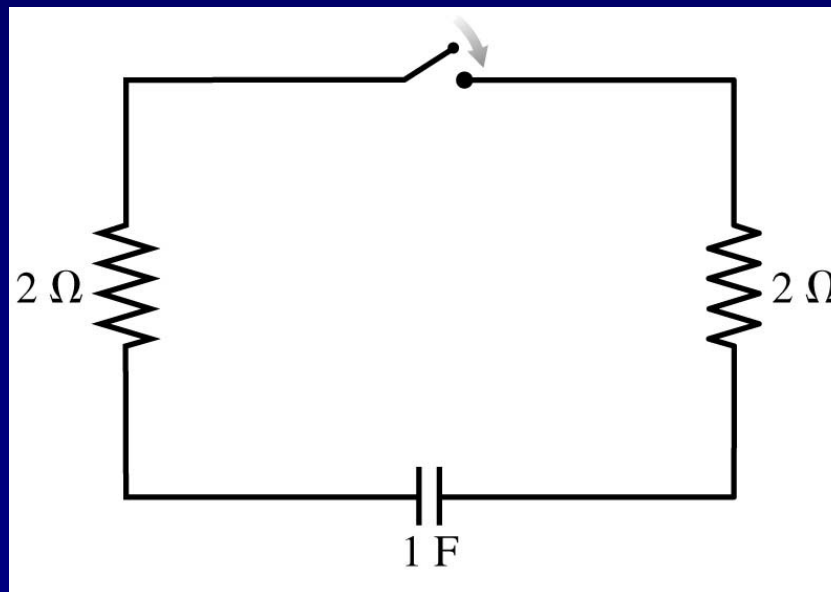

Circuits III

The three lightbulbs in the circuit all have the **same resistance of $1\ \Omega$** . By how much is the **brightness of bulb B** greater or smaller than the **brightness of bulb A**? (brightness \iff power)

- 1) **twice as much**
- 2) **the same**
- 3) **$1/2$ as much**
- 4) **$1/4$ as much**
- 5) **4 times as much**

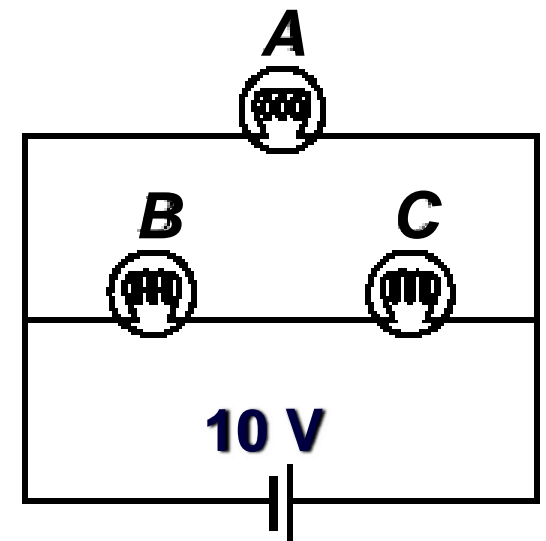

Circuits III


The three lightbulbs in the circuit all have the **same resistance of $1\ \Omega$** . By how much is the **brightness of bulb B** greater or smaller than the **brightness of bulb A**? (brightness \iff power)

- 1) twice as much
- 2) the same
- 3) 1/2 as much
- 4) 1/4 as much
- 5) 4 times as much

We can use $P = V^2/R$ to compare the power:

$$P_A = (V_A)^2/R_A = (10\ \text{V})^2/1\ \Omega = 100\ \text{W}$$
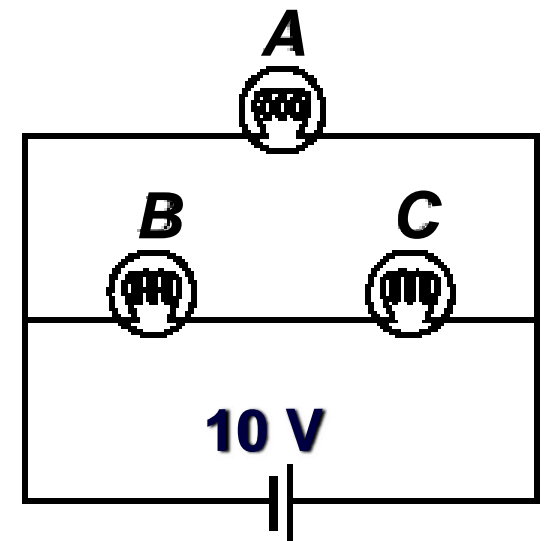
$$P_B = (V_B)^2/R_B = (5\ \text{V})^2/1\ \Omega = 25\ \text{W}$$



Follow-up: What is the total current in the circuit?