

## Physics 102– Pledged Problem 6

Time allowed: 2 hours at a single sitting

**Due 5PM Monday, March 6, 2006**, in the boxes marked Phys 101-102 in the physics lounge. You may use your own textbook, your notes, and a non-programmed calculator. You may also consult the on-line solutions to the corresponding suggested problems. You should consult no other help. Show how you arrived at your answer; the correct answer by itself may not be sufficient.

Further instructions:

- Write legibly on **one** side of 8.5" x 11" white or lightly tinted paper.
- Staple all sheets together, including this one, in the upper left corner and make one vertical fold.
- On the outside, staple side up, print your name in capital letters, your LAST NAME first followed by your FIRST NAME.
- Below your name, print the phrase "Pledged Problem 6", followed by the due date.
- Also indicate **start time** and **end time**.
- Write and sign the pledge, with the understanding that you may consult the materials noted above.


---

I. This problem consists of three questions about resistance, currents, and current densities.

- The wiring in a house must have low enough resistance so that it does not heat up too much while current is flowing. A particular copper wire needs to carry 20A of current, and it must not dissipate more than 2 Watts of power per meter of length. If the cross-section of this wire is circular, what is the minimum diameter that the wire must have so that it doesn't heat up too much? The resistivity of copper is  $\rho = 1.72 \times 10^{-8} \Omega - m$ .
- The density of copper metal is  $d = 9g/cm^3$ , and the atomic mass (averaged over naturally occurring isotopes) is 63.5 g/mole. Avagadro's number is  $N_A = 6.02 \times 10^{23}$  atoms/mole. Assume one charge carrier per atom and determine the density of charge carriers  $n$  (number of charge carriers/ $m^3$ ) in copper.
- A copper wire with a circular cross section with radius  $r = 1mm$  carries 1A of current. Determine the drift velocity of the electrons in the wire.

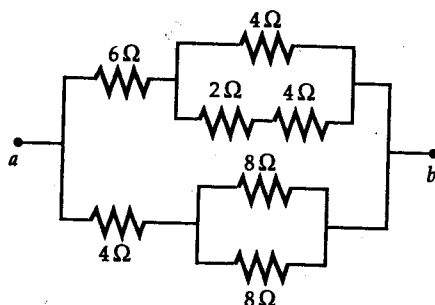II. For the circuit shown below, a 12V battery is connected across the points *a* and *b*. Determine the following:

- The effective resistance  $R_{eff}$  of the circuit.
- The total current and the total power supplied by the battery.
- The current through each resistor and the power dissipated in each resistor.
- For the power dissipation, does the sum of all the contributions in (c) equal the result in (b)?



# Phys102

## Pledged Problem 6

$$I. (a) \rho = 1.72 \times 10^{-8} \Omega \cdot m$$

$$I = 20 A$$

$$P_{\text{power}} = I^2 R = 2 \text{ Watts/m}$$

$$R = \frac{2 \text{ Watts}}{400 A} = .005 \Omega$$

$$R = \frac{\rho l}{A} = \frac{(1.72 \times 10^{-8} \Omega \cdot m)(1m)}{A} = .005 \Omega$$

$$A = \frac{1.72 \times 10^{-8} m^2}{5 \times 10^{-3}} = .344 \times 10^{-5} m^2 = \pi r^2$$

$$.109 \times 10^{-5} m^2 = r^2$$

$$1.046 \times 10^{-3} m = r = 1.046 \text{ mm}$$

$$\text{diameter} = 2.09 \text{ mm}$$

$$(b) \quad d = 9 \text{ g/cm}^3 \quad A = 63.5 \text{ g/mole} \quad N_A = 6.02 \times 10^{23} \text{ atoms/mole}$$

$$n = \frac{9 \text{ g/cm}^3 (6.02 \times 10^{23} \text{ atoms/mole})}{63.5 \text{ g/mole}}$$

$$n = 0.85 \times 10^{23} \text{ atoms/cm}^3$$

watch units — need answer in atoms/m<sup>3</sup>

$$n = 8.5 \times 10^{22} \text{ atoms/cm}^3 (10^6 \text{ cm}^3/\text{m}^3)$$

$$\boxed{n = 8.5 \times 10^{28} / \text{m}^3}$$

(c)



$$\Delta Q = n A n_d q \Delta t$$

$$\frac{\Delta Q}{\Delta t} = I = n A n_d q$$

Use  $n$  from (b),  $I = 1 \text{ Amp}$

$$r = 1 \text{ mm} = 0.1 \text{ cm}$$


$$q = 1.6 \times 10^{-19} \text{ C}$$

$$A = \pi r^2 = 0.0314 \text{ cm}^2$$


$$n_d = \frac{I}{n A q} = \frac{1 \text{ A}}{(8.5 \times 10^{22} / \text{cm}^3) (0.0314 \text{ cm}^2) (1.6 \times 10^{-19} \text{ C})}$$

$$\boxed{n_d = 2.34 \times 10^{-3} \text{ cm/s} = 2.34 \times 10^{-5} \text{ m/s}}$$

II.

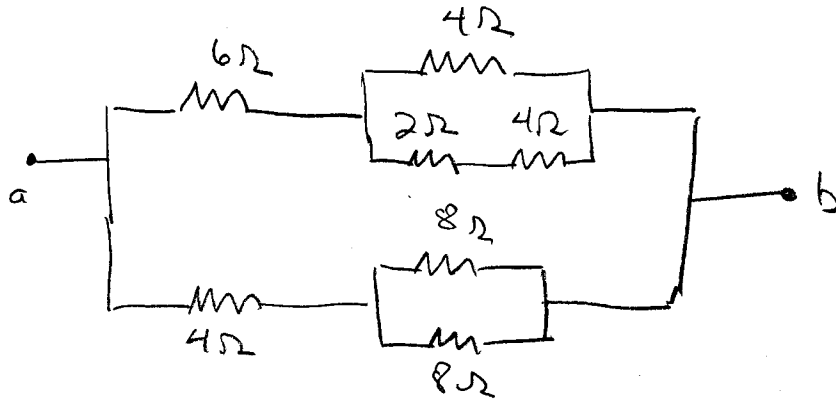


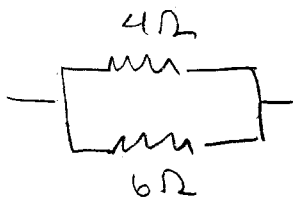(9) Find  $R_{eff}$  - first combine the two sets of parallel resistors:



$$\Rightarrow \frac{1}{4} + \frac{1}{6} = \frac{1}{R_{eff1}} = \frac{3}{12} + \frac{2}{12} = \frac{5}{12}$$

$$R_{eff1} = \frac{12}{5} = 2.4\Omega$$

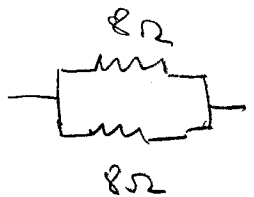

$$\Rightarrow \frac{1}{8} + \frac{1}{8} = \frac{2}{8} = \frac{1}{4} \quad R_{eff2} = 4\Omega$$

$R_{eff1}$  is in series with  $6\Omega \Rightarrow R_{eff3} = 8.4\Omega$

$R_{eff2}$  is in series with  $4\Omega \Rightarrow R_{eff4} = 8\Omega$

$R_{eff3}$  and  $R_{eff4}$  are in parallel with each other,

$$\frac{1}{R_{eff}} = \frac{1}{R_{eff3}} + \frac{1}{R_{eff4}} = \frac{1}{8.4} + \frac{1}{8}$$


$$R_{eff} = 4.1\Omega$$

$$(b) I = \frac{V}{R_{eq}} = \frac{12V}{4.1\Omega}$$

$$I = 2.93A$$

$$Power = IV = (2.93A)(12V) = 35.2 \text{ Watts} = P$$

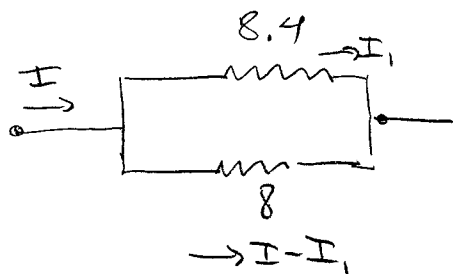(c) To determine the current in each resistor, first see how it splits between  $R_{eq3}$  and  $R_{eq4}$




$$8.4(I_1) = 8(I - I_1)$$

$$16.4 I_1 = 8I$$

$$I_1 = .49I = 1.436A$$

$$I_2 = I - I_1 = .51I = 1.494A$$

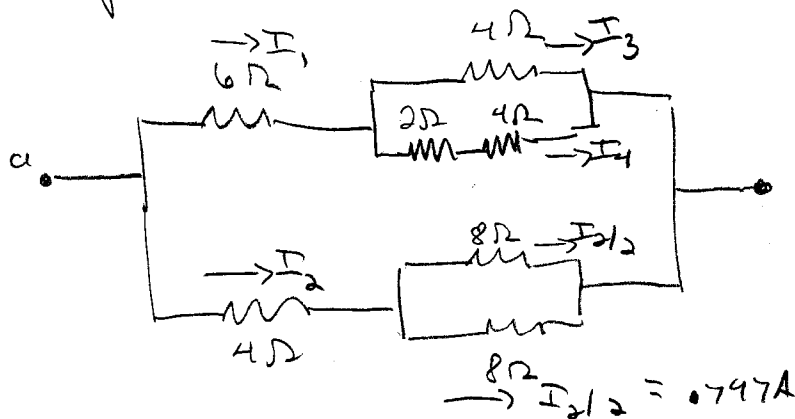These currents get split at the next set of parallel junctions



In the lower section, the current must split evenly, since the two resistors are equal ( $8\Omega$  each).

In the upper section, the current will not split evenly, but the voltage drop must be the same:

$$4I_3 = 6(I_1 - I_3)$$

$$10I_3 = 6I_1$$

$$I_3 = .6I_1$$


$$I_4 = I_1 - I_3 = .4I_1$$

$$I_3 = .862A$$

$$I_4 = .579A$$


$$P = I^2 R \text{ for each resistor}$$

Upper section of circuit:

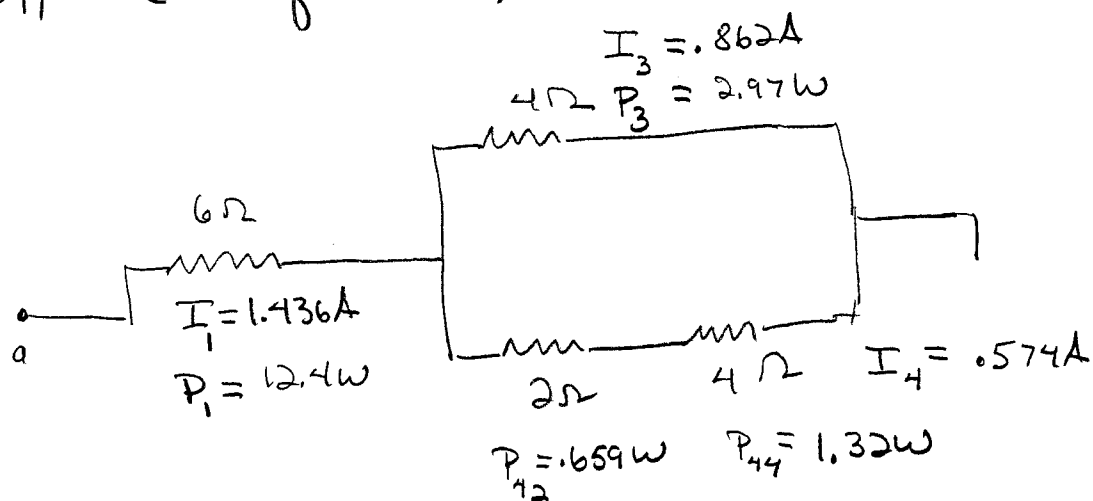

(current must be the same in  $2\Omega$  &  $4\Omega$  resistors)

Lower section:

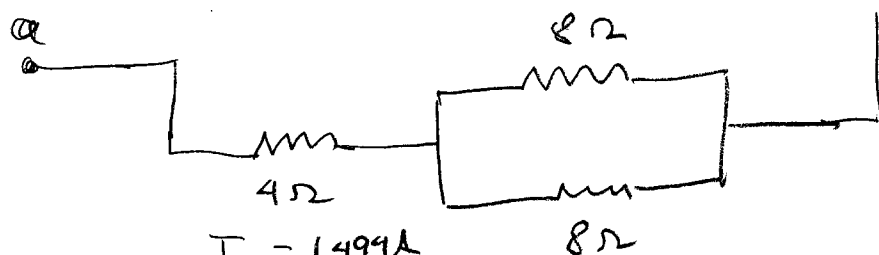

(d) Add up Power in all 7 resistors:

$$P_{TOT} = 12.4 + 2.97 + 0.659 + 1.32 + 8.93 + 2(4.46) \text{ W}$$

$$P_{TOT} = 35.2 \text{ Watts}$$

It works! Power delivered by the battery appears as heat in the resistors.