

Physics 102– Pledged Problem 10


Time allowed: **2 hours at a single sitting**

Due 5PM Wednesday, April 25, 2007, in the boxes marked Phys 101-102 in the physics lounge. You may use your own textbook, your notes, and a non-programmed calculator. You may also consult the on-line solutions to the corresponding suggested problems. You should consult no other help. Show how you arrived at your answer; the correct answer by itself may not be sufficient.

Further instructions:

- Write legibly on **one side** of 8.5" x 11" white or lightly tinted paper.
- Staple all sheets together, including this one, in the upper left corner. Make one vertical fold.
- On the outside, print your name in capital letters, your **LAST NAME** followed by your **FIRST NAME**.
- Below your name, print the phrase "Pledged Problem 10", followed by the due date.
- Write and sign the pledge, with the understanding that you may consult the materials noted above.
- Indicate your **start time** and **end time**.

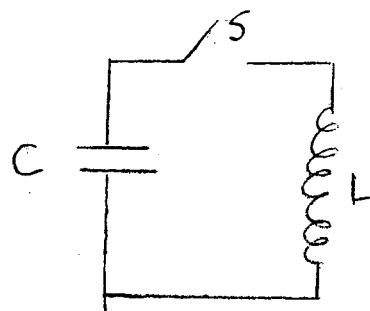
I. A capacitor C and an inductor L are connected in parallel as shown to form an LC oscillator. Initially the capacitor is charged to a voltage V_0 and the switch S is opened. At $t = 0$ the switch is closed. Neglect any resistance in the wires or in the inductor.



- Determine the energy stored in the capacitor at $t = 0$.
- Determine the period of oscillation T of the circuit.
- At $t = T/4$, $1/4$ of the way through the cycle, determine
 - The energy stored in the capacitor
 - The energy stored in the inductor
 - The current through the inductor
 - The total energy stored in the circuit.
- Repeat (c) for $t = T/2$, half way through the oscillation cycle.
- Describe qualitatively what happens if a small resistance R is included in the circuit.


II. A very large cylindrical capacitor of radius R and plate separation d is being charged slowly with constant current I . As the capacitor charges, the electric field between the plates increases with time. Take r to be the radial distance from the axis of the capacitor, as shown in the figure below.

- At a particular point in time, the surface charge density on the plates is σ . What is the electric field \vec{E} between the plates at that time?
- Determine the time rate of change of the electric field, $\frac{dE}{dt}$, in terms of I , R , and other constants.
- Near the center of the plates, the electric field is constant in space. Determine the magnetic field $\vec{B}(r)$ between the plates for $r < R$ in terms of I , R and other constants. Indicate both direction and magnitude of the field.
- Neglecting fringe effects around the edge of the capacitor plates, determine the magnetic field $\vec{B}(r)$ for $r = R$ and for $r > R$. Sketch $B(r)$ for all r .

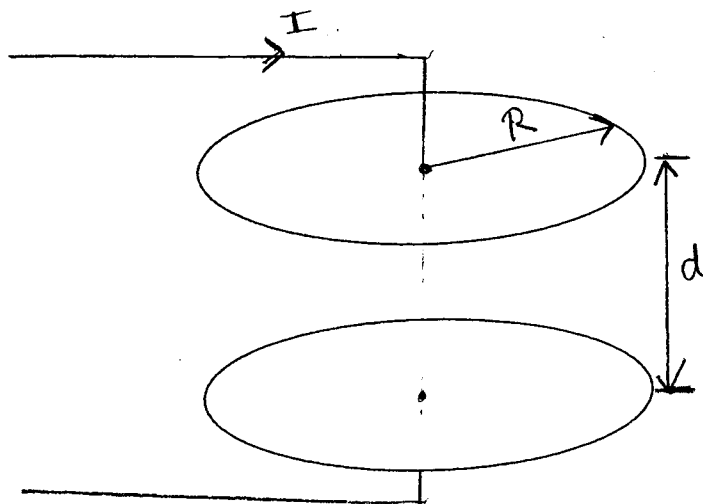

Phyp 102

Pledged Problem 10

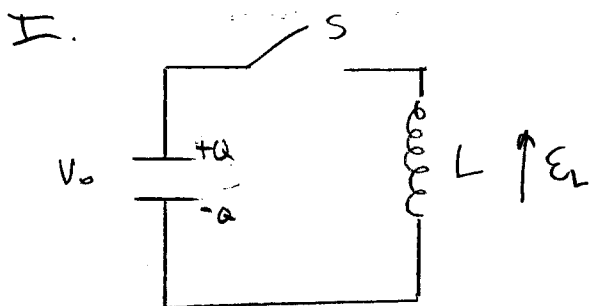

(a) $U_E = \frac{1}{2} C V_0^2$

(b) If the charge on the capacitor is Q , the voltage drop across C is $\frac{Q}{C}$. When the switch is closed, I is in the clockwise direction as is $\frac{dI}{dt}$. But $I = -\frac{dQ}{dt}$, since the charge on C is decreasing. Then Kirchoff's loop equation is

$$\frac{Q}{C} - L \frac{dI}{dt} = 0$$

$$\frac{Q}{C} + L \frac{d^2 Q}{dt^2} = 0 \quad \Rightarrow \quad \frac{d^2 Q}{dt^2} + \underbrace{\frac{1}{LC}}_{\omega^2} Q = 0$$

This last eqn. is exactly the form for simple harmonic oscillations with $\omega^2 = \frac{1}{LC}$

$$\omega = 2\pi\nu = \frac{2\pi}{T} = \frac{1}{\sqrt{LC}}$$

$$\text{or } T = 2\pi\sqrt{LC}$$

(C) The equation for Q is then

$$Q(t) = A \cos \omega t + B \sin \omega t$$

$$Q(t=0) = CV_0 = A$$

$$\frac{dQ(t)}{dt} = -I(t) = 0 = -\omega A \sin \omega t + \omega B \cos \omega t$$

$$0 = \omega B \quad \text{or} \quad B = 0$$

$$Q(t) = CV_0 \cos \omega t.$$

$$\text{At } t = T/4, \quad \omega t = \frac{2\pi}{T} \left(\frac{T}{4} \right)$$

$$\omega t = \frac{2\pi}{4} = \frac{\pi}{2}$$

- This makes sense since one full cycle has $\omega t = 2\pi$

$$Q(T/4) = CV_0 \cos(\pi/2) = 0 \Rightarrow \text{no charge on the capacitor,}$$

$$\text{so } U_C = 0 \text{ at } t = T/4 \quad \text{(i)}$$

$$\frac{dQ}{dt} = I = -CV_0 \omega \sin \omega t$$

$$U_L = \frac{1}{2} L I^2 = \frac{1}{2} L (C^2 V_0^2 \omega^2 \sin^2(\pi/2))$$

$$U_L = \frac{1}{2} \cancel{L} \frac{C^2 V_0^2}{\cancel{LC}} = \frac{1}{2} C V_0^2$$

$$U_L = \frac{1}{2} C V_0^2 \quad \text{(ii)} - \text{at } t = T/4, \text{ all the energy is in the inductor!}$$

$$|I(t = \pi/4)| = \frac{CV_0}{\sqrt{LC}} \sin(\pi/2) \stackrel{=1}{}$$

$$I(\pi/4) = \frac{CV_0}{\sqrt{LC}} \quad (\text{iii})$$

Direction is clockwise



$$\text{Total energy is } U_C + U_L = \frac{1}{2} CV_0^2 \quad (\text{iv})$$

Same as the initial energy.

$$(d) \text{ At } t = \pi/2 = \frac{2\pi\sqrt{LC}}{2} = \pi\sqrt{LC}$$

$$Q(\pi/2) = CV_0 \cos\left(\frac{\pi\sqrt{LC}}{\sqrt{LC}}\right) = -CV_0$$

$$U_C = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{C^2 V_0^2}{C} = \frac{1}{2} CV_0^2$$

$$U_C = \frac{1}{2} CV_0^2 \quad (\text{i})$$


$$I = \frac{dq}{dt} = -\omega CV_0 \sin \pi = 0$$


$$\text{Since } I = 0, \quad U_L = 0 \quad (\text{ii})$$

$$I = 0 \quad (\text{iii})$$

$$U_{\text{TOT}} = U_C + U_L = \frac{1}{2} CV_0^2 \quad (\text{iv}) \quad \text{— Same as the initial energy!}$$

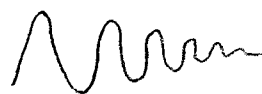(e) If there is some resistance R in the circuit, the total energy decays with time due to $I^2 R$ losses in R . The amplitude of the oscillation decreases with time.



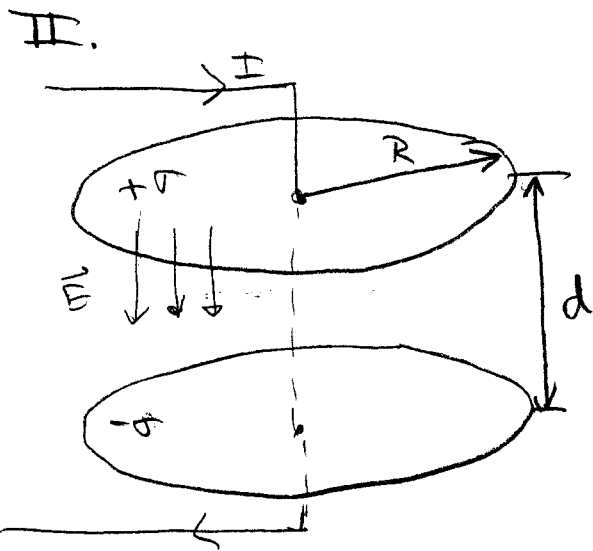

(9) When the surface charge on the plates = σ , by Gauss' law



$$\int \vec{E} \cdot d\vec{A} = E A = \frac{\sigma A}{\epsilon_0}$$

$$|\vec{E}| = \frac{\sigma}{\epsilon_0}$$

Direction is \perp to the plates, away from the top plate ($-\hat{j}$).

$$(b) I = \frac{dQ}{dt}$$

$$Q_{\text{on the plates}} = \sigma (\pi R^2)$$

$$\sigma = \frac{Q}{\pi R^2} \quad \frac{d\sigma}{dt} = \frac{dQ}{dt} \cdot \frac{1}{\pi R^2} = \frac{I}{\pi R^2}$$


$$\frac{dE}{dt} = \frac{d\sigma}{dt} \cdot \frac{1}{\epsilon_0} = \frac{I}{\pi R^2 \epsilon_0}$$

$$\left| \frac{d\vec{E}}{dt} \right| = \frac{I}{\pi R^2 \epsilon_0}$$

As σ increases, \vec{E} increases downward, in the $-\hat{j}$ direction

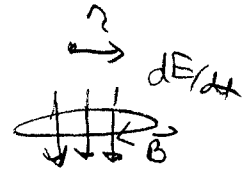(c) from the generalized form of Ampere's law,

$$\oint \vec{B} \cdot d\vec{\ell} = \mu_0 I + \mu_0 \epsilon_0 \frac{d\Phi_E}{dt}$$




$$2\pi r B = \mu_0 \epsilon_0 \frac{d}{dt} (E (\pi r^2)) \quad (\Phi_E = \pi r^2 E)$$

$$|\vec{B}| = \frac{\mu_0 \epsilon_0}{2} \frac{dE}{dt} = \frac{\mu_0 \epsilon_0}{2} \left(\frac{IR}{\pi R^2 \epsilon_0} \right) \quad - B \text{ increases linearly w/ } r$$

$$|\vec{B}| = \frac{\mu_0 IR}{2\pi R^2}$$

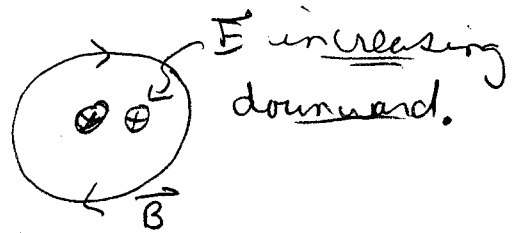direction is clockwise loops, as seen from above.



(d) for $r = R$

$$|\vec{B}| = \frac{\mu_0 I}{2\pi R} \quad - \text{clockwise loops as seen from above}$$

for $r > R$, $\Phi_E = \pi R^2 E$, since we are taking \vec{E} to drop to zero for $r > R$

$$\begin{aligned} \oint \vec{B} \cdot d\vec{s} &= 2\pi r B = \mu_0 \epsilon_0 \frac{d}{dt} (E \pi R^2) \\ &= \mu_0 \epsilon_0 (\pi R^2) \left(\frac{I}{\pi R^2 \epsilon_0} \right) = \mu_0 I \end{aligned}$$

$$|\vec{B}| = \frac{\mu_0 I}{2\pi r}$$

direction is clockwise loops as seen from above.

