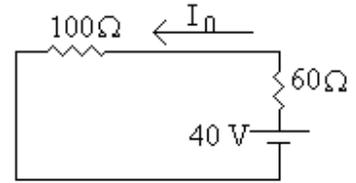



Solution – Pledged Problems #9

1. (a) If the switch has been closed for a long time, then the current has settled down to a constant value and the inductor plays no role in the circuit. The relevant circuit is shown in the figure to the right, and the current through the inductor will be



$$I_0 = \frac{V}{R_{eq}} = \frac{40V}{100\Omega + 60\Omega} = 0.25A$$

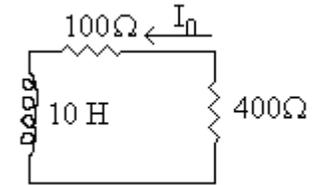(b) When the switch is thrown to the position B, then the circuit is shown in the figure to the right, and the initial current through the inductor will be the I_0 calculated in part 1(a). Therefore, the potential drop across the 100Ω resistor will be



$$V_1 = (100\Omega)(0.25A) = 25V.$$

And since current can't accumulate, the same I_0 will initially flow across the 400Ω resistor, so the potential drop across it will be

$$V_2 = (400\Omega)(0.25A) = 100V.$$


Finally, Kirchhoff's Loop Rule dictates that the potentials will add to zero when following a loop from a point back to that point, so the potential drop across the 10H inductor must be $V_1 + V_2 = 125V$

(c) The energy in the inductor at any given time is $U(t) = \frac{1}{2} L(I(t))^2$, where $I(t) = I_0 e^{-Rt/L}$. Therefore, $U(t) = \frac{1}{2} L I_0^2 e^{-2Rt/L}$. The initial rate of energy-loss is the time derivative of $U(t)$ evaluated at $t = 0$.

$$\frac{dU(t)}{dt} = \frac{1}{2} L I_0^2 \left(\frac{-2R}{L} \right) e^{-2R(t=0)/L} = \frac{1}{2} (10H)(0.25A)^2 \left(\frac{-2(500\Omega)}{10H} \right) = -31.25W$$

Alternatively, the power dissipation associated with the inductor will equal the power dissipated through the resistors $= I^2 R = (0.25A)^2 500\Omega = 31.25W$.

Modifying the circuit by adding a resistor in parallel with the inductor will not affect the answer to (a), since the inductor essentially acts as a short across the 100Ω resistor after the switch S has been in position A for a long time. After the switch is thrown to position B, the circuit will be as shown to the right. The initial current through the 100Ω and 500Ω resistors will remain $0.25A$, for the reasons given in the earlier discussion. However, the power being dissipated includes not only the $-31.25W$ associated with the

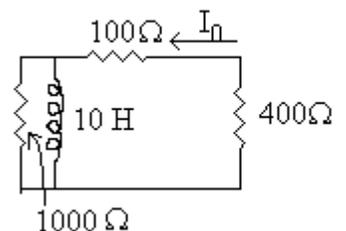

0.25A flowing through the original resistors, but also the power being dissipated through the 1000Ω resistor, also initially held at 125V, which equals $\frac{V^2}{R} = \frac{125^2}{1000} = 15.625W$.

Therefore, the total initial rate of energy loss from the inductor will be

$$31.25W + 15.625W = 46.875W.$$

2. (a) The magnitude of the magnetic induction \vec{B} at the center of the coil can be derived using the Biot-Savart Law, with each element of the coil, dl , contributing $d\vec{B} = \frac{\mu_0 N_1 I_1 dl}{4\pi R_1^2}$ to the field. The total field then has magnitude –

$$B = \int d\vec{B} = \int \frac{\mu_0 N_1 I_1}{4\pi R_1^2} dl = \frac{\mu_0 N_1 I_1}{4\pi R_1^2} \int dl = \frac{\mu_0 N_1 I_1}{4\pi R_1^2} 2\pi R_1 = \frac{\mu_0 N_1 I_1}{2R_1}$$

Given the direction of the current in the loop, the right hand rule indicates the direction of \vec{B} is to the left.

(b) The torque experienced by the small coil can be approximately determined by assuming that \vec{B} is constant in the vicinity of the small coil. The direction and magnitude of the torque on a current loop are given by $\vec{\tau} = \vec{\mu}_2 \times \vec{B}$, where $\vec{\mu}_2 = N_2 I_2 A_2 = N_2 I_2 \pi R_2^2$. Therefore, the torque experienced by the loop 2 is

$$\vec{\tau} = \vec{\mu}_2 \times \vec{B} = (N_2 I_2 \pi R_2^2) \frac{\mu_0 N_1 I_1}{2R_1} \sin \theta$$

(c) The mutual inductance between the two coils can be derived from the equation of the flux in the inner loop associated with the magnetic induction \vec{B} produced by the outer loop.

$$\begin{aligned} \Phi_2 &= \int \vec{B} \cdot d\vec{A}_2 = BA_2 \cos \theta = \frac{\mu_0 N_1 I_1}{2R_1} \pi N_2 R_2^2 \cos \theta = \frac{\mu_0 \pi N_2 N_1 R_2^2 \cos \theta}{2R_1} I_1 \\ \rightarrow M &= \frac{\mu_0 \pi N_2 N_1 R_2^2 \cos \theta}{2R_1} \end{aligned}$$

since, by definition, the mutual inductance is the constant of proportionality between the current I_1 and flux Φ_2 .