

Physics 102 Spring 2007: Suggested Problems # 6

1. Problem 27-64. (+5 pts)

a. +3 pts - Correct value for the current after applying Kirchhoff's rules for circuits.

$$I = 0.3A.$$

b. +1 pt - Correct power through the battery.

$$P_V = V I = 1.8W.$$

c. +1 pt - Correct power through the resistor.


$$P_R = V I = I^2 R = 1.8W.$$

2. Problem 27-80 (+5 pts)

a. +5 pts - Correct answer for the charge on the plates with *correct sign* ($Q_C = 5\mu C$ with top plate positive).

b. +5 pts - Correct answer for the current through the $35\text{-}\Omega$ resistor ($I_{35\Omega} = 0.1A$).

27-64

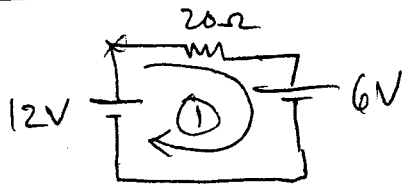

$$\Delta V = 0 = -20I - 6V + 12V = -20I + 6V$$

$$\Rightarrow I = \frac{6}{20} \text{ Amp}$$

(a)

$$I = \frac{3}{10} \text{ Amp}$$

(b) Power through battery (6V)

$$P_{6V} = V_{6V} I = (6V) \left(\frac{3}{10} A \right) = \frac{18}{10} W = 1.8 W \quad \#$$

(c) Power through resistor.


$$P_{20\Omega} = V_{20\Omega} I_{20\Omega} = I_{20\Omega}^2 (20\Omega) = \left(\frac{9A^2}{100} \right) (20\Omega)$$

$$P_{20\Omega} = \frac{9}{5} W = \frac{18}{10} W = 1.8 W$$


$$\text{Note: } P_{12V} = (12V) \left(\frac{3}{10} A \right) = \frac{36}{10} W = 3.6 W$$

$$\text{So } P_{12V} = P_{6V} + P_{20\Omega}$$


27-80

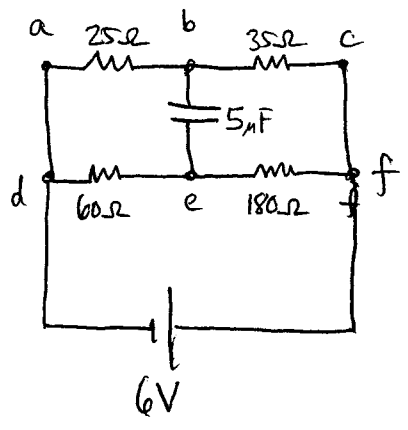

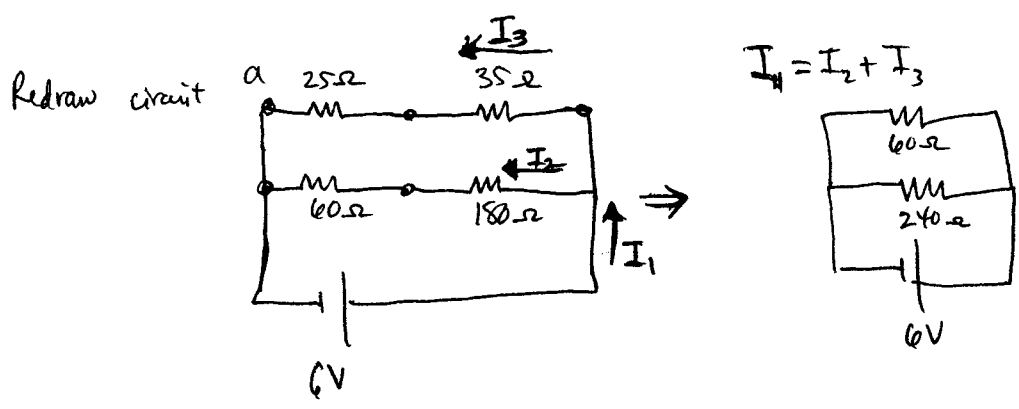After a very long time the capacitor is fully charged so no current "flows" thru capacitor.



$$\frac{1}{R_{eff}} = \frac{1}{60} + \frac{1}{240} = \frac{5}{240} \Rightarrow \frac{240}{5} \Omega = R_{eff}$$

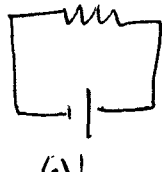
\Rightarrow  $R_{eff} = 48 \Omega$ #

$$\Rightarrow I_T = \frac{6V}{48\Omega} = \frac{1}{8} A$$

27-80


A current of $\frac{6V}{240\Omega} = 0.025A$ through 240Ω (effective resist)

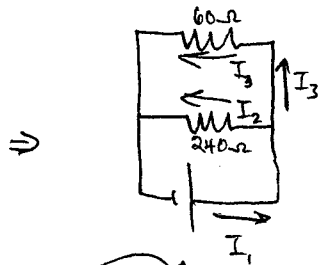A current of $\frac{6V}{60\Omega} = \frac{1}{10}A = 0.1A$ through 60Ω (effective resistor),



$$I_1 = I_2 + I_3 = 0.125A \quad \checkmark$$
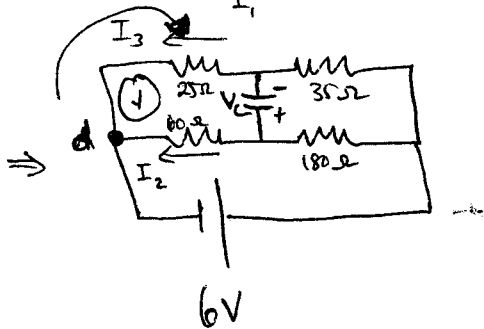
$$I_2 = 0.025A \quad \& \quad I_3 = 0.1A$$



Applying Kirchhoff's Rules to loop labeled

①

$$\Delta V_{\text{loop}} = 0 = I_3(25\Omega) + V_c - I_2(60\Omega) -$$

I have assumed top plate of capacitor is (-) w.r.t. bottom plate!
so $V_b < V_e$ (in my assumption).

$$\Rightarrow V_c = 60I_2 - 25I_3 = 60(0.025A) - 25(0.1A)$$

$$V_c = 1.5V - 2.5V = -1V$$

$\Rightarrow V_b > V_e$ so my assumption was incorrect!

$$\boxed{V_b - V_e = +1V} \Rightarrow \underline{\text{Top plate is (+).}}$$

$$(a) \quad \boxed{Q = (1V)(5\mu F) = 5\mu C}$$

(b) Current through 35Ω resistor is $I_3 = 0.1A$

#