

Last Name:

First Name:

## Physics 102 Spring 2006: Test 2—Free Response and Instructions

- Print your LAST and FIRST name on the front of your blue book, on this question sheet, the multiple-choice question sheet and the multiple-choice answer sheet.
- TIME ALLOWED 90 MINUTES
- The test consists of two free-response questions and 15 multiple-choice questions.
- The test is graded on a scale of 100 points; the free-response questions are worth a total of 70 points, and the multiple-choice questions account for 30 points (two points each).
- Answer the two free-response questions in your blue book. Answer the multiple-choice questions by marking a dark X in the appropriate column and row in the table on the multiple-choice answer sheet.
- Consult no books or notes of any kind. You may use a hand-held calculator in non-graphing, non-programmed mode.
- Do NOT take test materials outside of the class at any time. Return this question sheet along with your blue book and multiple-choice question sheet.
- Write and sign the Pledge on the front of your blue book.

\*\*\*\*\*


Show your work for the free-response problems, including neat and clearly labeled figures, in your blue book.

Answers without explanation (even correct answers) will not be given credit.

\*\*\*\*\*

I. (35 pts) The sketch below shows a simple  $RC$  circuit. The capacitor is initially uncharged, and at  $t = 0$  the switch  $S$  is closed. Express your answers in terms of  $V_0$ ,  $R_1$ ,  $R_2$ , and  $C$ .

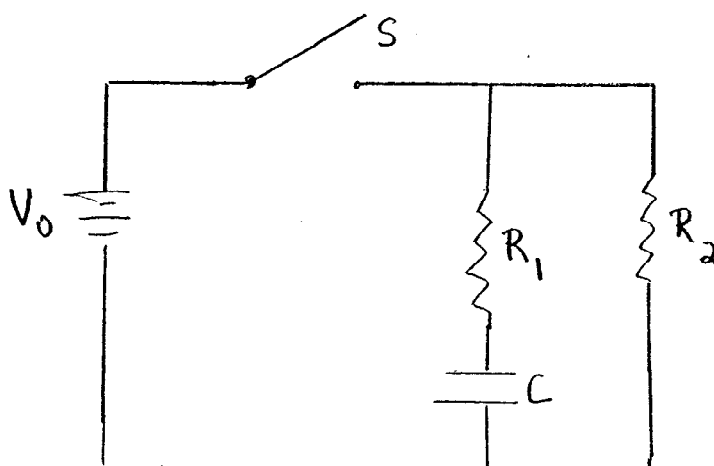- (a) Determine the current through each resistor immediately after the switch is closed.
- (b) Determine the charge on the capacitor  $Q(t)$  as a function of time after the switch is closed. What are the initial charge  $Q(t = 0)$ , the final charge  $Q(t \rightarrow \infty)$ , and the time constant? Sketch  $Q(t)$  vs.  $t$ .
- (c) Determine the current through the capacitor  $I(t)$  as a function of time after the switch is closed. What are the initial current  $I(t = 0)$ , the final current  $I(t \rightarrow \infty)$ , and the time constant? Sketch  $I(t)$  vs.  $t$ .
- (d) Determine the current through each resistor a long time after the switch is closed.
- (e) After the switch has been closed for a long time, it is opened again. Determine the current through the capacitor  $I(t)$  as a function of time after the switch is opened. What are the initial current  $I(t = 0)$ , the final current  $I(t \rightarrow \infty)$ , and the time constant in this case? Sketch  $I(t)$  vs.  $t$ .




$$\ln(Q - V_0 C) = -t/R_1 C + A$$

$$Q(t) = V_0 C + B e^{-t/R_1 C}$$

$$Q(t=0) = 0 \Rightarrow B = -1$$

$$Q(t) = V_0 C (1 - e^{-t/R_1 C})$$

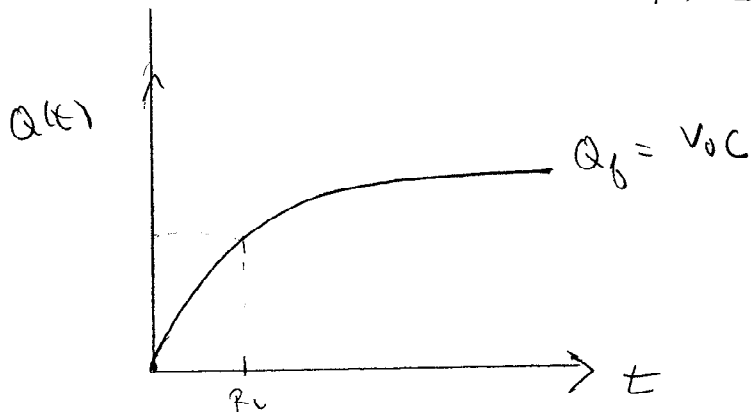
$$\begin{aligned} Q(t=0) &= 0 \\ Q(t \rightarrow \infty) &= V_0 C \end{aligned}$$



$$(c) I = \frac{dQ}{dt} = -V_0 C \left( \frac{-1}{R_1 C} \right) e^{-t/R_1 C}$$

$$I(t) = \frac{V_0}{R_1} e^{-t/R_1 C}$$
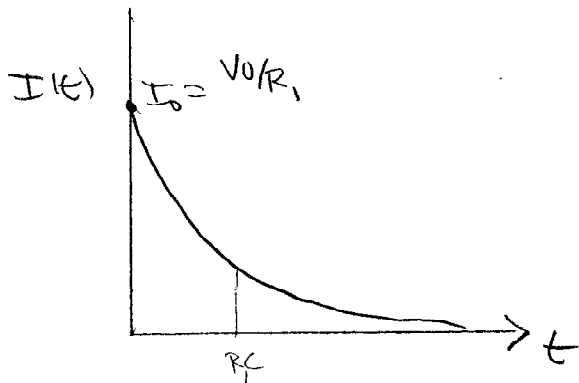
$$\begin{aligned} I(t=0) &= \frac{V_0}{R_1} \\ I(t \rightarrow \infty) &= 0 \end{aligned}$$




(d) A long time after the switch is closed, C acts like an open circuit:

$$I_1(t \rightarrow \infty) = 0 \quad I_2(t \rightarrow \infty) = \frac{V_0}{R_2}$$

The current in  $R_2$  is unchanged.

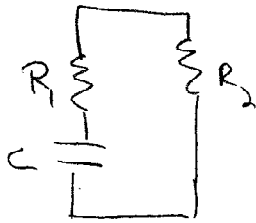(e) When S is opened again, the capacitor discharges through both  $R_1$  &  $R_2$  in series



$$R_{\text{eff}} = R_1 + R_2 \quad \tau = (R_1 + R_2)C$$


$$I(t) = I_0 e^{-t/(R_1 + R_2)C}$$

Before S is opened, C is charged to  $V_0$ .

$$I(0) = \frac{V_0}{R_1 + R_2} \text{ is the initial current}$$

$$I(t) = \frac{V_0}{R_1 + R_2} e^{-t/(R_1 + R_2)C}$$


$$I(t \rightarrow \infty) = 0$$

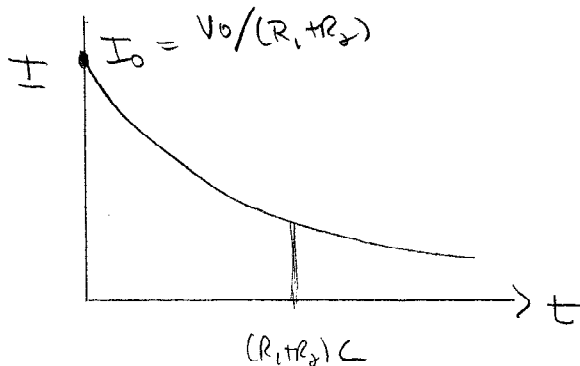


The time constant is longer for discharging.


35 II. (35 pts) Three very long parallel wires are arranged as shown below. Two wires, which carry current  $I$  out of the page, pass through the points  $y = 0, x = \pm a$ . The third wire carries a current  $I$  into the page and is located at the point  $x = 2a, y = -a$ .

- 8 (a) Determine the magnetic field at the location of the top left wire ( $x = 0, y = a$ ) due to the other two wires.
- 5 (b) Determine the force per unit length on the top left wire.
- 9 (c) Determine the magnetic field  $\vec{B}_{12}(x)$  due to the two wires located at  $x = 0, y = \pm a$  at an arbitrary point  $P$  on the  $x$ -axis, a distance  $x$  from the origin.
- 10 (d) Determine the magnetic field  $\vec{B}_3(x)$  at the point  $P$  due to the single wire at  $x = 2a, y = -a$ .
- 3 (e) From (c) and (d), determine the total magnetic field at the point  $P$ .

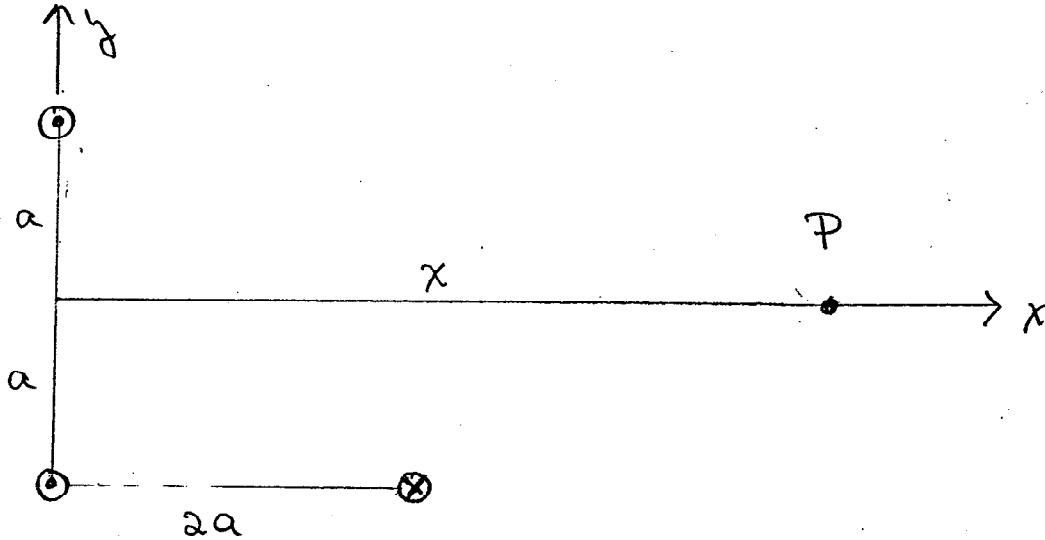


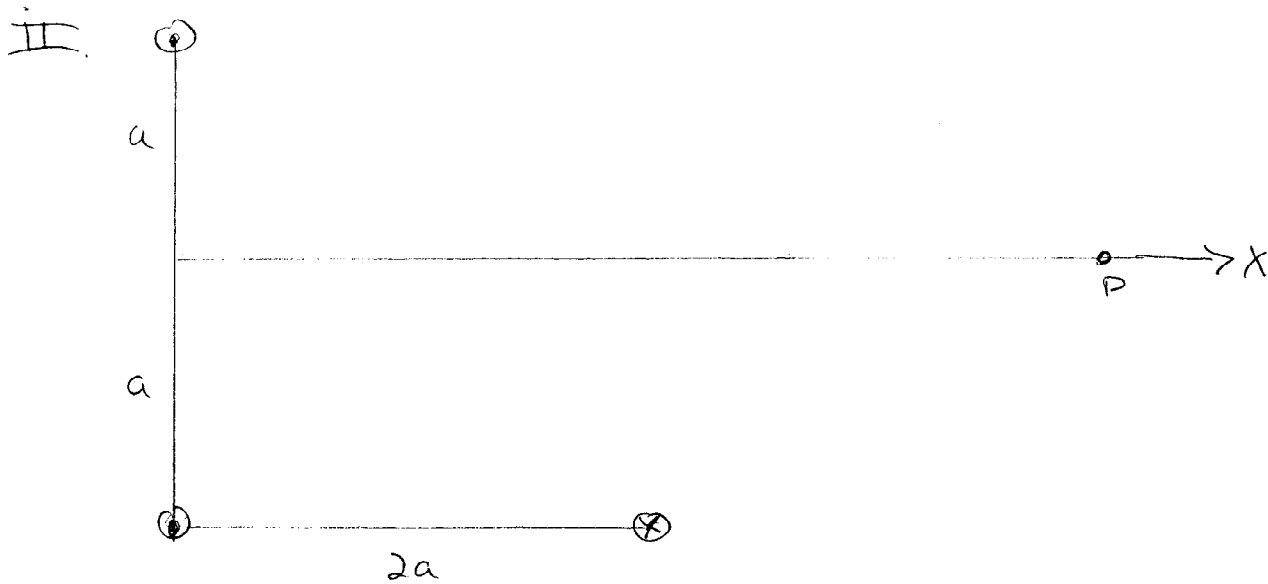

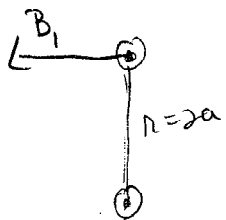(a)  $\vec{B}$  at top left due to the other two wires



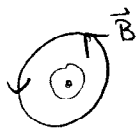From Ampere's law we know that the field due to a long wire forms concentric loops




$$\oint \vec{B} \cdot d\vec{l} = \mu_0 I$$

$$B = \frac{\mu_0 I}{2\pi r}$$

This gives  $\vec{B}_1$  (due to lower left wire) =  $\frac{\mu_0 I}{4\pi a} (-\hat{i})$

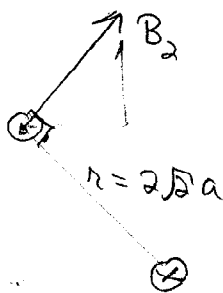$\vec{B}_2$  due to the lower right wire will be at  $45^\circ$ :



$$\vec{B}_2 = \frac{\mu_0 I}{4\pi(2\sqrt{2}a)} \left( \frac{1}{\sqrt{2}} \hat{i} + \frac{1}{\sqrt{2}} \hat{j} \right)$$

$$\vec{B}_{TOT} = \vec{B}_1 + \vec{B}_2 = \frac{\mu_0 I}{4\pi a} \left( -\frac{1}{2} \hat{i} + \frac{1}{2} \hat{j} \right)$$


(b)  $F/L$  on top left wire

$$\vec{F} = I \vec{L} \times \vec{B} \quad \vec{L} = L \hat{k} \quad \text{current in } +z \text{ direction}$$

$$\vec{F} = IL \left( \frac{\mu_0 I}{4\pi a} \right) \left( \underbrace{-\frac{1}{2} \hat{k} \times \hat{i}}_{-\frac{1}{2} \hat{j}} + \underbrace{+\frac{1}{2} \hat{k} \times \hat{j}}_{-\frac{1}{2} \hat{i}} \right)$$

$$\vec{F}/L = \frac{\mu_0 I^2}{4\pi a} \left( -\frac{1}{2} \hat{i} - \frac{1}{2} \hat{j} \right)$$

(c)

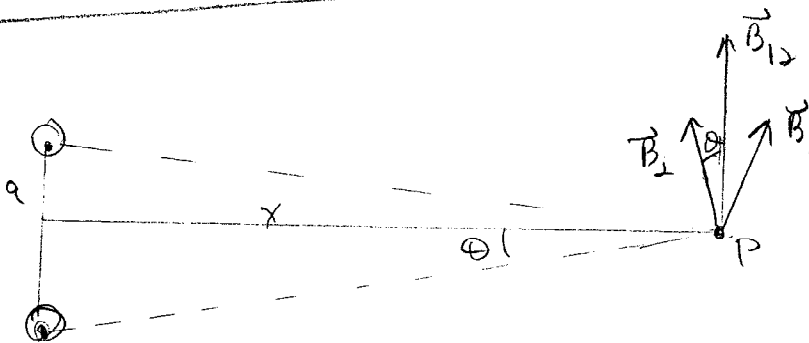

The horizontal components cancel - vertical components add


$$B_{2y} = B_{1y} = B_1 \cos \theta \quad \cos \theta = \frac{x}{\sqrt{x^2 + a^2}}$$

$$|B_1| = \frac{\mu_0 I}{2\pi (x^2 + a^2)^{3/2}}$$

$$\vec{B}_{12}(x) = \frac{2\mu_0 I x}{2\pi (x^2 + a^2)^{3/2}} \hat{j} = \frac{\mu_0 I x}{\pi (x^2 + a^2)^{3/2}} \hat{j}$$

Factor of 2 comes from adding the two contributions

(d)

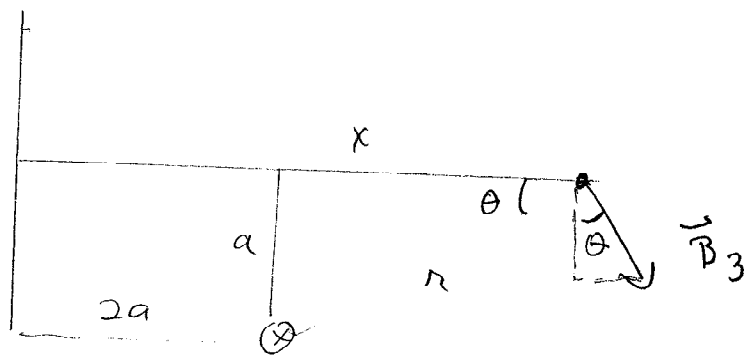

$$|B_3| = \frac{\mu_0 I}{2\pi r} \quad \text{where } r = (a^2 + (x-2a)^2)^{\frac{1}{2}}$$

$\vec{B}_3$  has both x & y components

$$B_{3x} = B_3 \sin\theta \quad B_{3y} = -B_3 \cos\theta$$

$$\sin\theta = \frac{a}{[(x-2a)^2 + a^2]^{\frac{1}{2}}}$$

$$\cos\theta = \frac{x-2a}{[(x-2a)^2 + a^2]^{\frac{1}{2}}}$$

$$\vec{B}_3 = \frac{\mu_0 I}{2\pi [(x-2a)^2 + a^2]^{\frac{1}{2}}} \left[ \frac{a}{[(x-2a)^2 + a^2]^{\frac{1}{2}}} \hat{i} + \frac{x-2a}{[(x-2a)^2 + a^2]^{\frac{1}{2}}} \hat{j} \right]$$

$$\vec{B}_3 = \frac{\mu_0 I}{2\pi [(x-2a)^2 + a^2]} \left[ a \hat{i} - (x-2a) \hat{j} \right]$$

Note that the y-component changes sign for  $x < 2a$ ,  
our expression works for both cases.

(e) Superposition tells us we just add the contributions

$$\vec{B}_{\text{TOT}} = \frac{\mu_0 I}{2\pi} \left[ \frac{a}{(x-2a)^2 + a^2} \hat{i} + \left( \frac{x}{x^2 + a^2} - \frac{x-2a}{(x-2a)^2 + a^2} \right) \hat{j} \right]$$