

Physics 112 Laboratory Report

Simple Oscillators

Name _____

Date _____

Lab Partner _____

Free oscillations

On a separate sheet, sketch one example each of underdamped, critically damped and overdamped decays, indicating the time scale on each.

Measured decay time τ when $R = 0$ _____

Driven oscillations

Resonant frequency f_0 _____

On a separate sheet, sketch v_C vs frequency. Does it look like Fig. 3?

Approximate phase shift at f_0 _____

Approximate phase shift at $f \ll f_0$ _____

Approximate phase shift at $f \gg f_0$ _____

Are the phase shifts consistent with Fig. 3?

Frequencies for which v_C is reduced by $1/\sqrt{2}$ _____

Resonant width $\Delta\omega$ _____

Provide estimates of Q from the

resonant width $\Delta\omega$ _____

ratio of v_C to v_D _____

decay time τ _____

Are these estimates of Q consistent?

Radio circuit

capacitor setting	frequency (MHz)

Do these frequencies fall within the AM radio band?

Attach sketches of the voltage waveforms at the following locations. Clearly indicate the zero-voltage level in each sketch.

- (a) Across the capacitor, with modulation on, but without the diode in the circuit.
- (b) Across the $1k\Omega$ resistor, with the diode in place.
- (c) Across the earphone, with the diode in place.

Explain the difference between (a) and (b) in terms of the action of the diode.

Explain the lack of high frequency (near 1 MHz) signal in (c). Why is the time-average of this waveform not zero?

Describe some of the radio stations you can hear:

capacitor setting	program